

Concurrent Operation of Wireless Power Transfer Based Contactless Slip Ring and Motor Drive System with a Single Converter

Enes Ayaz

M.Sc. Thesis Defense

Middle East Technical University (METU), Department of Electrical and Electronics Engineering Ankara, TURKEY


September 2022




Outline

- 1. Aim of Study**
2. Wireless Power Transfer System Basics
3. Theory Of Operations
4. Implementation for DC Motor
5. Implementation for AC Motor
6. Implementation for field excitation
7. Conclusion

Power Transfer to Rotating Frames

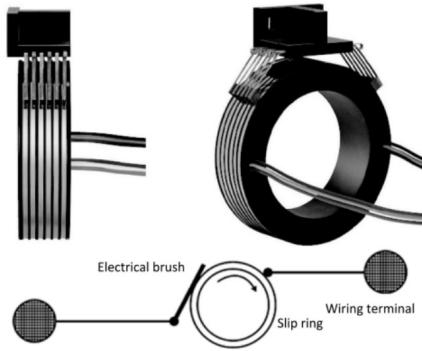


Slip Rings

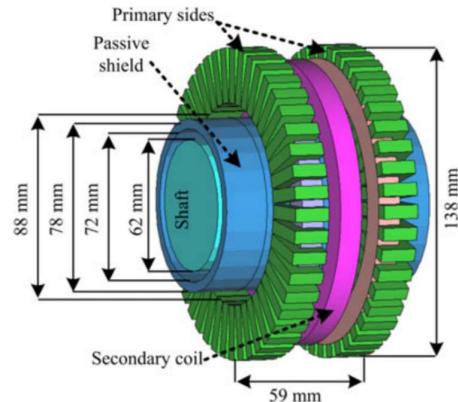


Contactless

Slip Rings

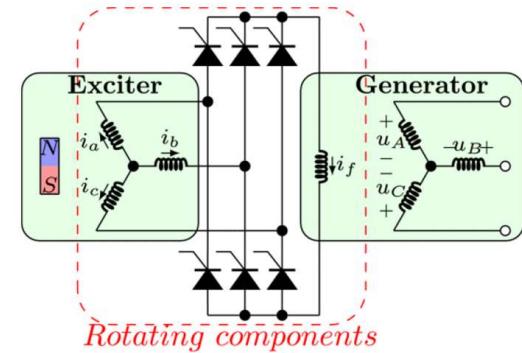


Brushless Exciter

Power Transfer to Rotating Frames

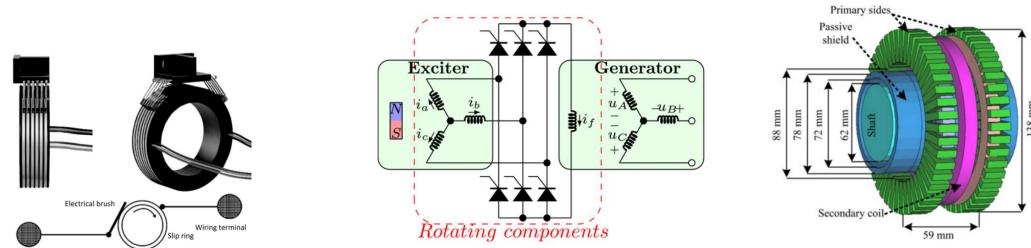

	Slip Rings	Brushless Exciters	Contactless Slip Rings
Reliability	-	+	+
Maintenance	-	+	+
Simplicity	+	+	-
Speed Independence	+	-	+
Cost Effectivity	+	+	-
Efficiency	+	-	+

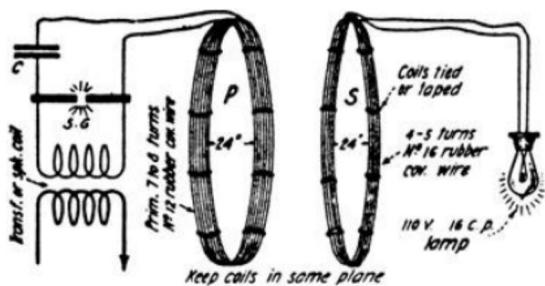
Wireless Power Transfer Based Contactless Slip Rings



Tesla's WPT System


	Inductive Power Transfer	Capacitive Power Transfer
Transfer Type	Varying MF	Varying EF
Power Ratings	High	Low
Frequencies	Low	High
Efficiency	High	High
Distance	Moderate	Low

Inductive Power Transfer

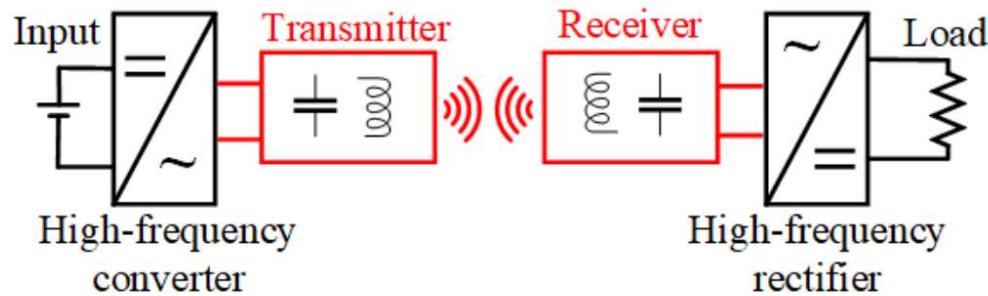

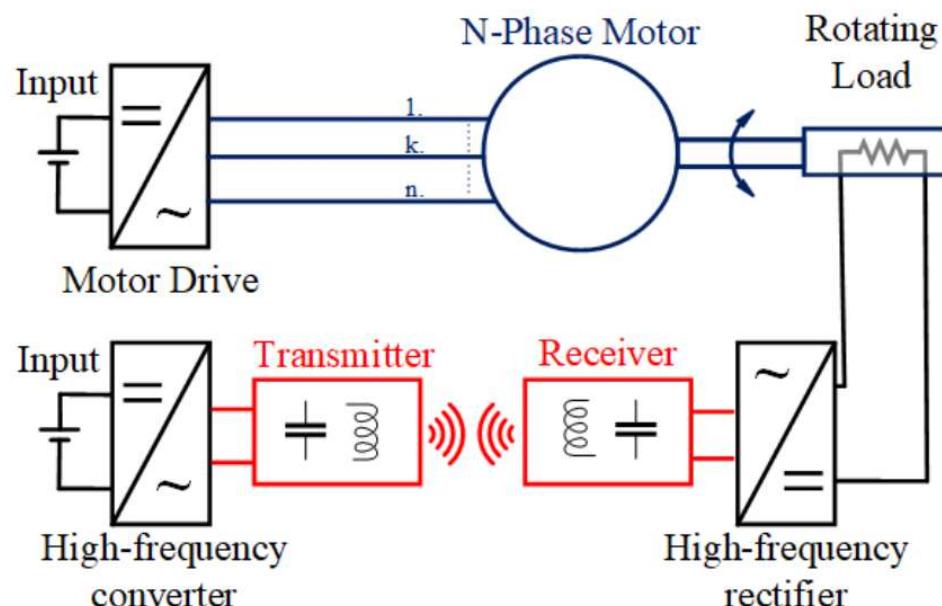1. DC/AC converter
2. Compensation Circuits
3. Transmitter/Receiver Coils
4. AC/DC Rectifiers

Conventional Inductive Power Transfer Based Contactless Slip Ring



Two converters:

1. To drive the motor
2. To excite the Tx coil

Motor → attenuated in motor current


The motor drive → generating low and high frequency

Motor → used to drive

The WPT converter → generating high frequency

The WPT system → behaves like band-pass filter

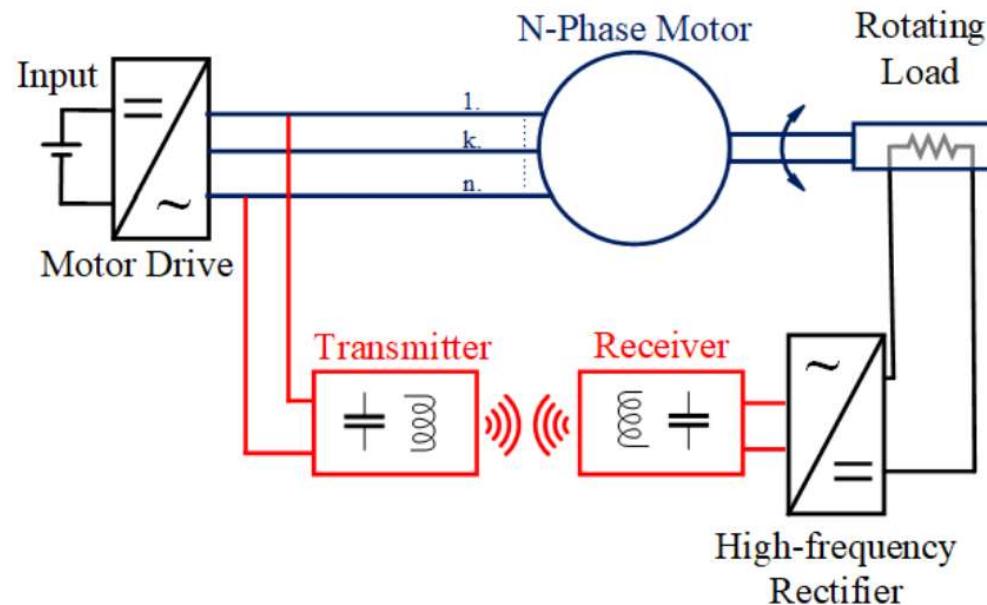Proposed Inductive Power Transfer Based Contactless Slip Ring



The motor drive → generating high frequency
combining

The WPT system → behaves like band-pass filter

eliminating
The WPT converter → generating high frequency



Proposed Inductive Power Transfer Based Contactless Slip Ring

	Conventional Contactless Slip Ring	Proposed Contactless Slip Rings
Reliability	+	+
Maintenance	+	+
Simplicity	-	+
Speed Independence	+	+
Cost Effectivity	-	+
Efficiency	+	+


Outline

1. Aim of Study
2. **Inductive Power Transfer System Basics**
3. Theory Of Operations
4. Implementation for DC Motor
5. Implementation for AC Motor
6. Implementation for field excitation
7. Conclusion

Inductive Power Transfer System

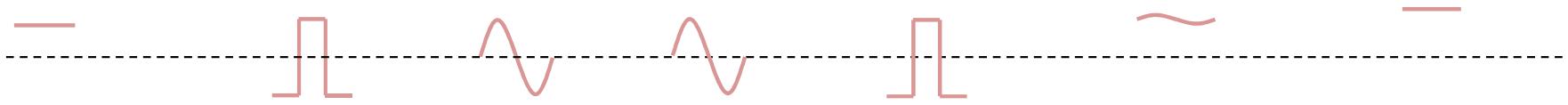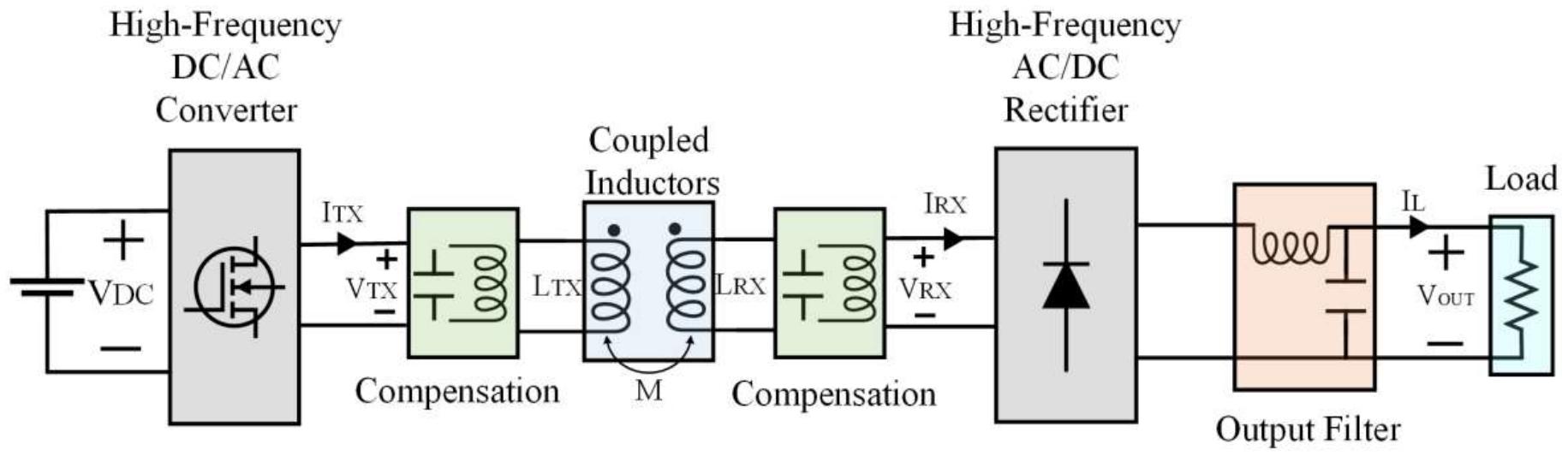




Compensation Topologies

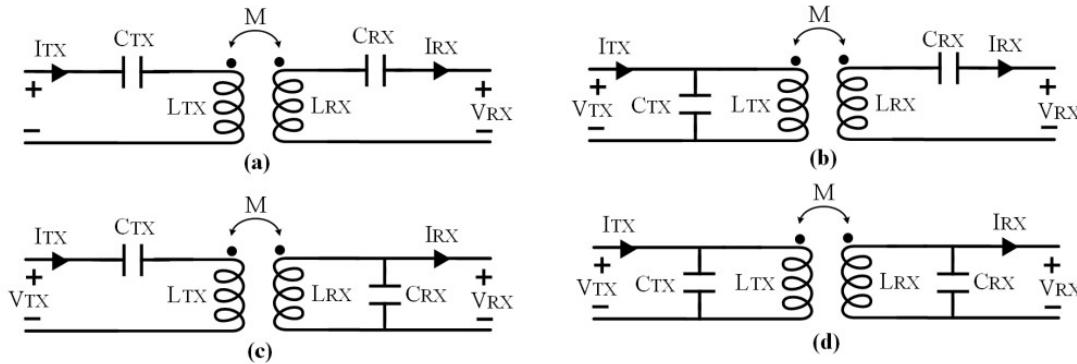


- a)** Series-series
- b)** Parallel-series
- c)** Series-parallel
- d)** Parallel-parallel

Series-Series Compensation	
Source Type	Voltage Source
Resonant frequency	Load Independent
Resonant frequency	Coupling Independent
No load operation	Short Circuit
Capacitor Size	Large

Series-Series IPT System

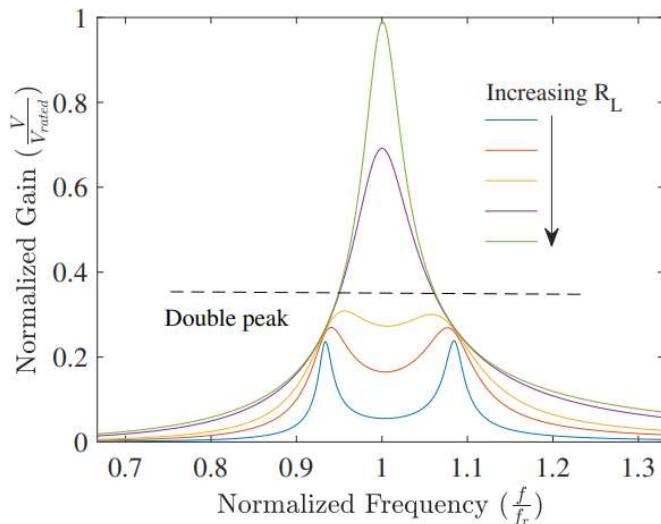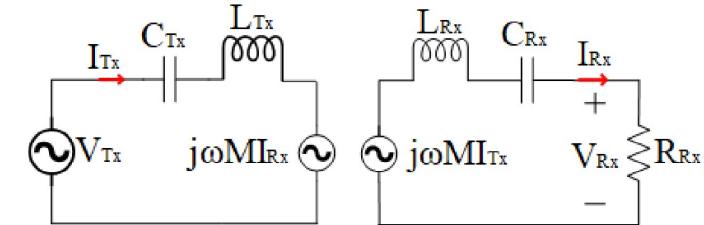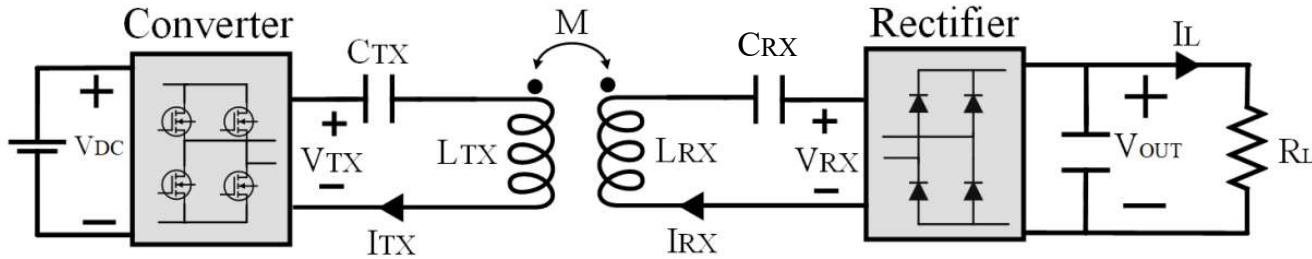

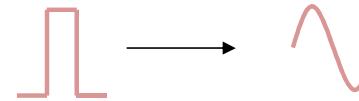
Single-peak band pass filter
 ↓
 First Harmonic Approach (FHA)





Phase < 0 → Inductive region

$f_{op} > f_r \rightarrow$ Inductive region
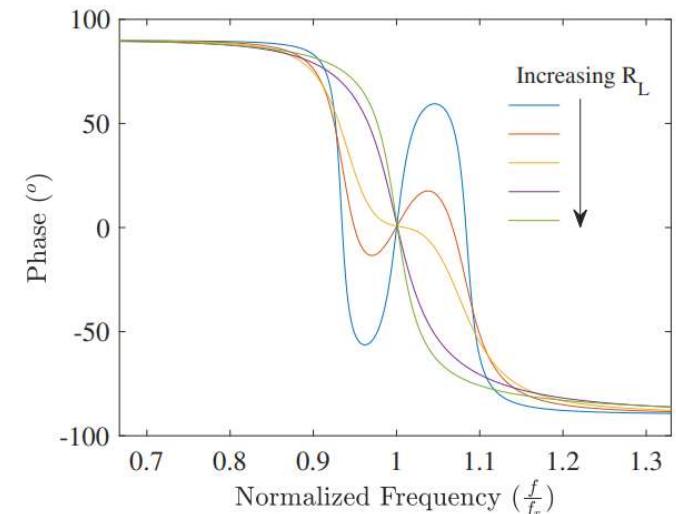
$$f_r = \frac{1}{\sqrt{L_{Tx}C_{Tx}}} = \frac{1}{\sqrt{L_{Rx}C_{Rx}}}$$




Zero Voltage Switching

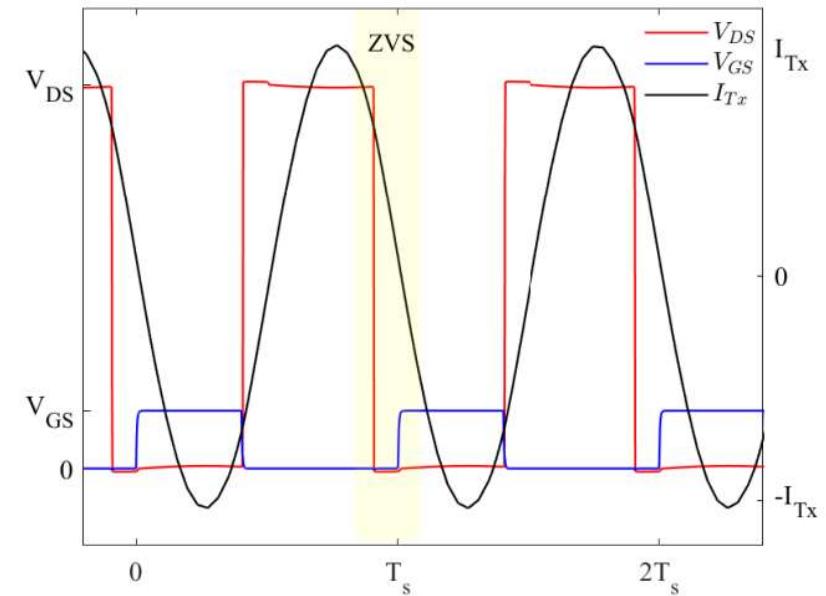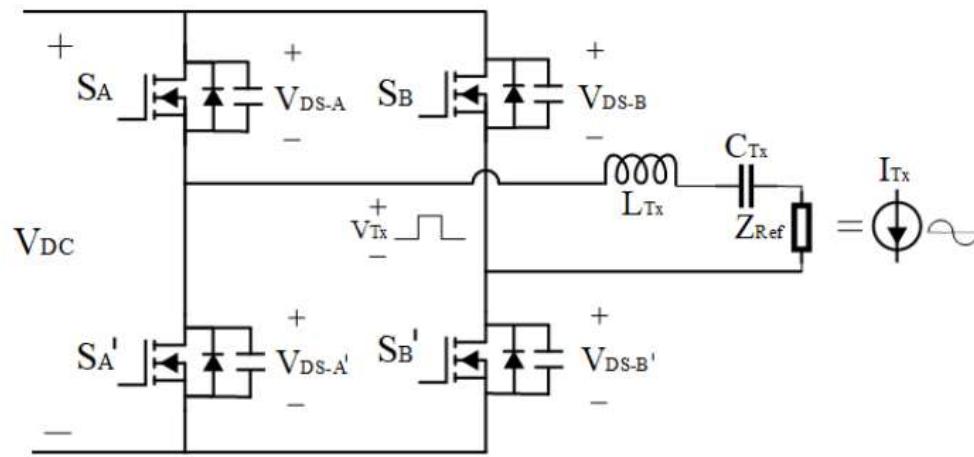


Inductive region → The capacitance of the switches discharges by the load current during dead time.

Bifurcation Phenomenon

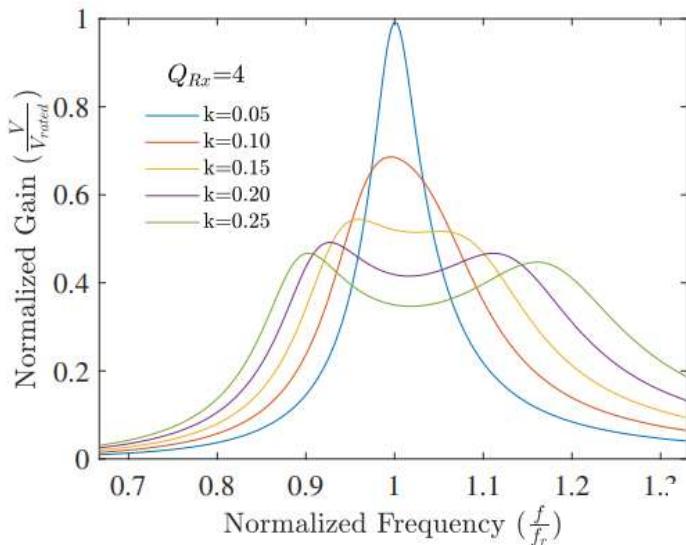

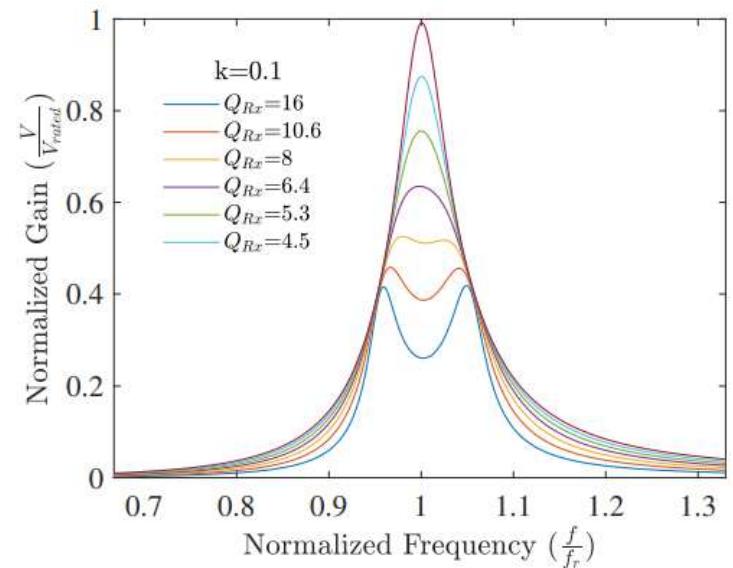- Double-peak
- $f_{op} > f_r \rightarrow$ Inductive region
- Making control difficult
 - Decreasing efficiency



$$k_c = \frac{1}{Q_{Rx}} \sqrt{1 - \frac{1}{4Q_{Rx}^2}}$$




Multifrequency IPT Systems

Aims:

1. To Increase power
2. To reduce switching components
3. To increase DC-link utilization rate
4. Operating in more than one standards

Studies:

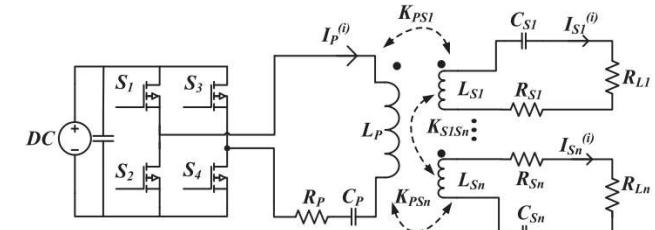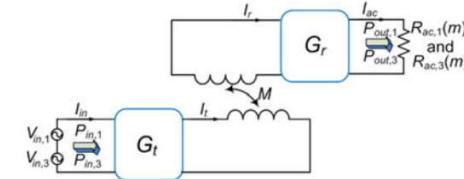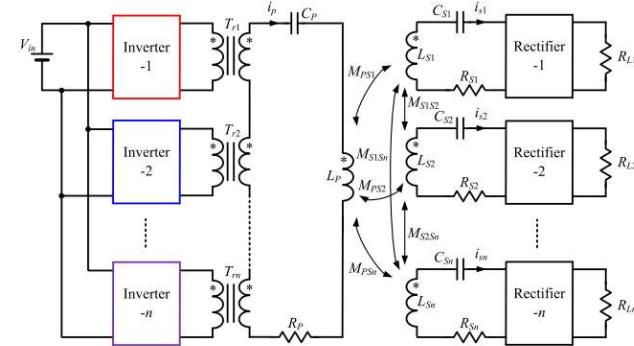
1. Multi-converter and multi-resonant
2. Single-converter and multi resonant
3. Single-converter and multi-load



Outline

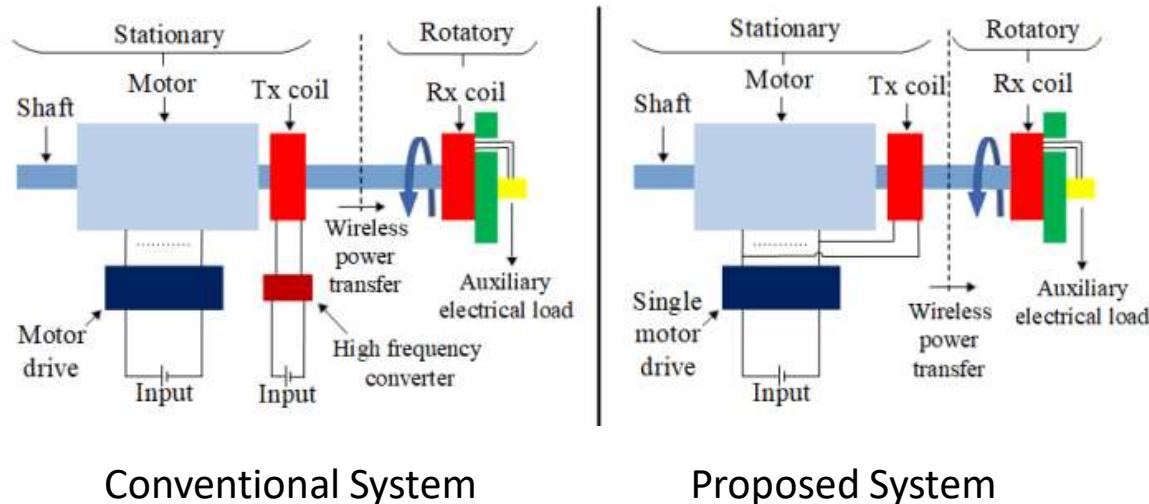1. Aim of Study
2. Inductive Power Transfer System Basics
3. Theory Of Operations
4. Implementation for DC Motor
5. Implementation for AC Motor
6. Implementation for field excitation
7. Conclusion

The Proposed Contactless Slip Ring Method




Conventional System

Proposed System


Motor Drives

- DC motor drive
- AC motor drive



DC Motor Drives

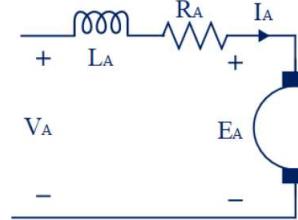


Varying
armature voltage

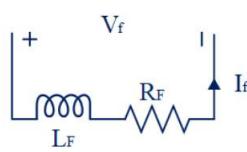

Constant field
excitation

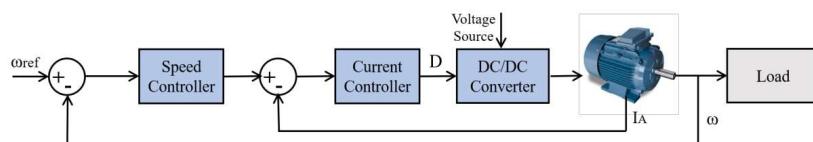
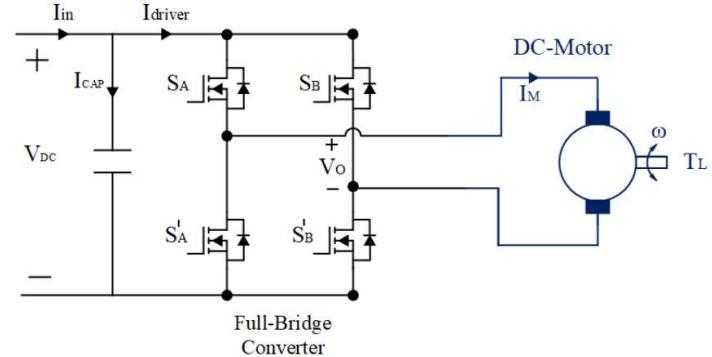


Control diagram



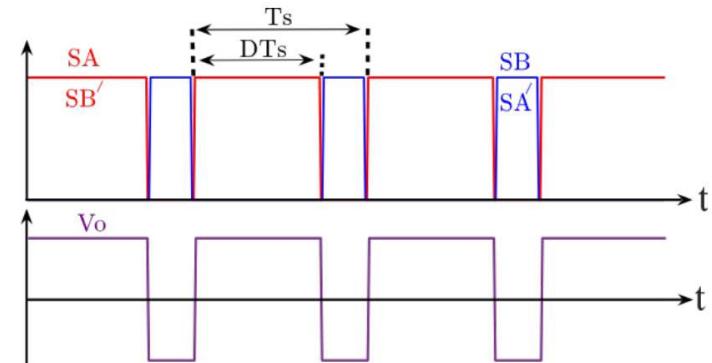


Proposed Modulation Technique

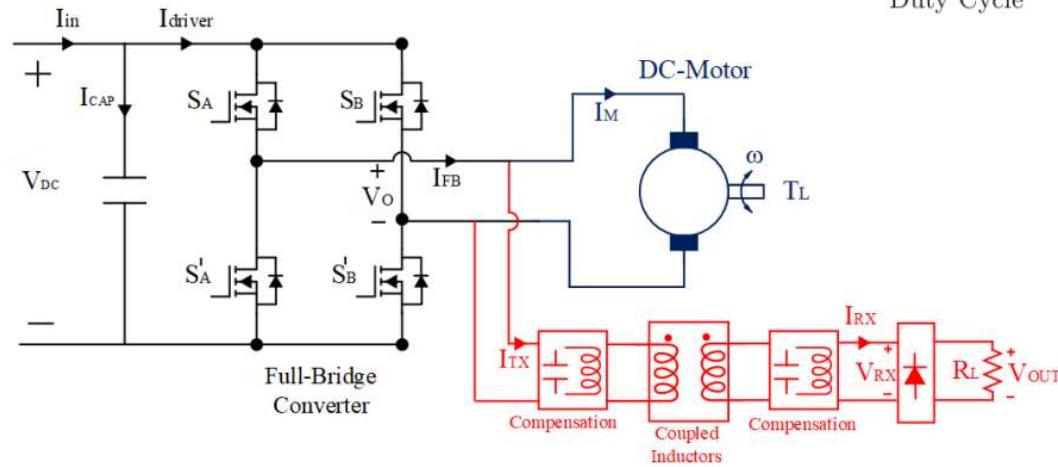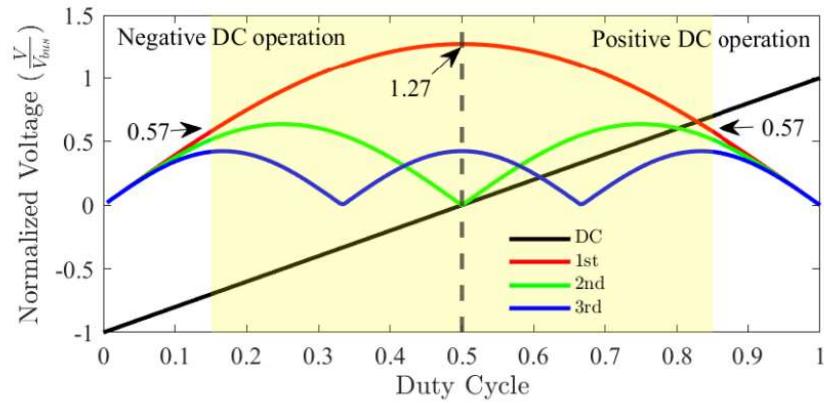
$$S(t) = D + \sum_{k=1}^{\infty} \frac{2}{k\pi} \sin(k\pi D) \cos(2\pi kf_s t)$$




Proposed Control Method

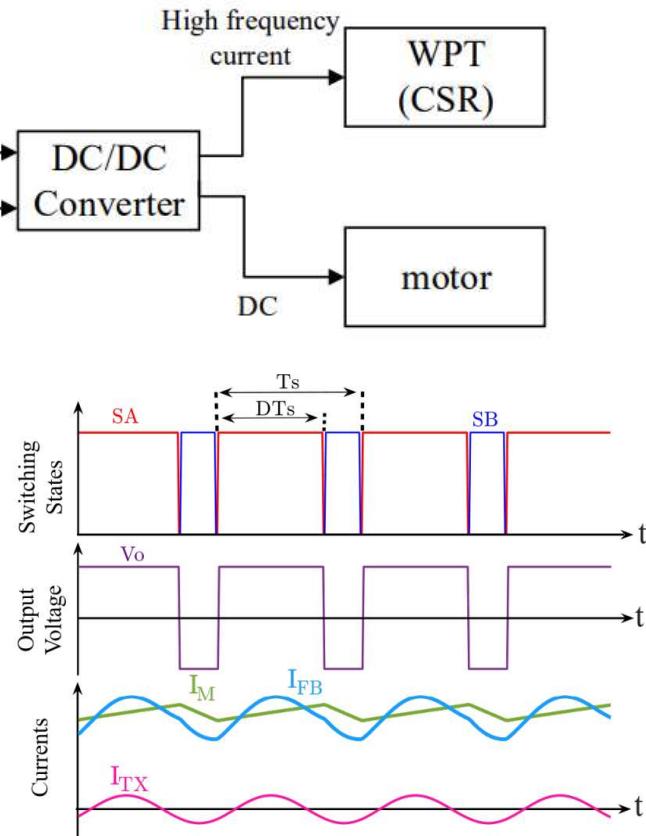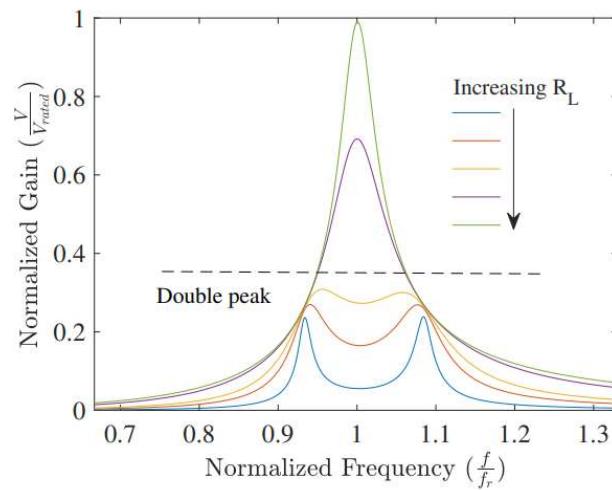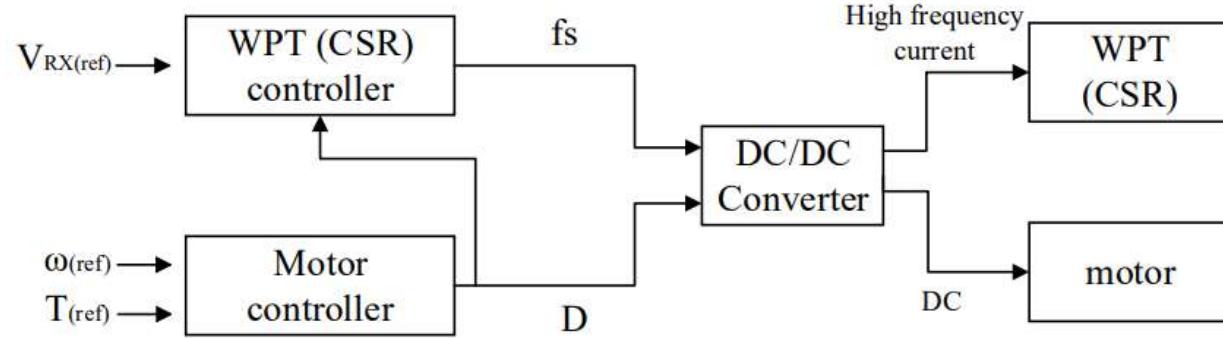

AC Motor Drives


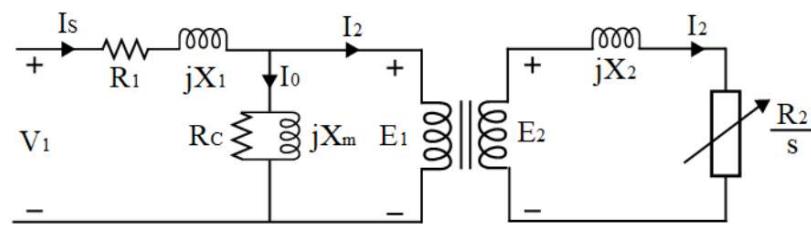


Induction motor

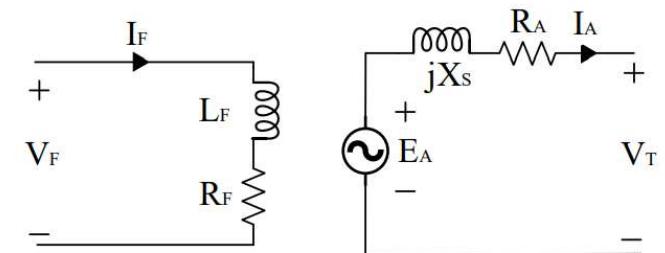

Synchronous motor



Varying armature voltage and frequency

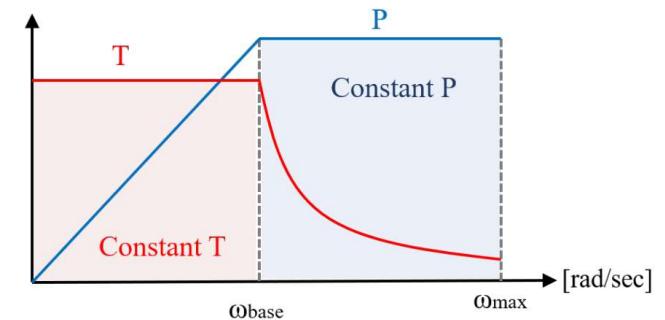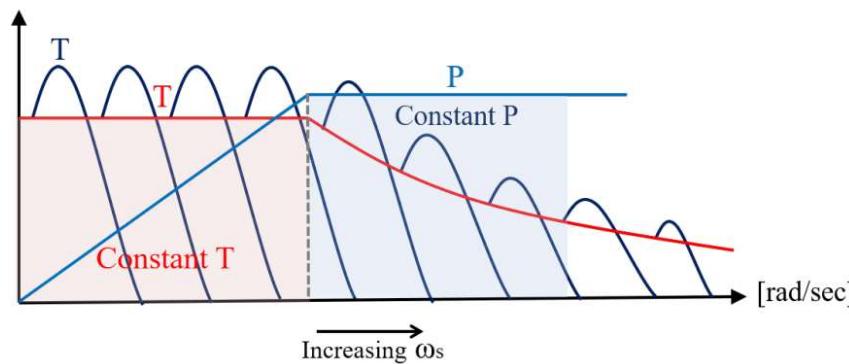

Conventional Modulation Technique

$$S = \frac{1}{2} + \frac{m_a}{2} \cos(\omega_o t + \theta_o) + \frac{2}{\pi} \sum_{i=1}^{i=\infty} J_o\left(i\frac{\pi}{2}m_a\right) \sin\left(i\frac{\pi}{2}\right) \cos\left(i(\omega_c t + \theta_c)\right) + \frac{2}{\pi} \sum_{i=1}^{i=\infty} \sum_{k=-\infty}^{k=\infty} \left(\cos\left(i(w_c t + \theta_c) + k(w_o t + \theta_o)\right) \right)$$

Frequency	Leg A	Leg B	Leg C	Sequence
f_o	0°	120°	-120°	Positive
$f_s - 2f_o$	0°	120°	-120°	Positive
f_s	0°	0°	0°	Zero
$f_s + 2f_o$	0°	-120°	120°	Negative

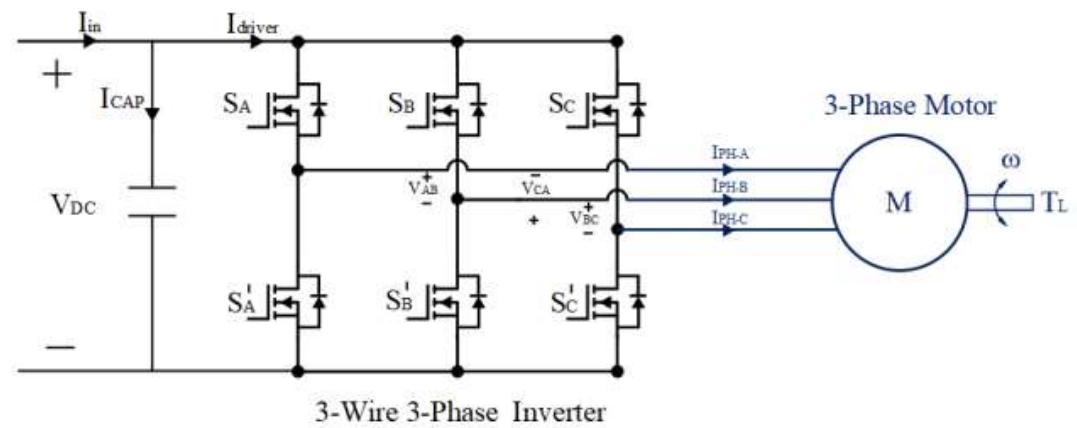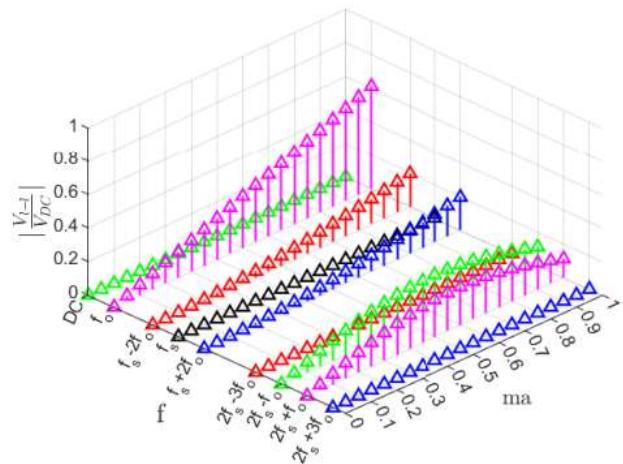


Proposed Modulation Technique

$$Carrier \text{ phases} \begin{cases} \phi_{cA} = 0 \\ \phi_{cB} = \phi_{CPS} \\ \phi_{cC} = 0 \end{cases}$$




$$V_{sl}(m_a) = \frac{2}{\pi} J_2 \left(m_a \frac{\pi}{2} \right) \sqrt{1 - \cos(\phi_{CPS} + 120^\circ)}$$

$$V_s(m_a) = \frac{2}{\pi} J_o \left(m_a \frac{\pi}{2} \right) \sqrt{1 - \cos(\phi_{CPS})}$$
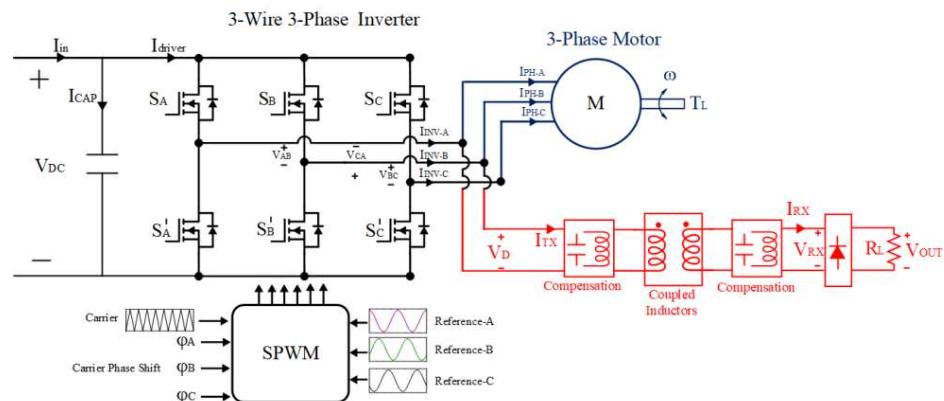
$$V_{sh}(m_a) = \frac{2}{\pi} J_2 \left(m_a \frac{\pi}{2} \right) \sqrt{1 - \cos(\phi_{CPS} - 120^\circ)}$$





Proposed Modulation Technique

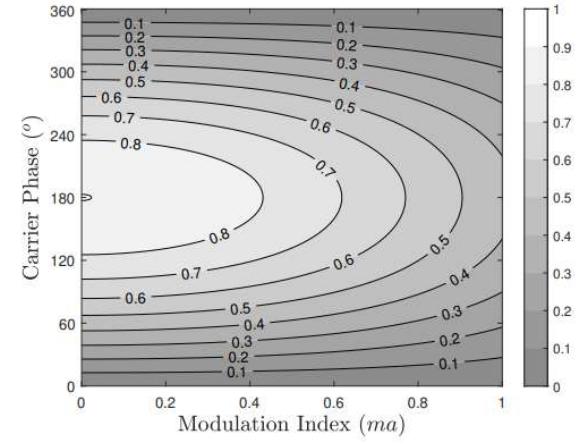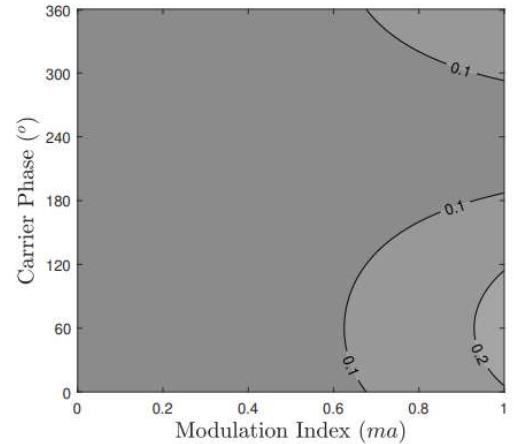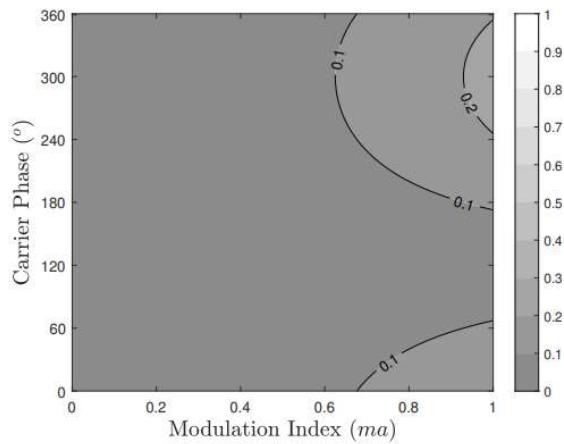


$$V_D = \sqrt{\left(V_{sl}^2 + V_{sw}^2 + V_{sh}^2 \right)}$$

Proposed Control Method

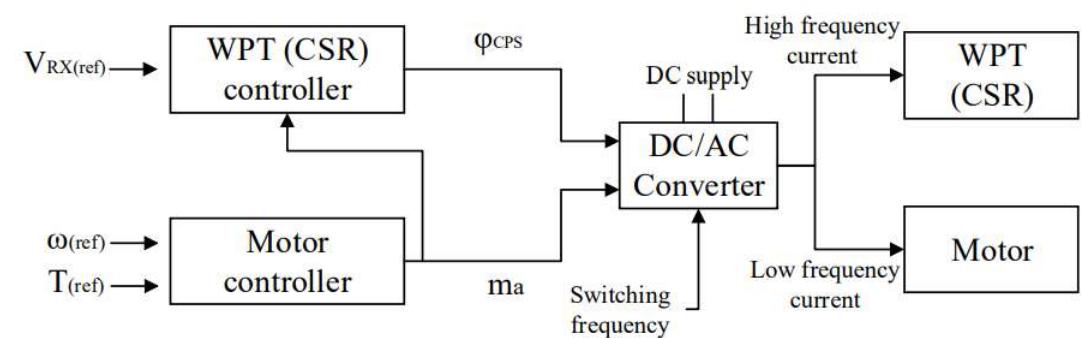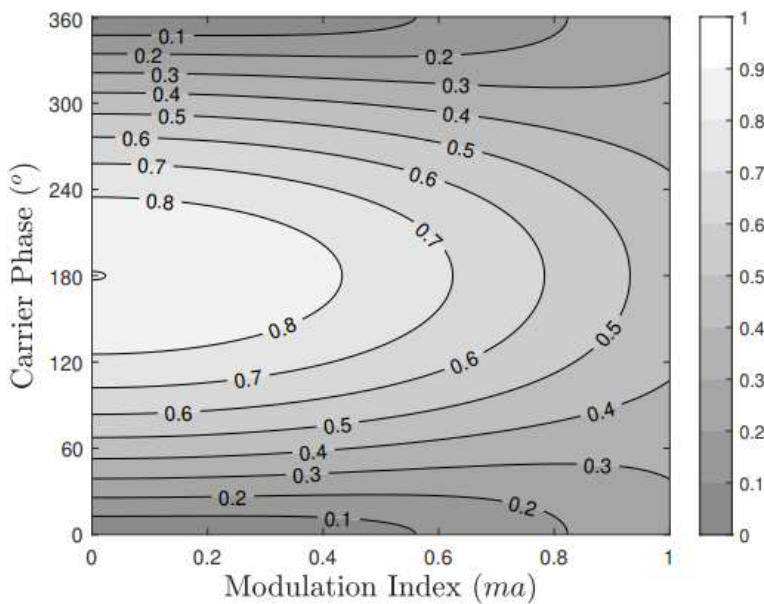



Practical Considerations

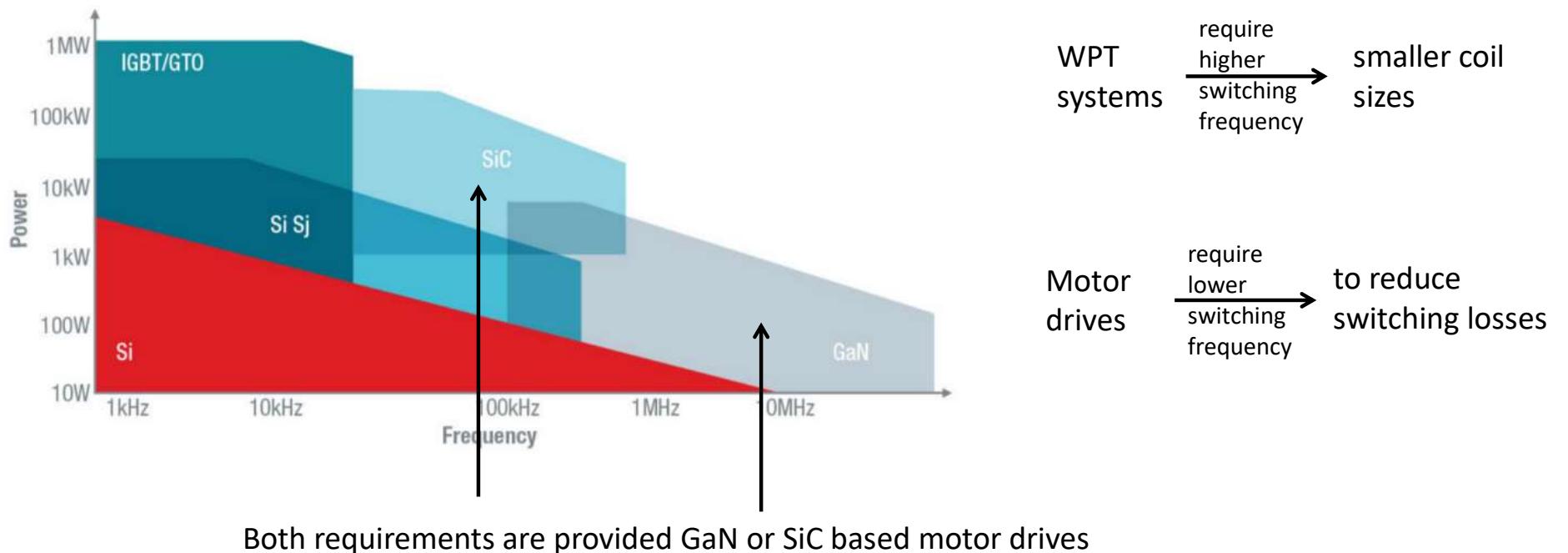

Outline

1. Aim of Study
2. Inductive Power Transfer System Basics
3. Theory Of Operations
- 4. Implementation for DC Motor**
5. Implementation for AC Motor
6. Implementation for field excitation
7. Conclusion

System Overview and Experimental Setup

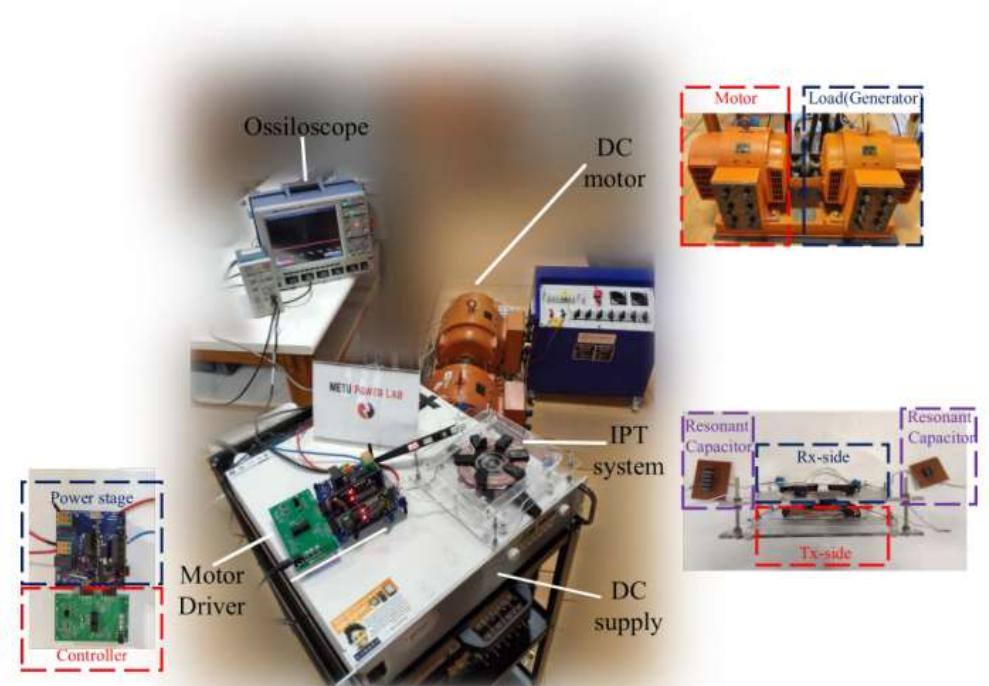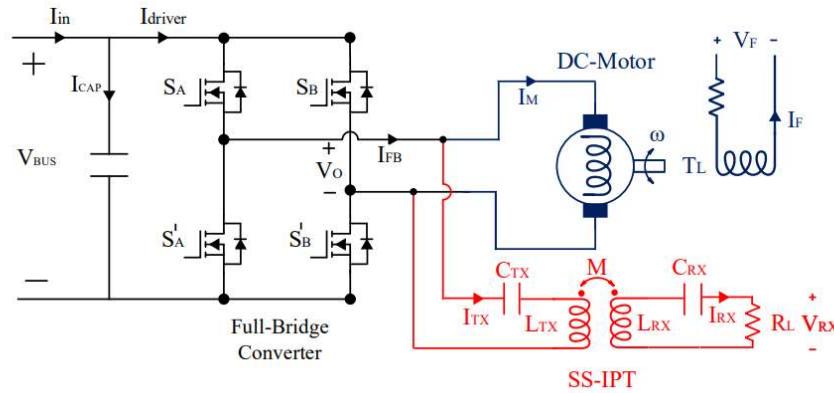

Wireless Power Transfer System Design

The Rated Voltages and Powers

Input Voltage (V_{BUS})	100 V _{DC}
IPT Output Voltage (V_{RX})	20 V _{RMS}
Motor Output Power (P_M)	500 W
IPT Output Power (P_o)	50 W

The Motor Parameters

Armature resistance (R_a)	2 Ω
Armature inductance (L_a)	7 mH
Motor electrical time constant (T_s)	3.5 ms

The Drive Parameters

Duty cycle(D)	0.15 – 0.85
Switching frequency (f_s)	< 100 kHz
Switching period (T_s)	> 10 μs

$$V_{o,1^{st}}(rms) = \frac{4}{\sqrt{2}\pi} V_{Bus} \sin(\pi D)$$


$$0.15 < D < 0.85$$

$$40 V_{RMS} < V_{o,1^{st}}(rms) < 90 V_{RMS}$$

$$Q_{RX} \rightarrow L_{RX} = \frac{Q_{RX} R_L}{\omega_0} \rightarrow M = \frac{V_{RX} V_{o,1^{st}}}{P_o \omega_0}$$


$$C_{TX,RX} = \frac{1}{L_{TX,RX}} \omega_0^2 \leftarrow L_{TX} = \frac{V_{o,1^{st}}^2}{k^2 \omega_0^2 Q_{RX}} \leftarrow k$$

Wireless Power Transfer System Design

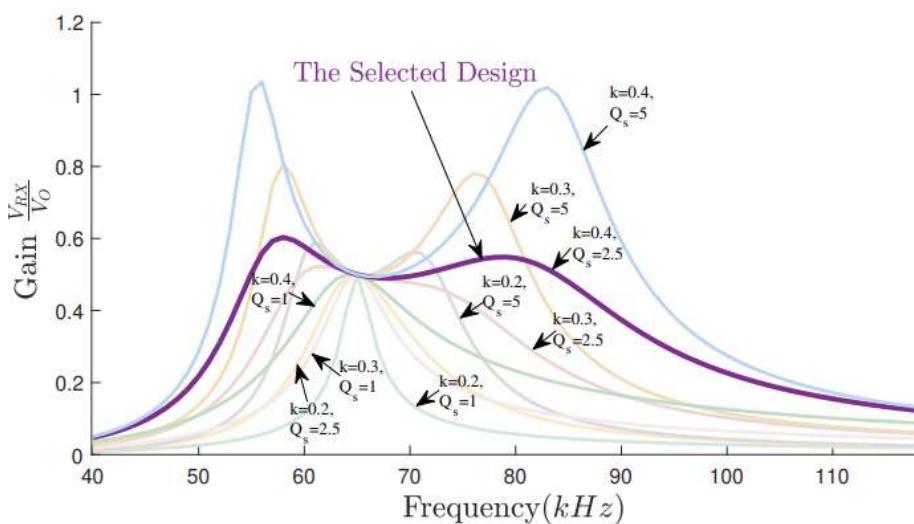




Receiver quality factor (Q_{RX})	2.6
Resonant frequency (f_0)	65 kHz
Coupling factor (k)	0.40
Load resistance (R_L)	8 Ω
Receiver coil inductance (L_{RX})	51 μ H
Mutual inductance (M)	41 μ H
Transmitter coil inductance (L_{TX})	205 μ H
Receiver resonant capacitance (C_{TX})	115 nF
Transmitter resonant capacitance (C_{RX})	29 nF
Voltage gain at f_0	0.5

Coil Design

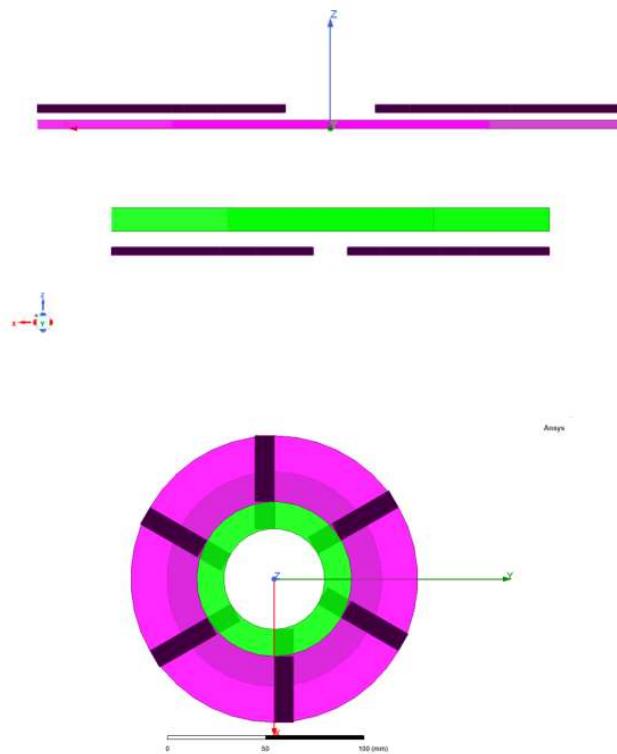


Tx-coil inner diameter	52 mm
Tx-coil outer diameter	110.6 mm
Tx number of layer	3
Tx conductor diameter	2 mm
Tx-coil total turns/turns per layer	44/15
Rx-coil inner diameter	80 mm
Rx-coil outer diameter	148 mm
Rx conductor diameter	2 mm
Rx-Coil total turns/turns per layer	17/17
Airgap	20 mm
Tx-coil inductance	$204 \mu\text{H}$
Rx-coil inductance	$52 \mu\text{H}$
Mutual inductance	$41 \mu\text{H}$

Impedance Modelling and Control

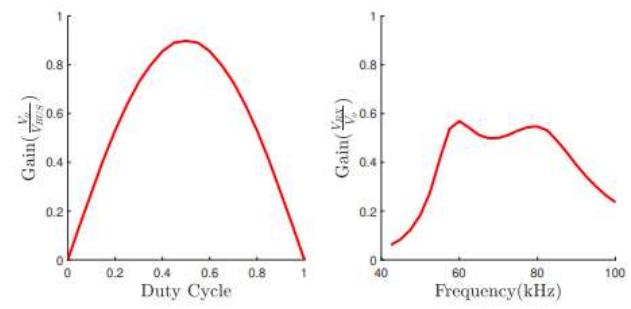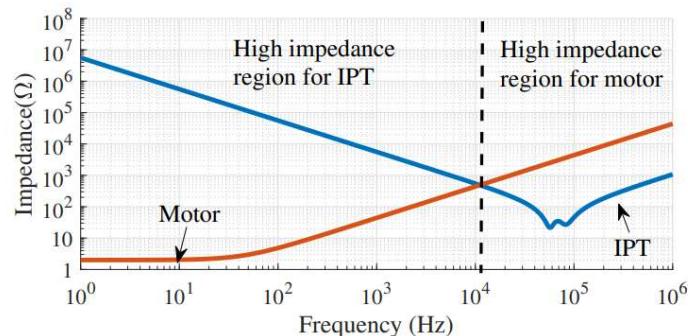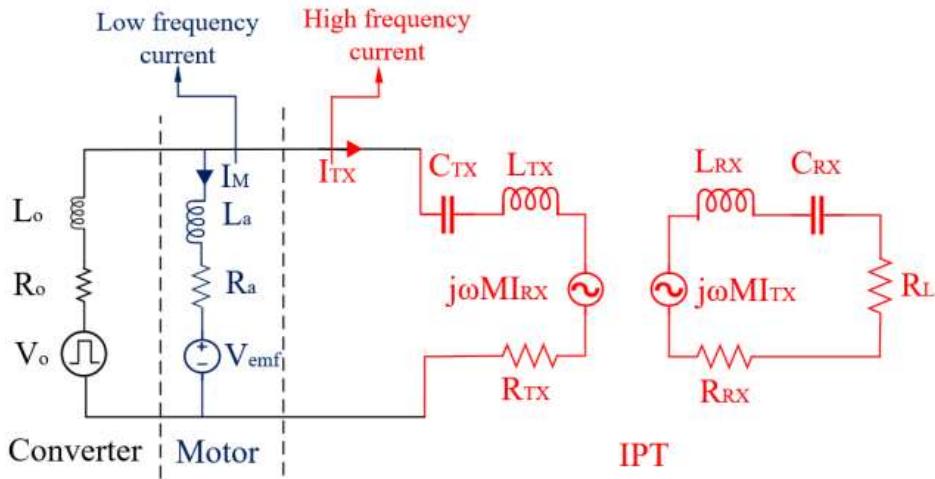

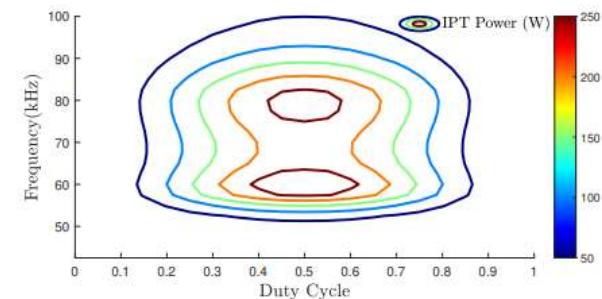
(a) Duty cycle-gain characteristic of IPT (b) Frequency-gain characteristic of IPT at 80 kHz.
 $(D = 0.5)$.




(c) The iso-power lines of IPT through duty cycle and frequency.

Experimental Results- WPT System Validation




	Design values	Measured values
Transmitter inductance	$204\mu\text{H}$	$205\mu\text{H}$
Receiver inductance	$52\mu\text{H}$	$51\mu\text{H}$
Mutual inductance	$41\mu\text{H}$	$40\mu\text{H}$

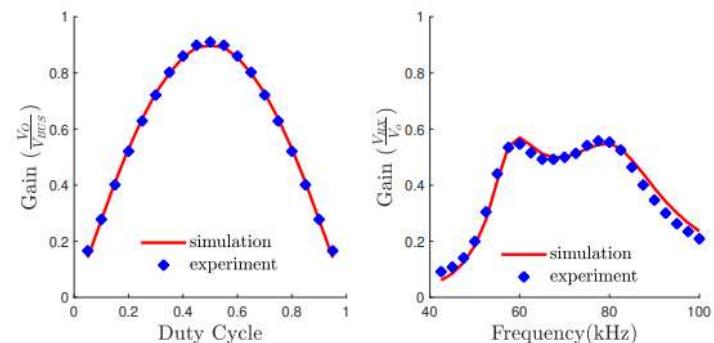

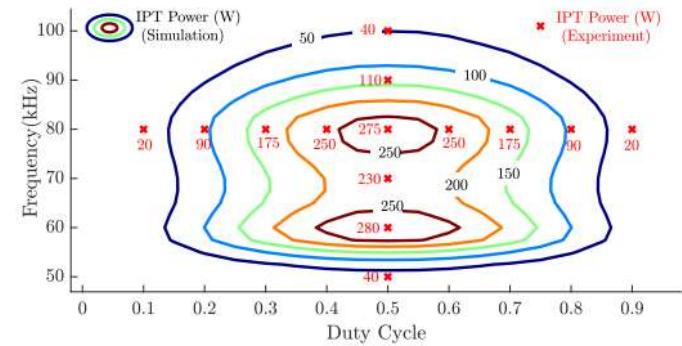(a) Duty cycle-gain characteristic of WPT at 80 kHz. (b) Frequency-gain characteristic of WPT ($D = 0.5$).



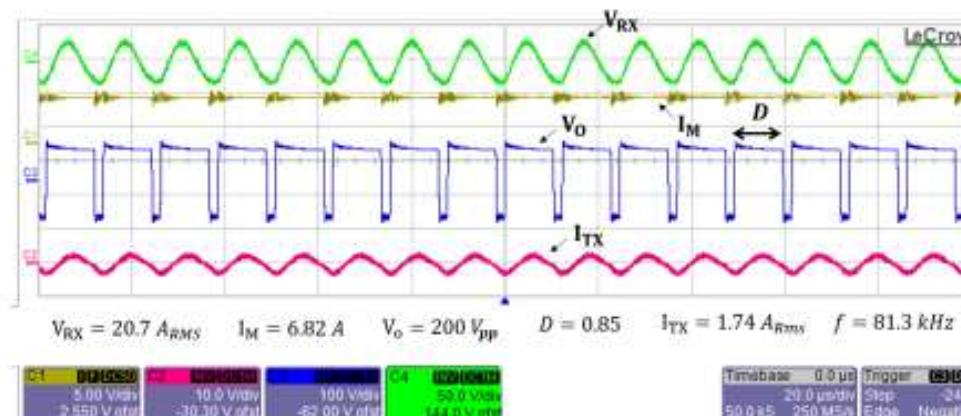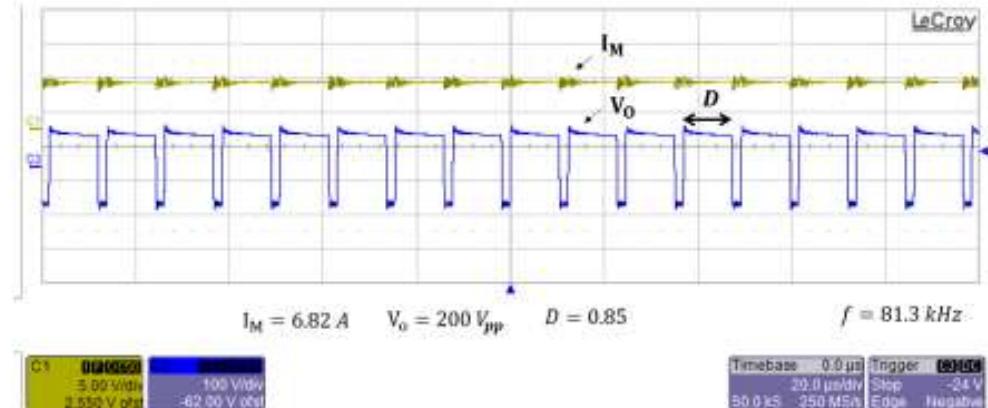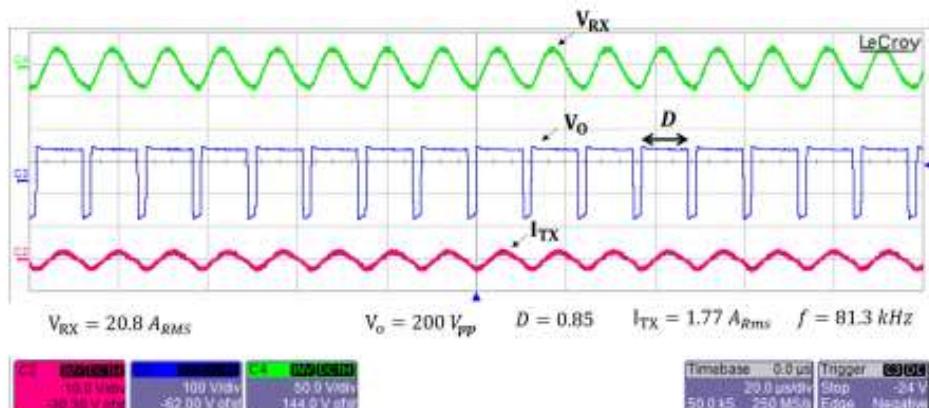
Experimental Results - Concurrent Operation



Experimental Results – Loss and Efficiency

Operation	Input Power (W)	Drive Losses (W)	Converter Output Power (W)	Efficiency (%)
Only IPT	67.6	7.3	60.3	89.2
Only Motor	457.1	12.8	444.3	97.2
IPT and Motor	522.2	14.1	508.1	97.3

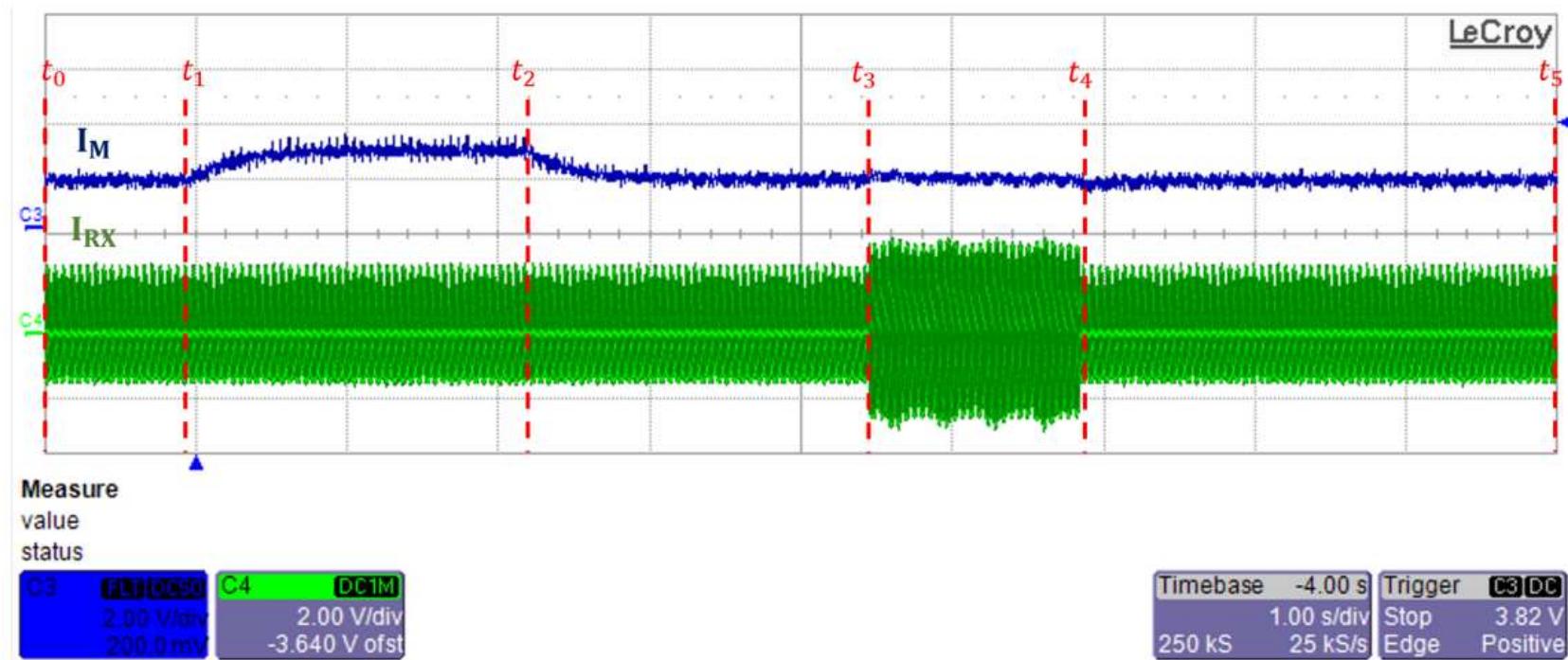Experimental Results – Transient Load Changes





Experimental Results – Different Operating Conditions

	Cases						
	A	B	C	D	E	F	G
Frequency (kHz)	95	90	90	95	90	90	97.5
Duty Cycle	0.6	0.75	0.75	0.6	0.6	0.6	0.5
Load Torque (N.m)	0.24	0.27	0.37	0.21	0.21	0.17	-
Motor Power (W)	125	179	244	109	110	89	-
IPT Power (W)	50	51	51	50	90	90	52.7



Outline

1. Aim of Study
2. Inductive Power Transfer System Basics
3. Theory Of Operations
4. Implementation for DC Motor
5. **Implementation for AC Motor**
6. Implementation for field excitation
7. Conclusion

System Overview and Experimental Setup

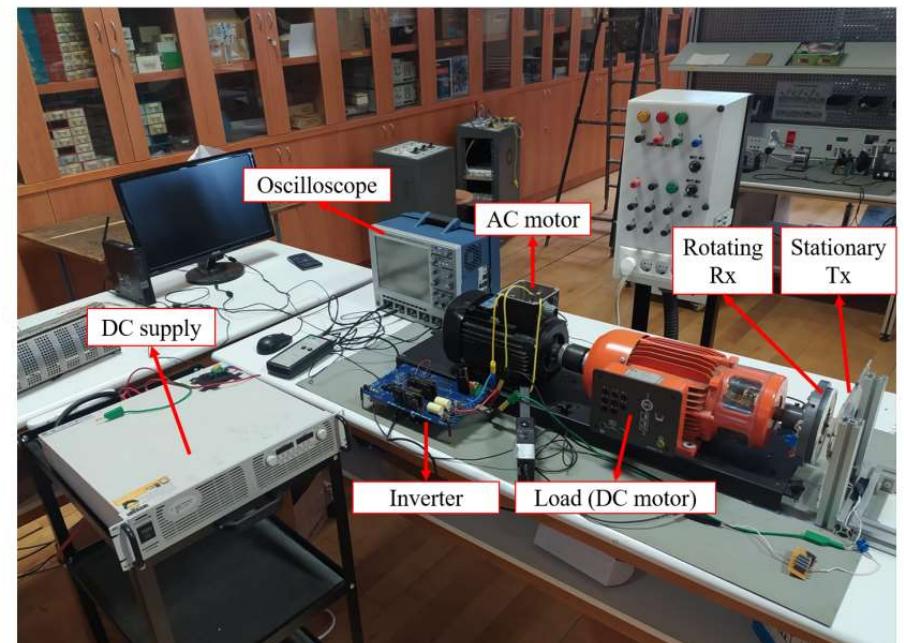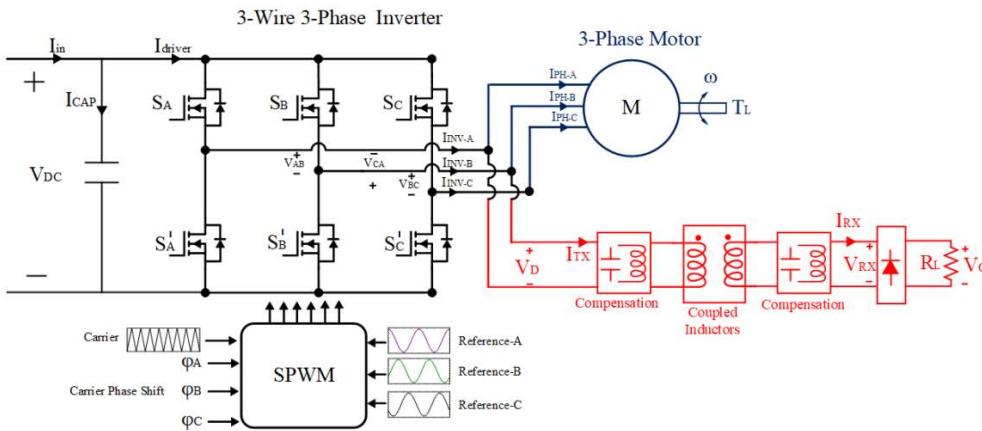


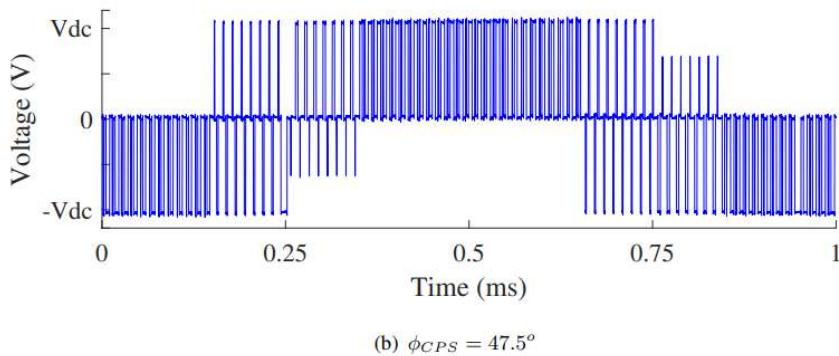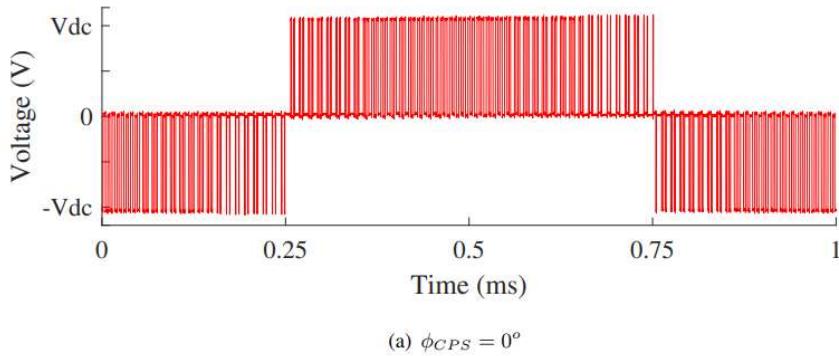Experimental Results- Carrier Phase Shift Validation



		$A_{INV} (\hat{V}_{ll}/V_{dc})$			
		at f_o	at f_l	at f_s	at f_h
$m_a = 0.6$	Theoretical	0.519	0.113	0	0.113
	Experimental	0.532	0.110	0.011	0.115
	Error	2.5%	2.6%	-	1.7%
$m_a = 0.6$	Theoretical	0.519	0.130	0.405	0.077
	Experimental	0.537	0.127	0.414	0.084
	Error	3.4%	2.3%	2.2%	9.1%

Wireless Power Transfer System Design

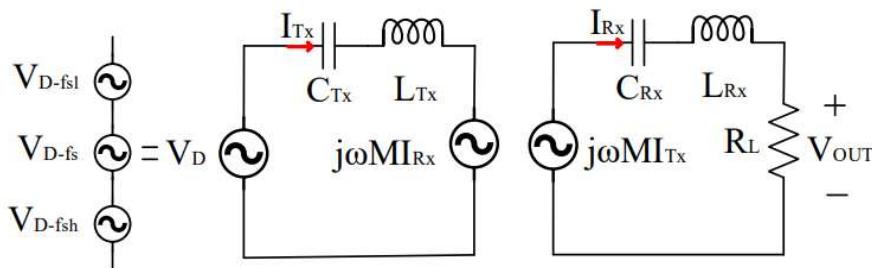

$$\omega_{rl} = \omega_r \sqrt{\frac{1}{1+k}}$$

$$\omega_{rh} = \omega_r \sqrt{\frac{1}{1-k}}$$

$$A_{WPT} = \left| \frac{V_{OUT}}{V_{IN}} \right|$$

$$\frac{dA_{WPT}}{dR_L} = 0$$

$$L_{Rx} = \frac{Q_{Rx} R_L}{\omega_{rh}} \longrightarrow A_{WPT(\omega_{rh})} = \left| \sqrt{\frac{L_{Rx}}{L_{Tx}}} \right| \longrightarrow L_{Tx} = \frac{L_{Rx}}{A_{WPT(\omega_{rh})}^2}$$

$$C_{Tx} = \frac{1}{\omega_r^2 L_{Tx}}$$


$$C_{Rx} = \frac{1}{\omega_r^2 L_{Rx}}$$



$$M = k \sqrt{L_{Tx} L_{Rx}}$$


Wireless Power Transfer System Design

Initial/Choosen Parameters	Values	Derived Parameters	Values
P_{rated}	24 W	A_{WPT}	0.5
V_D	$30 V_{RMS}$	R_L	9.3Ω
V_{out}	$15 V_{RMS}$	L_{Rx}	$50 \mu H$
f_{rh}	85 kHz	L_{Tx}	$200 \mu H$
Q_{Rx}	2.9	M	$40 \mu H$
k	0.4	f_r	65.85 kHz
		C_{Tx}	29.2 nF
		C_{Rx}	117 nF

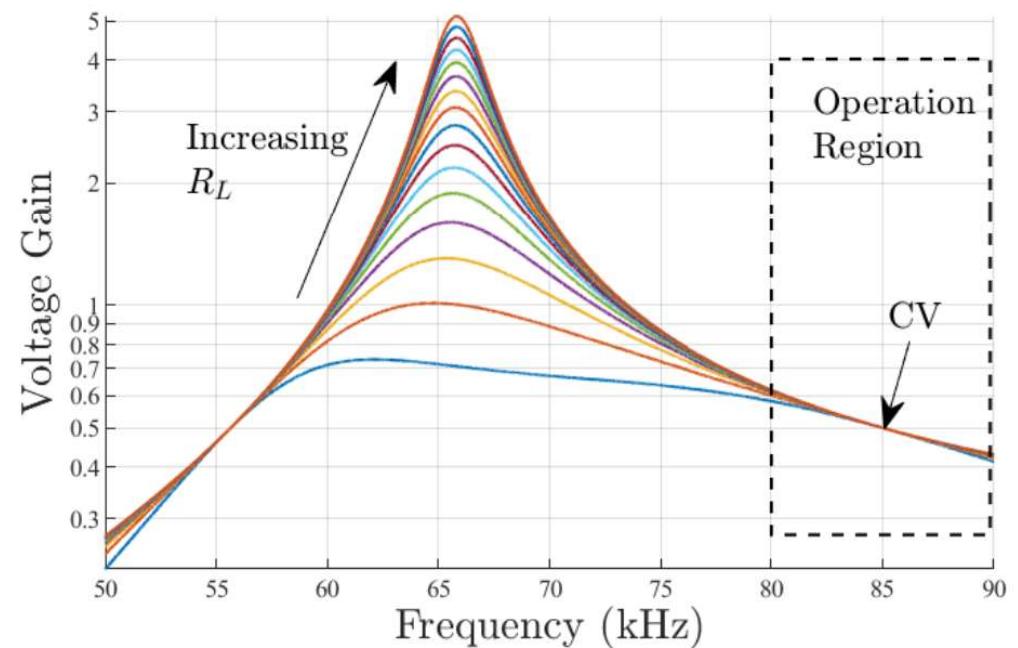


Experimental Results- WPT System Validation


	Design values	Measured values
Transmitter inductance	$204\mu\text{H}$	$205\mu\text{H}$
Receiver inductance	$52\mu\text{H}$	$51\mu\text{H}$
Mutual inductance	$41\mu\text{H}$	$40\mu\text{H}$

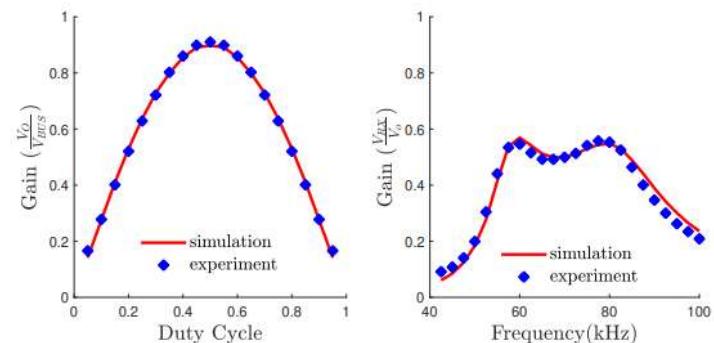

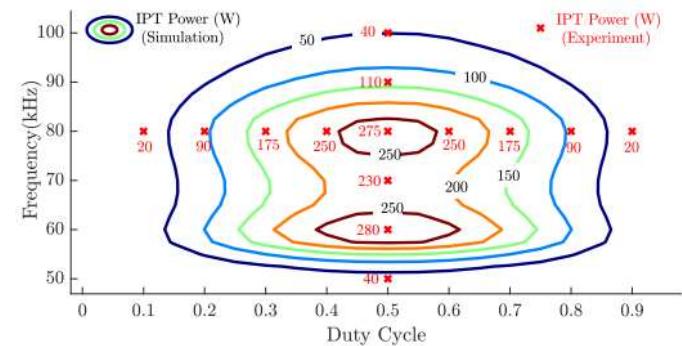
(a) Duty cycle-gain characteristic of WPT at 80 kHz. (b) Frequency-gain characteristic of WPT ($D = 0.5$).



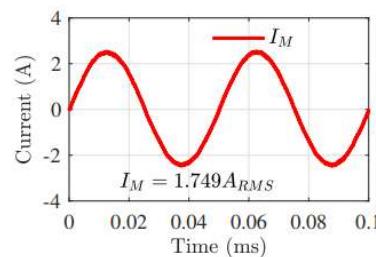
Experimental Results - Concurrent Operation



(a) Only motor operation.

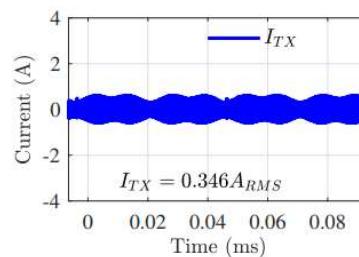


(b) Only WPT operation.

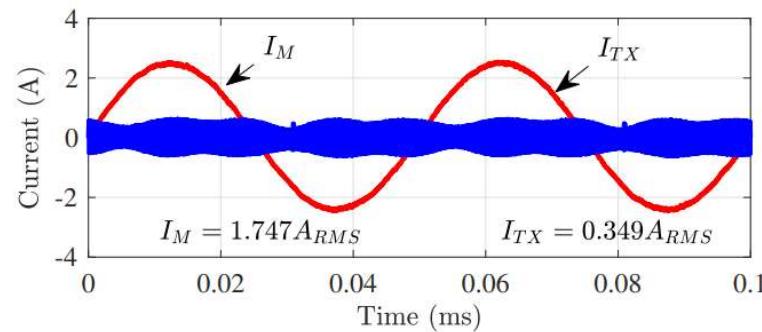


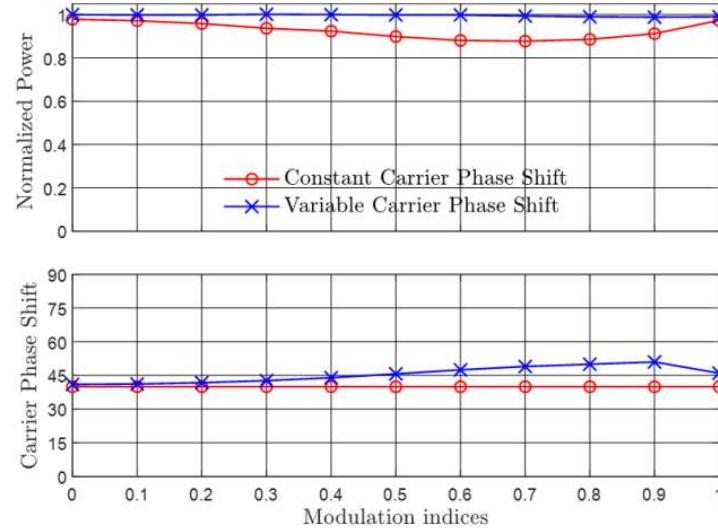
(c) Concurrent operation of motor and WPT.

Experimental Results – Variable Carrier Phase Shift



Modulation index (m_a)	0	0.1	0.2	0.3	0.4	0.5	0.6	0.7	0.8	0.9	1
Phase shift (θ_{an}) (Theoretical)	41	41	41.2	42.4	44.1	46.0	48.2	50.3	51.9	52.0	46
Phase shift (θ_{exp}) (Experimental)	41	41.2	41.8	42.7	44	45.7	47.5	49	50	51	46

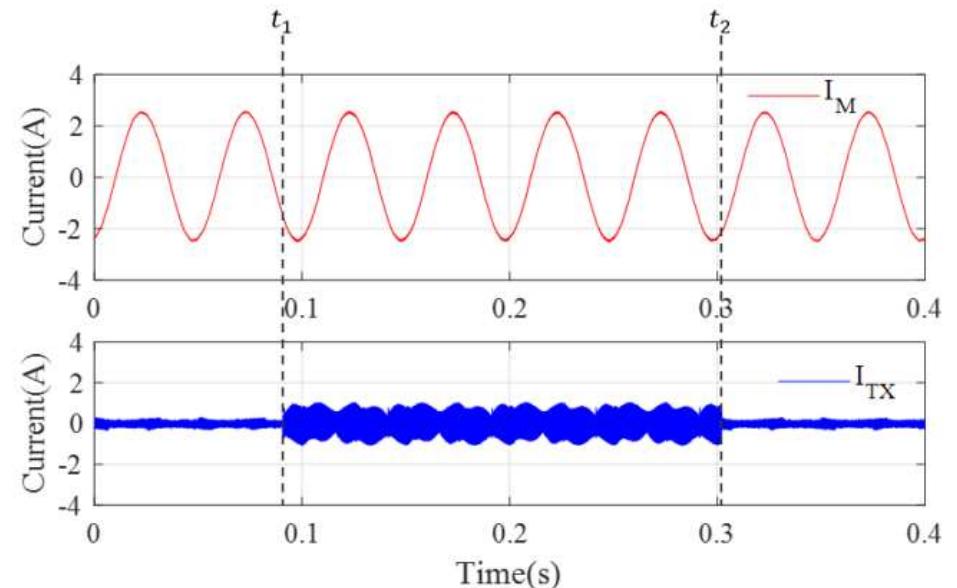
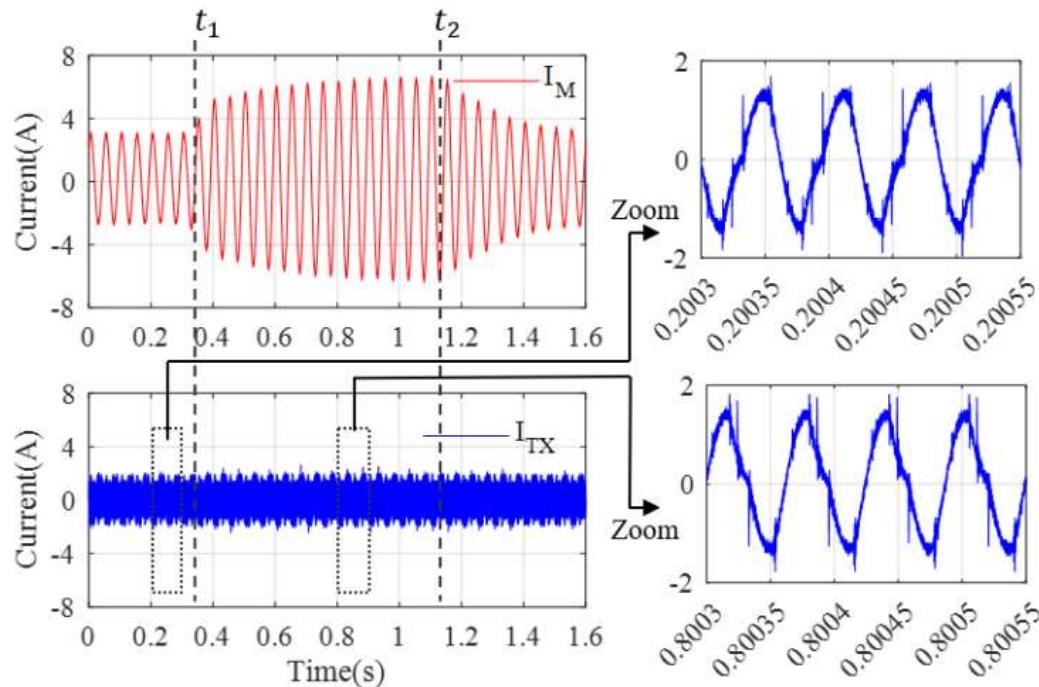
Experimental Results – Transient Load Changes



Outline


1. Aim of Study
2. Inductive Power Transfer System Basics
3. Theory Of Operations
4. Implementation for DC Motor
5. Implementation for AC Motor
6. **Implementation for field excitation**
7. Conclusion

System Overview and Experimental Setup

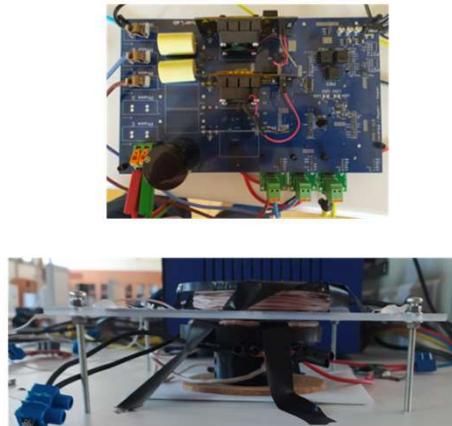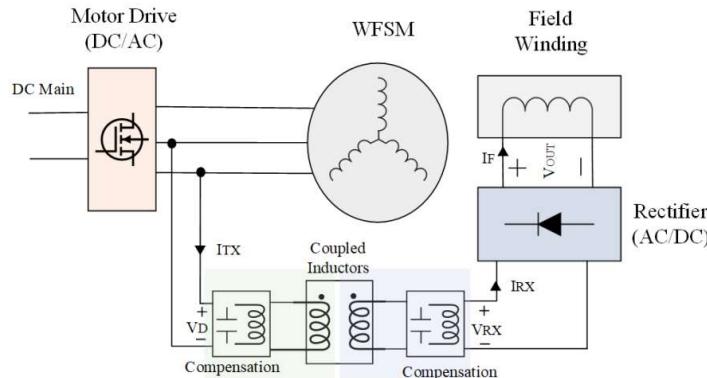


Ratings

DC-link voltage (V_{DC})	100 V
Modulation index (m_a)	0 – 1
Field current (I_f)	5 A
Field resistance (R_L)	1.2Ω
The WPT system's rated output voltage (V_{OUT})	6 V
The WPT system's input voltage (V_D)	40 V _{RMS}
The WPT system's rated power ($P_{WPT-CSR}$)	30 W
Switching frequency (f_s)	60kHz

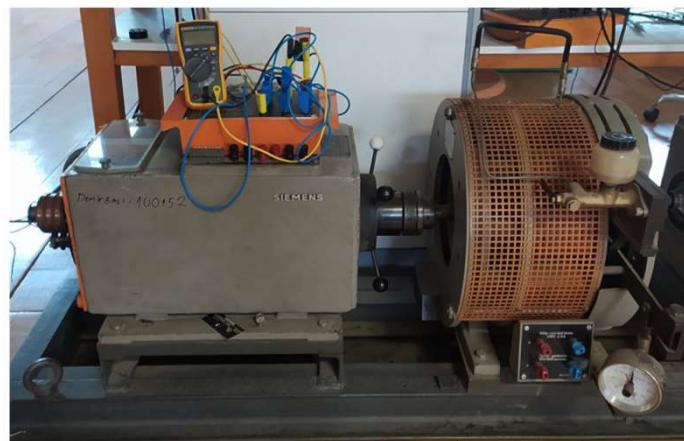

Wireless Power Transfer System Design

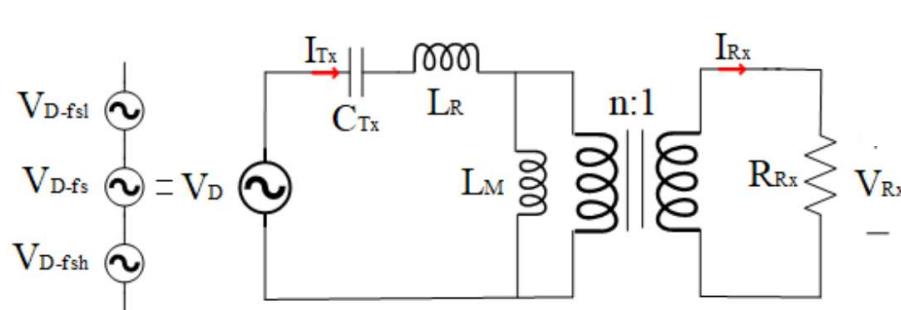



$$L_{Rx} = Q \frac{R_{Rx}}{\omega_r} \rightarrow n = k \sqrt{\frac{L_{Tx}}{L_{Rx}}} \rightarrow L_{Tx} = \frac{n^2}{k^2} L_{Rx}$$

$$n = \frac{V_D}{V_{Rx}}$$



$$C_{Tx} = \frac{1}{\sqrt{\omega_r^2 L_R}}$$

Initial/Chosen Parameters	Values	Derived Parameters	Values	Experimental Values
P _{rated}	30 W	V _{Rx}	7.56	-
V _D	40 V _{RMS}	R _{Rx}	0.97 Ω	-
V _{OUT}	6 V _{DC}	n	5.95	-
f _{rh}	60 kHz	L _{Tx}	1510 μH	-
Q _{Rx}	2.5	L _{Rx}	6.5 μH	-
k	0.7	M	42 μH	-
R _L	1.2 Ω	C _{Tx}	6.7 nF	-

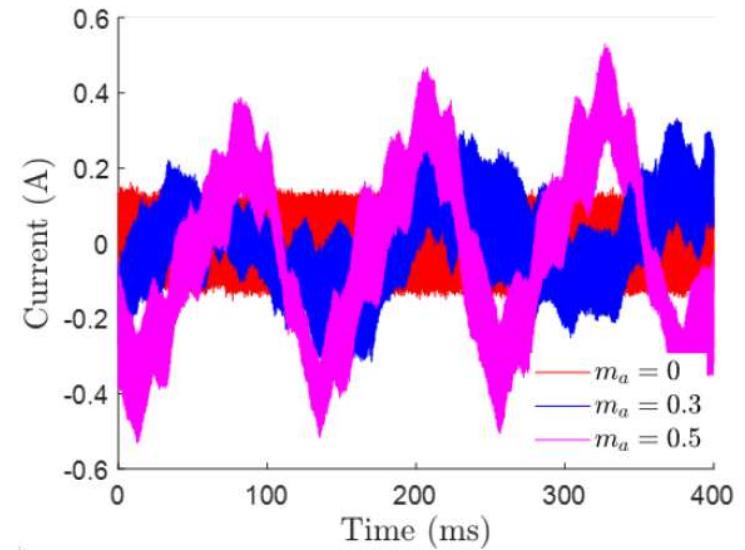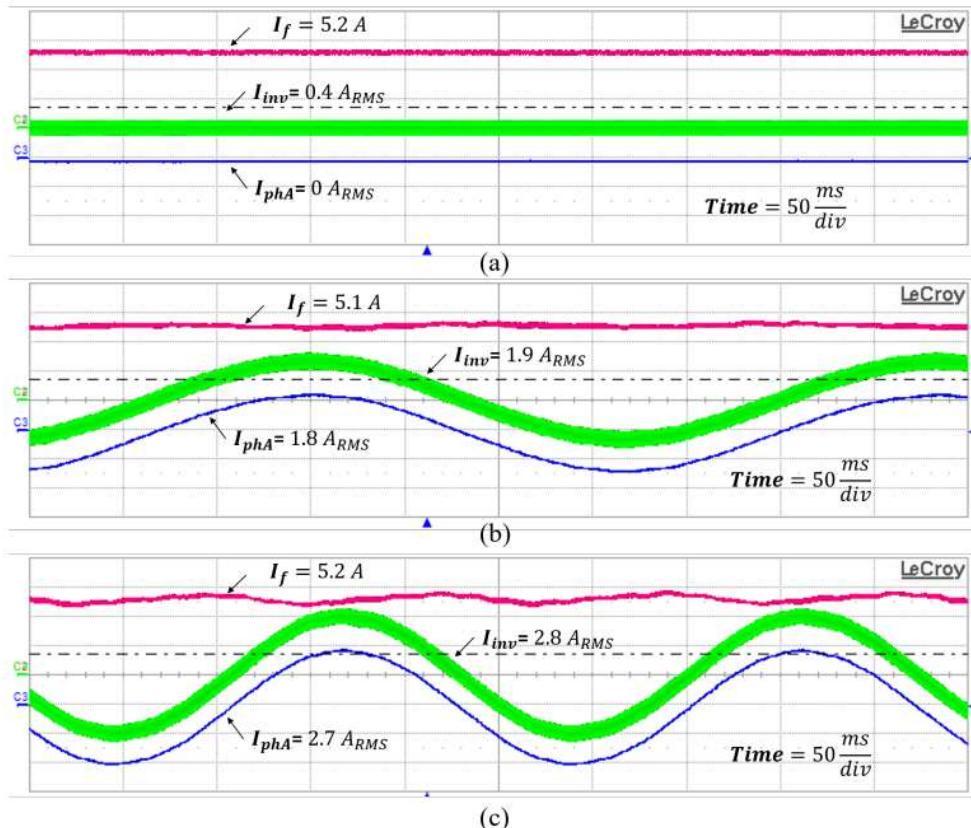Experimental Validation- Carrier Phase Shift



New real-time algorithm

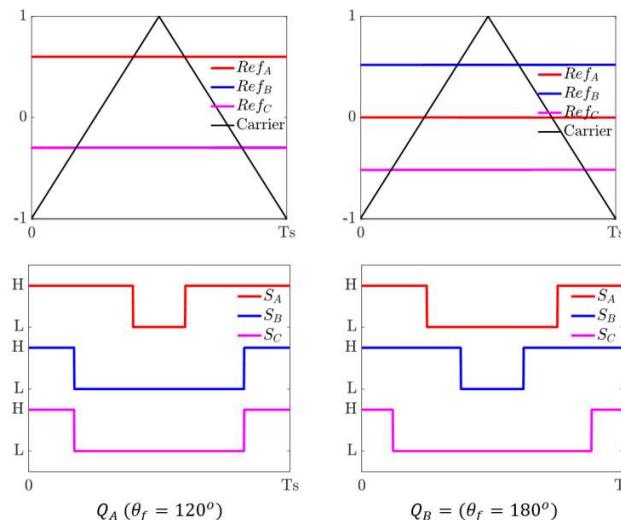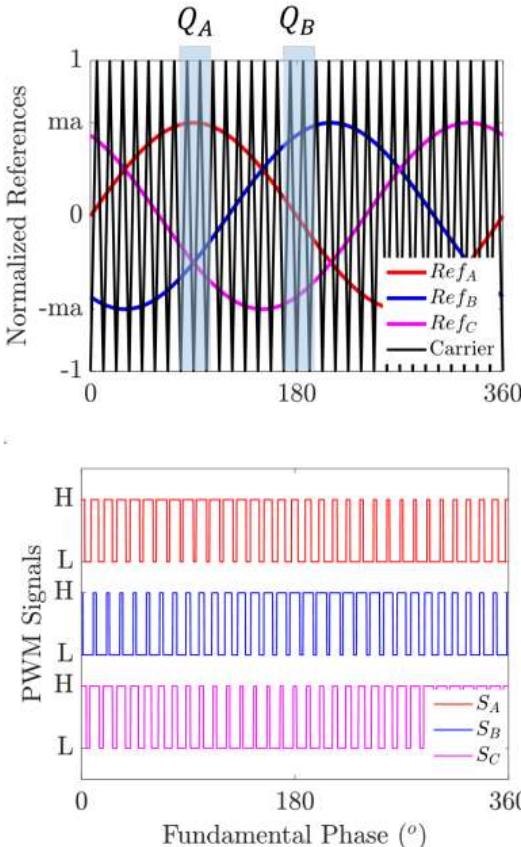

$$D_A = \frac{1 + m_a \sin(\theta_f)}{2}$$

$$D_B = \frac{1 + m_a \sin(\theta_f - 120)}{2}$$

$$D_C = \frac{1 + m_a \sin(\theta_f + 120)}{2}$$

$$S(t) = D + \sum_{k=1}^{\infty} \frac{2}{k\pi} \sin(k\pi D) \cos(2\pi kf_s t + k\phi_C)$$

New real-time algorithm

$$S_A(t)^{f_s} = \frac{2}{\pi} \sin(\pi D_A) \cos(2\pi f_s t + \phi_{C-A})$$

$$S_B(t)^{f_s} = \frac{2}{\pi} \sin(\pi D_B) \cos(2\pi f_s t + \phi_{C-B})$$

$$S_C(t)^{f_s} = \frac{2}{\pi} \sin(\pi D_C) \cos(2\pi f_s t + \phi_{C-C})$$

$$S_{AB}(t)^{f_s} = S_A(t)^{f_s} - S_B(t)^{f_s}$$

$$= \frac{2}{\pi} \sin(\pi D_A) \cos(2\pi f_s t + \phi_{C-A})$$


$$- \frac{2}{\pi} \sin(\pi D_B) \cos(2\pi f_s t + \phi_{C-B})$$

$$\hat{S}_{AB_{f_s}} = \frac{2}{\pi} \sqrt{\sin(\pi D_A)^2 + \sin(\pi D_B)^2 - 2(\sin(\pi D_A)(\sin(\pi D_B)\cos(\phi_A - \phi_B))}$$

New real-time algorithm

$$\frac{2}{\pi} |\sin(\pi D_A) - \sin(\pi D_B)| < \hat{S}_{AB_{fs}}$$

$$< \frac{2}{\pi} |\sin(\pi D_A) + \sin(\pi D_B)|$$


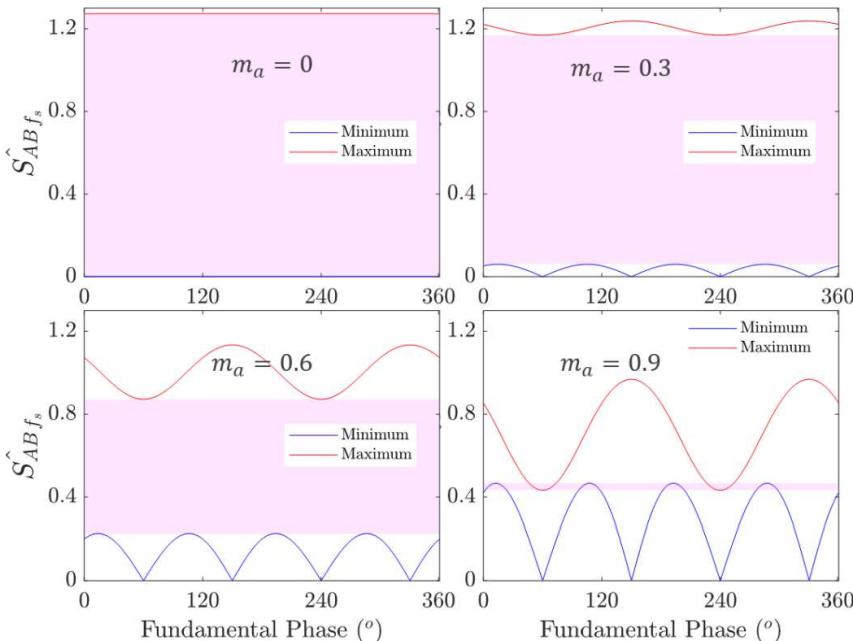


$$\hat{S}_{AB_{fs}} = 0.43 !$$

$$\phi_{C-A} - \phi_{C-B} =$$

$$\arccos \left[\frac{\sin(\pi D_A)^2 + \sin(\pi D_B)^2 - (\frac{\pi}{2} \hat{S}_{AB_{fs}})^2}{2 \sin(\pi D_A) \sin(\pi D_B)} \right]$$

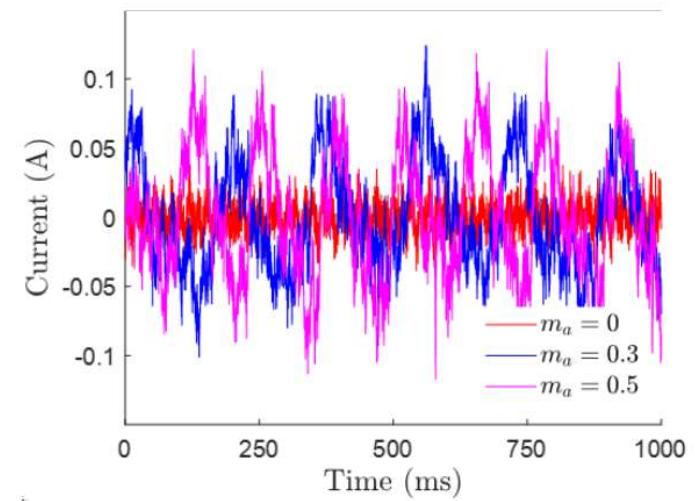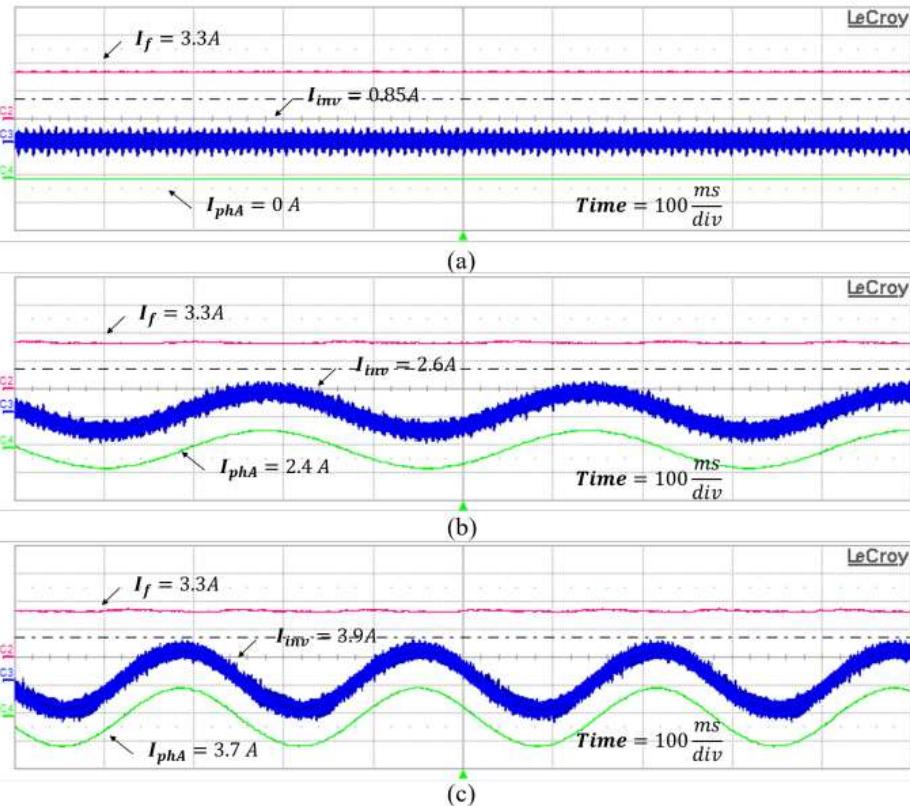Experimental Validation- Carrier Phase Shift



Outline

1. Aim of Study
2. Inductive Power Transfer System Basics
3. Theory Of Operations
4. Implementation for DC Motor
5. Implementation for AC Motor
6. Implementation for field excitation
7. Conclusion

Performance Comparisons

Performance Metrics	Retrieved from [78]				The Proposed System
	Slip Rings	Brushless Exciters	Inductive Couplers	Capacitive Coupler	
Maintanance	Yes	No	No	No	No
Speed Sensitivity	Yes	Possible	No	Possible	No
Scalability	Diffucult	Easy	Possible	Possible	Difficult
Power Output	DC	DC	AC	AC	AC
Power Source	External DC	Shaft	External AC	External AC	Internal AC
Size	Small	Large	Medium	Medium	Medium

Performance Comparisons

	[79]	[78]	[20]	[80]	[21]	[22]	[23]	[24]	[69]	[25]	[81]	This work
Frequency (kHz)	5	>650	250	100	848	50	1000	50	82.6	50	585	65
Power (W)	300	340	300	1000	100	231	10	500	3000	1000	10	50
Topology	RT	CPT	IPT	RT	CPT	IPT						
Airgap (mm)	0.5	0.081	18	< 2	0.125	70	2	-	10	0.6	10	10
Diameter (mm)	171	76.2	120	-	160	95	46	100	100	-	50	110
Efficiency (%)	85	85	92-95	90	94	>82	80	>80	92	>95	81	89
Additional converter	Yes	Yes	Yes	Yes	Yes	Yes	Yes	Yes	Yes	Yes	Yes	No

	Transfer Channels	Converter Numbers (Tx)	Offline Algoirthm	Operating Frequency
[40]	1	1	Not Required	$\geq f_s$
[41]	2	2	Not Required	f_s
[42]	2	1	Required	$\leq f_s$
[44]	4	1	Not Required	$< f_s$
This work	2	1	Not Required	$= f_s$

Contributions

1. A cost-efficient and simple-to-implement contactless slip ring is introduced.
2. For DC motor drives, a multi-frequency approach is presented to implement with a conventional DC motor PWM technique.
3. An independent control scheme, which comprises frequency and duty cycle control, is proposed for concurrent DC and high-frequency AC power transfer to the motor and rotating loads, respectively.
4. For AC motor drives, a multi-frequency approach is presented to implement with a conventional AC motor PWM technique.
5. An independent control scheme, which comprises carrier phase shift and modulation index control, is proposed for concurrent low-frequency AC and high frequency AC power transfer to the motor and slip rings, respectively.
6. For field excitation of the synchronous motors, a brushless slip ring is proposed to directly integrate into the motor drive with light-weight on the rotating side.
7. A novel real-time carrier-phase-shift calculation algorithm embedded in the motor control loop is developed to avoid low-frequency ripples stemming from the sideband harmonics.

Future Works

1. Improved coil design.
2. Capacitorless (Light-weight rotating side) WPT topologies.
3. Multi-phase WPT system.
4. Closed loop control, and current estimation algorithms.

Thanks!
