

# Concurrent Operation of Wireless and Wired Power Transfer System with a Single Converter/Inverter


---

Enes Ayaz  
20/10/2022


---



# Wireless Power Transfer

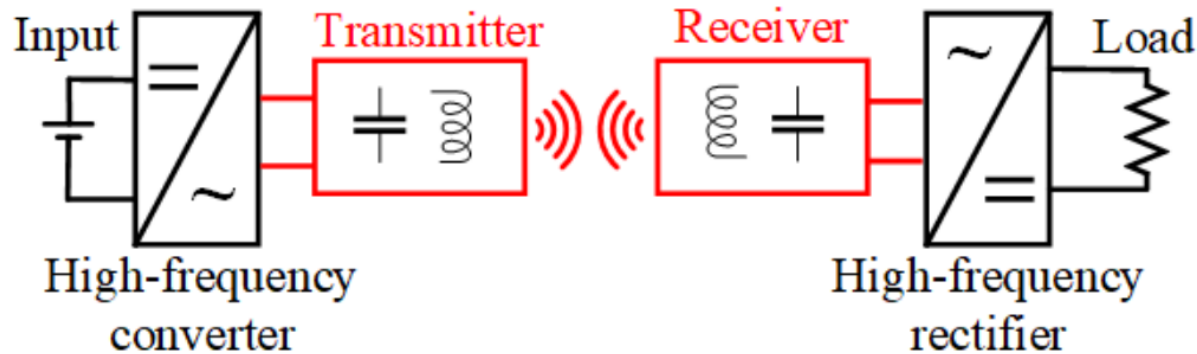

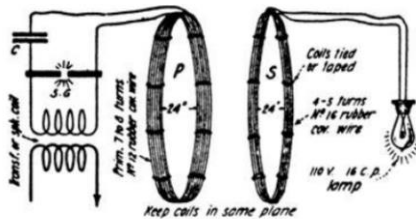
1. DC/AC Converter
2. Compensation Circuits
3. Transmitter/Receiver Coils
4. AC/DC Rectifiers



Tesla's WPT System

	Inductive Power Transfer	Capacitive Power Transfer
Transfer Type	Varying MF	Varying EF
Power Ratings	High	Low
Frequencies	Low	High
Efficiency	High	High
Distance	Moderate	Low

# Inductive Power Transfer System

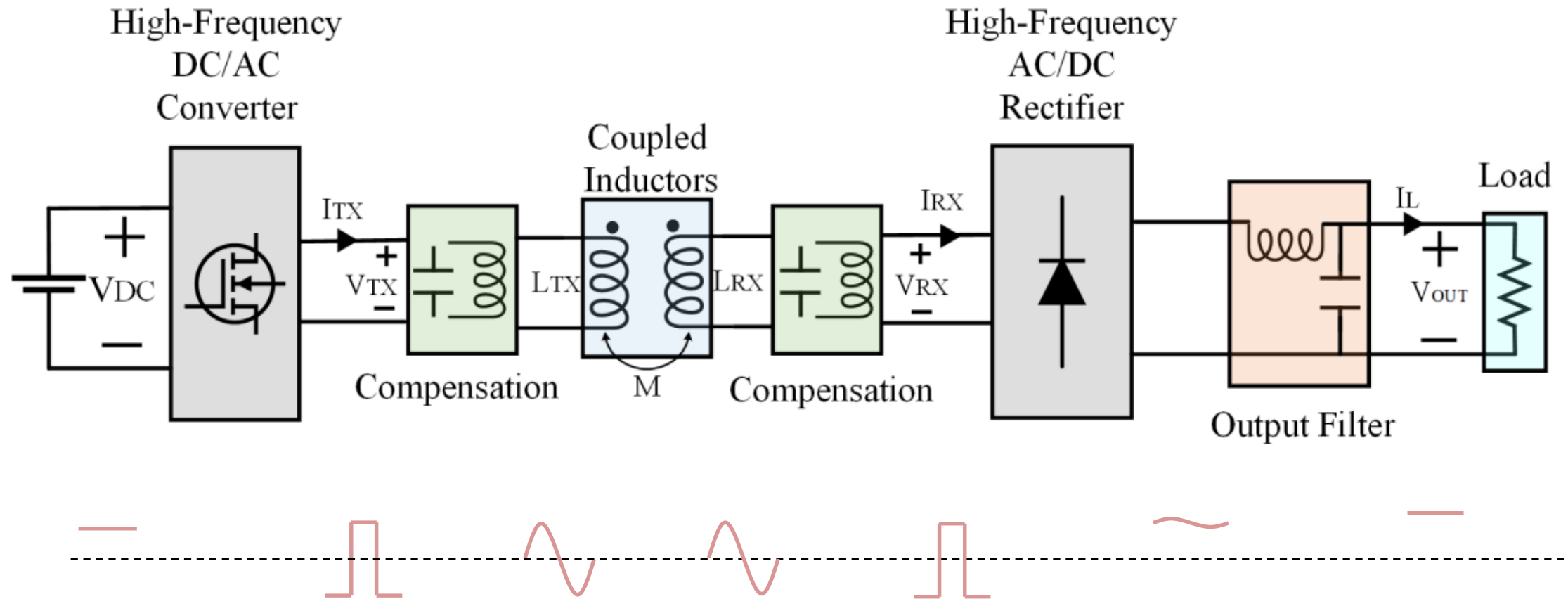

## Selective Power Transfer

1. Selective Omnidirectional Magnetic Resonant Coupling Wireless Power Transfer With Multiple-Receiver System(2018)
2. [Design and Analysis of Wireless Switched Reluctance Motor Drives\(2019\)](#)
3. Frequency Splitting-Based Wireless Power Transfer and Simultaneous Propulsion Generation to Multiple Micro-Robots(2018)
4. [Comparative Analysis of Frequency-Selective Wireless Power Transfer for Multiple-Rx Systems\(2020\)](#)
5. A Frequency-Selective EMI Reduction Method for Tightly Coupled Wireless Power Transfer Systems Using Resonant Frequency Control of a Shielding Coil in Smartphone Application(2020)
6. [Selective Wireless Power Transfer for Smart Power Distribution in a Miniature-Sized Multiple-Receiver System\(2016\)](#)
7. A Multifrequency Superposition Methodology to Achieve High Efficiency and Targeted Power Distribution for a Multiload MCRWPT System(2018)
8. [Cross Interference Minimization and Simultaneous Wireless Power Transfer to Multiple Frequency Loads Using Frequency Bifurcation Approach](#)

## Slip-Ring Applications

1. A Primary-Side Control Method of Wireless Power Transfer for Motor Electric Excitation(2019)
2. [Wireless DC Motor Drives with Selectability and Controllability\(2017\)](#)
3. An Airborne Radar Power Supply With Contactless Transfer of Energy—Part I: Rotating Transformer (2007)
4. [Aerodynamic Fluid Bearings for Translational and Rotating Capacitors in Noncontact Capacitive Power Transfer Systems\(2014\)](#)
5. Synchronous Generator Brushless Field Excitation and Voltage Regulation via Capacitive Coupling Through Journal Bearings(2017)
6. [Operation of an Electrical Excited Synchronous Machine by Contactless Energy Transfer to the Rotor\(2018\)](#)
7. A Rotation-Lightweight Wireless Power Transfer System for Solar Wing Driving(2019)
8. [Wireless Power Transfer for Smart Industrial and Home Applications\(2019\)](#)
9. Use of the Rotating Rectifier Board as a Capacitive Power Coupler for Brushless Wound Field Synchronous Machines(2022)

## Single-Stage Power Transfers

1. A High-Efficiency GaN-Based Single-Stage 6.78 MHz Transmitter for Wireless Power Transfer Applications(2019)
2. [Cooperative Integration of RF Energy Harvesting and Dedicated WPT for Wireless Sensor Networks\(2019\)](#)
3. A Three-Phase Single-Stage AC–DC Wireless-Power-Transfer Converter With Power Factor Correction and Bus Voltage Control(2020)
4. [Individually Regulated Multiple-Output WPT System With a Single PWM and Single Transformer \(2020\)](#)

## Concurrent Power Transfer

1. [Multifrequency Inductive Power Transfer\(2014\)](#)
2. Wireless Power Transfer With Concurrent 200-kHz and 6.78-MHz Operation in a Single-Transmitter Device (2016)
3. [Gan-Based Dual-Mode Wireless Power Transfer Using Multifrequency Programmed Pulse Width Modulation \(2017\)](#)
4. A Multifrequency Superposition Methodology to Achieve High Efficiency and Targeted Power Distribution for a Multiload MCRWPT System (2018)
5. [Cross Interference Minimization and Simultaneous Wireless Power Transfer to Multiple Frequency Loads Using Frequency Bifurcation Approach\(2019\)](#)
6. A Gallium Nitride (GaN)-Based Single-Inductor Multiple-Output (SIMO) Inverter With Multi-Frequency AC Outputs (2019)
7. [Single-Inductor Multiple-Output \(SIMO\) Buck Hybrid Converter for Simultaneous Wireless and Wired Power Transfer\(2020\)](#)
8. Generalized methodology to generate, amplify and compensate multi-frequency power for a single-inverter-based MF-MR-S-WPT system (2020)
9. [Concurrent Wireless Power Transfer to Multiple Receivers With Additional Resonant Frequencies and Reduced Power Switches \(2020\)](#)
10. Multifrequency and Multiload MCR-WPT System Using Hybrid Modulation Waves SPWM Control Method (2021)
11. [Multi-Frequency Multi-Amplitude Superposition Modulation Method With Phase Shift Optimization for Single Inverter of Wireless Power Transfer System \(2021\)](#)
12. Design and Control of a Decoupled Multichannel Wireless Power Transfer System Based on Multilevel Inverters (2022)
13. [A Dual-Frequency Three-Dimensional WPT System with Directional Power Transfer Capability at Two Separately Regulated Outputs \(2022\)](#)

## Simultaneous Information/Power Transfer

1. Simultaneous Wireless Information and Power Transfer (SWIPT): Recent Advances and Future Challenges (2018)
2. [Integrated Resonant Structure for Simultaneous Wireless Power Transfer and Data Telemetry\(2012\)](#)
3. A Simultaneous Wireless Power and Data Transmission Method for Multi-Output WPT Systems: Analysis, Design, and Experimental Verification (2020)

## Concurrent Power Transfer


### Motivations:

1. To increase power
2. To reduce switching components
3. To increase DC-link utilization rate
4. To provide operation for more than one standards

### Topologies:

1. Multi-converter and multi-resonant
2. Single-converter and multi-resonant
3. Single-converter and multi-load


## Contactless Slip Rings

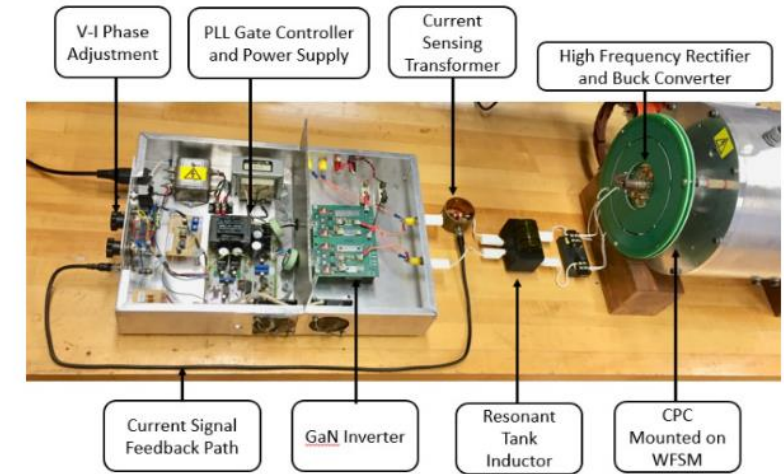

### Motivations:

1. To eliminate carbon brushes requiring periodic maintenance
2. To eliminate brushless exciters that are not suitable for variable speed drives
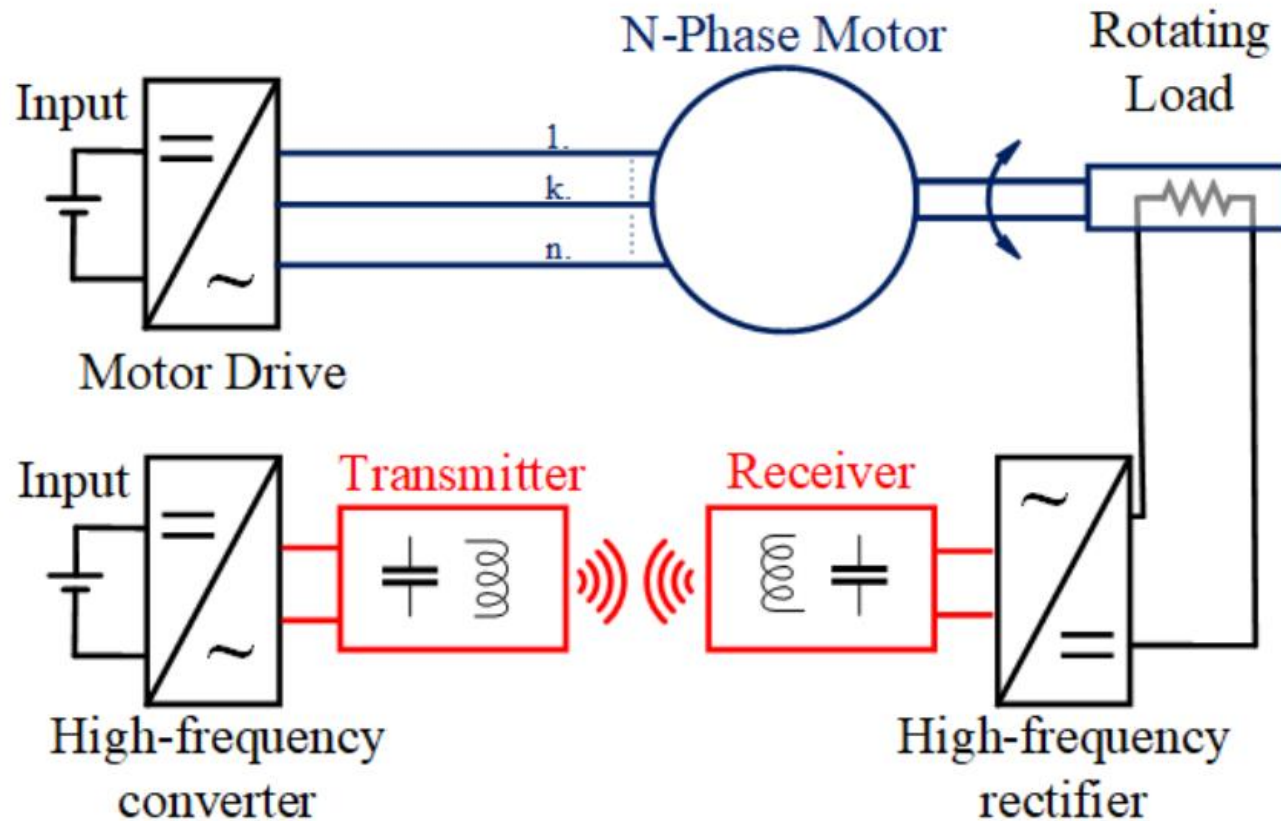
# Conventional Inductive Power Transfer Based Contactless Slip Ring



Two converters:

1. To drive the motor
2. To excite the Tx coil

Motor → attenuated in motor current

The motor drive → generating low and high frequencies


Motor → used to drive

The WPT converter → generating high frequency

The WPT system → behaves like band-pass filter


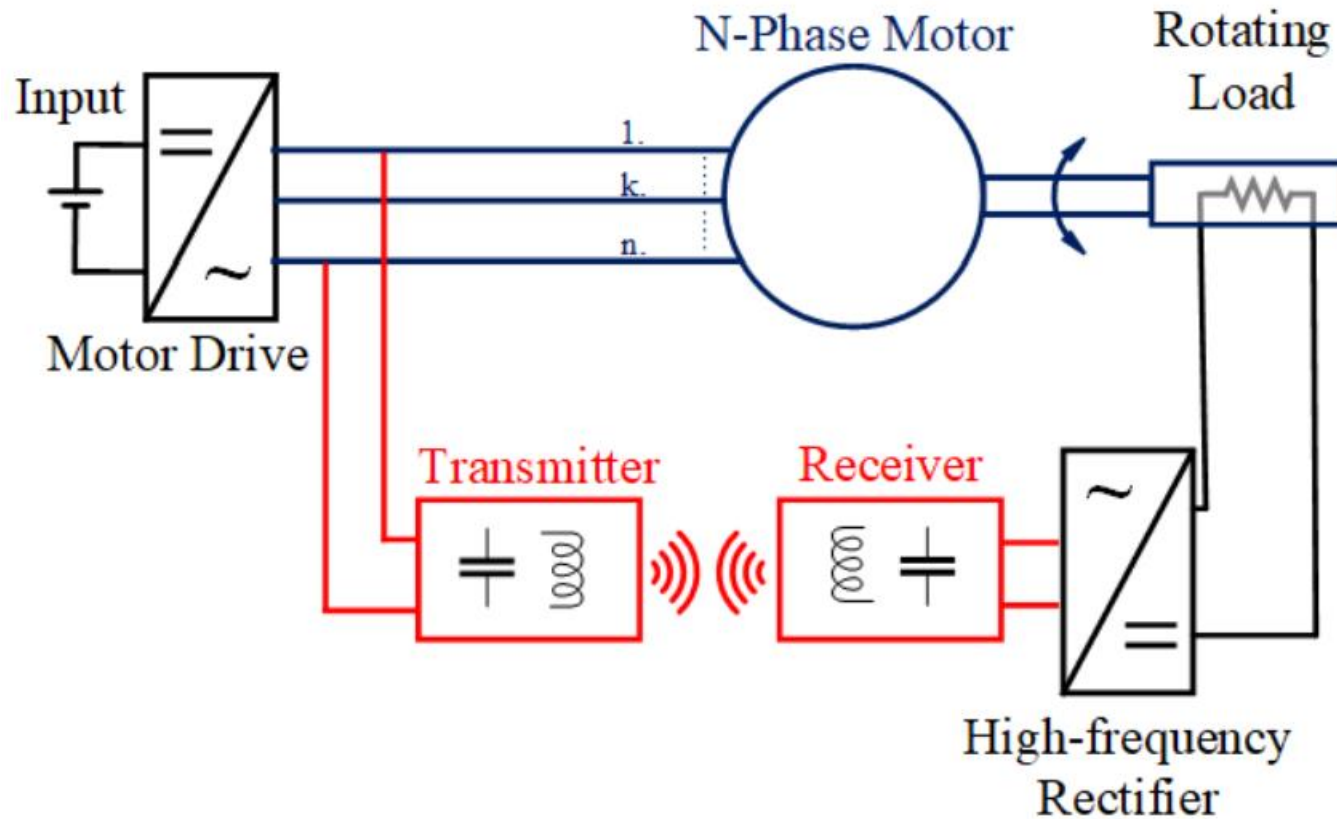
# Proposed Inductive Power Transfer Based Contactless Slip Ring




The motor drive → generating high frequency

combining

The WPT system → behaves like band-pass filter

No longer required

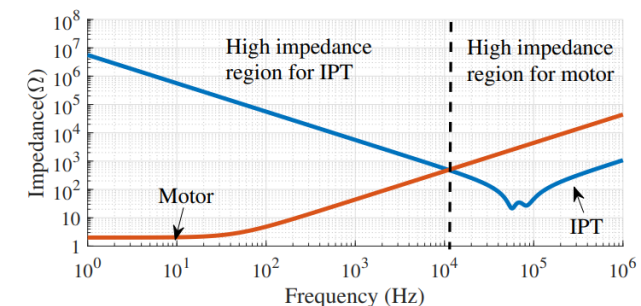~~The WPT converter → generating high frequency~~



# Challenge: Independent Control of Motor and Contactless Slip Ring Power



## Motor:

1. DC motor
2. AC motor

## Control:
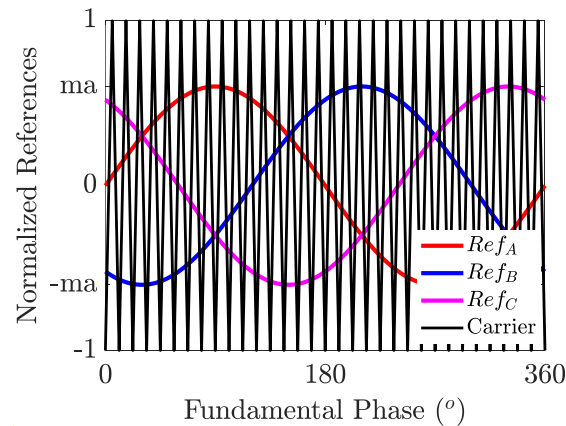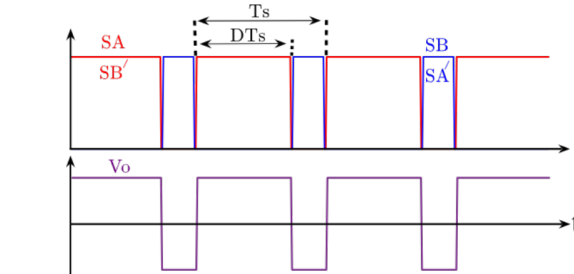
### Pulse Width Modulation

- Unipolar PWM
- Bipolar PWM
- SPWM
- SVPWM
- DPWM




## WPT:

### 1. Transmitter (Primary Side) Control

- Duty Cycle Control
- Phase Shift Control
- Switching Frequency Control
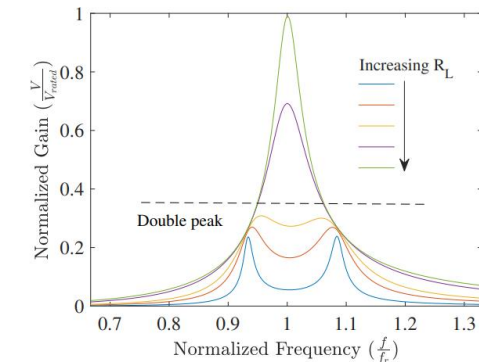
### 2. Receiver (Secondary Side) Control

- Additional active converter
- Active rectifier










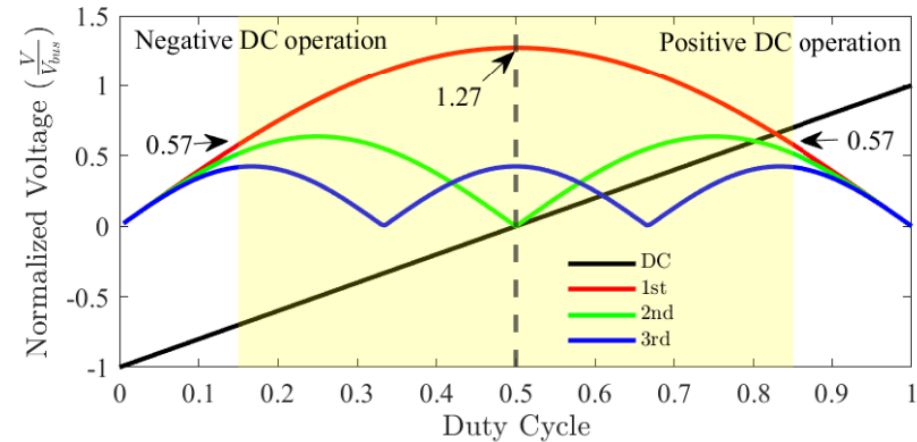
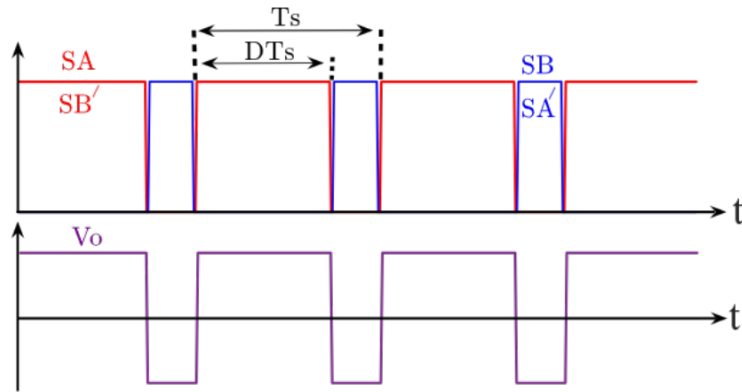
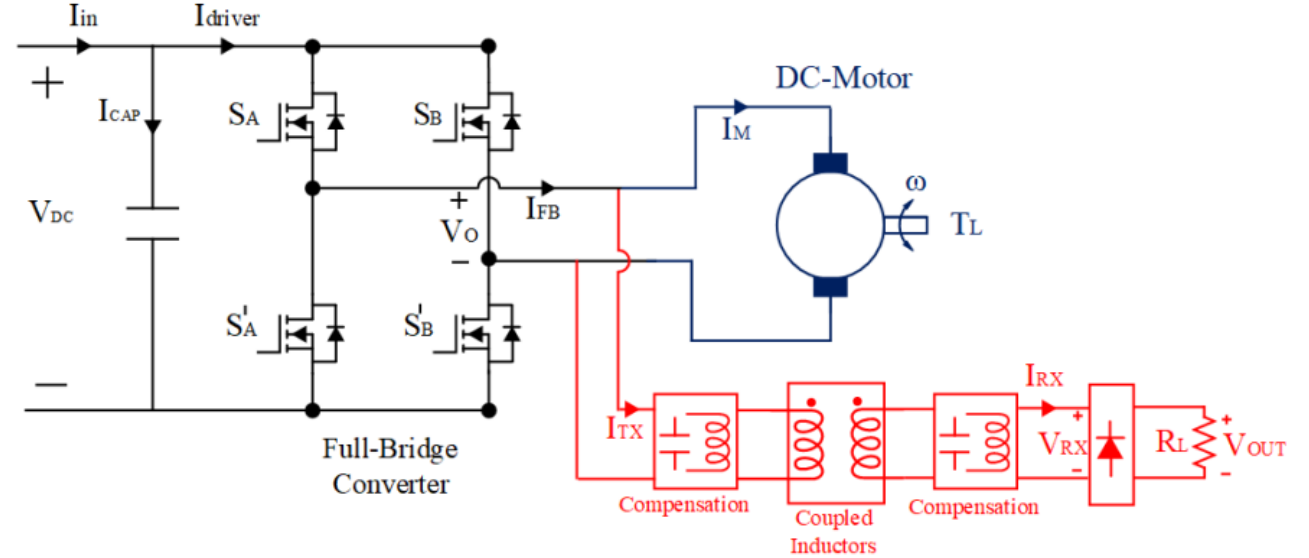
# DC Motor Drives

$$S_A = S'_B$$


$$S(t) = D + \sum_{k=1}^{\infty} \frac{2}{k\pi} \sin(k\pi D) \cos(2\pi k f_s t)$$



# Control Method

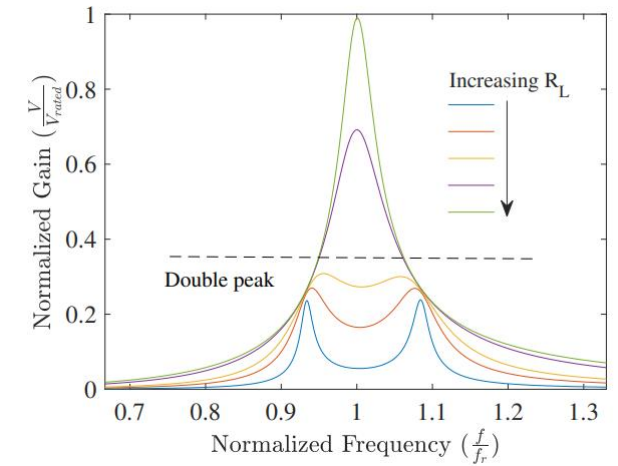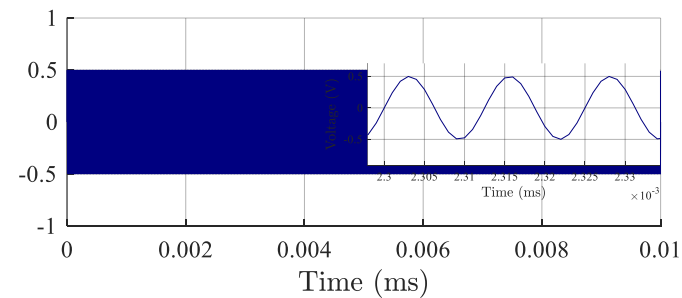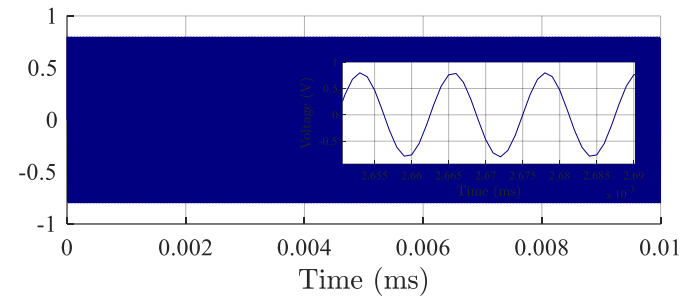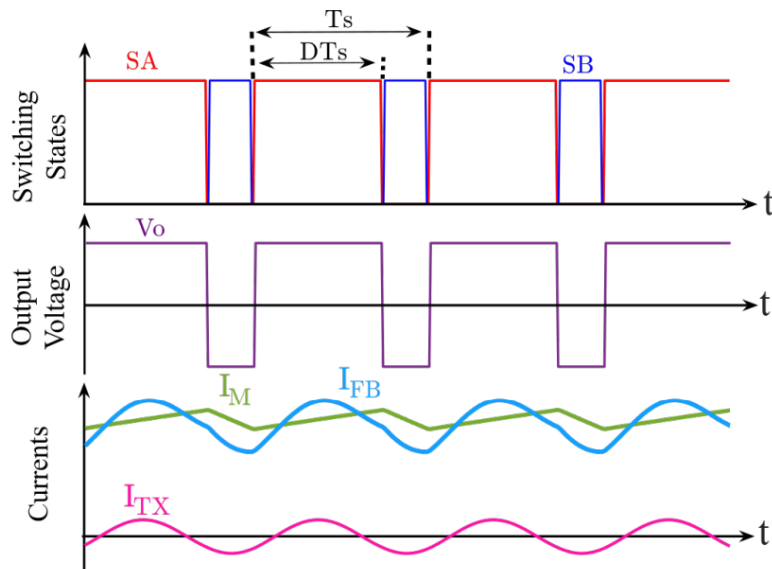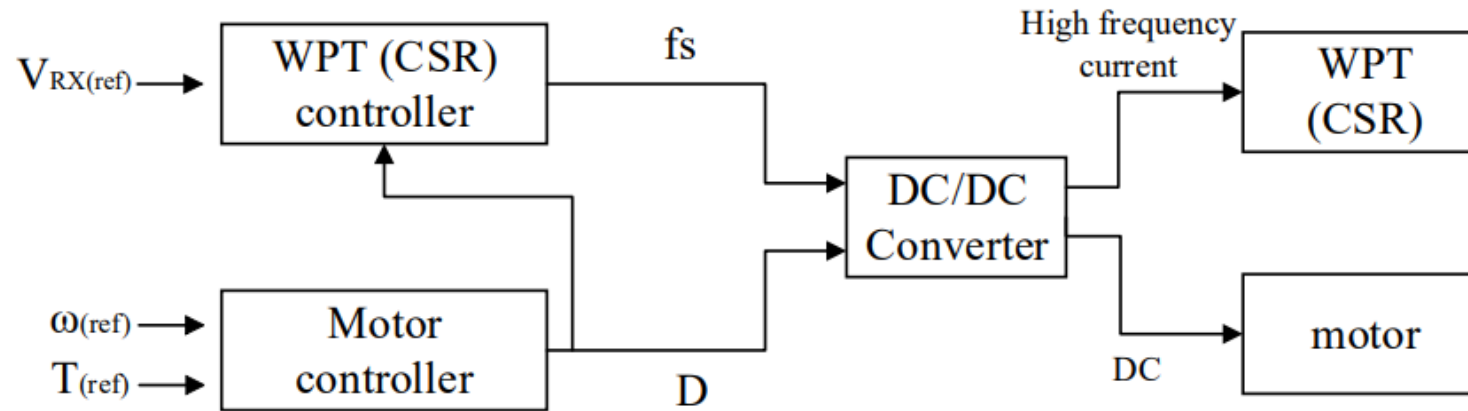





# Concurrent Operation

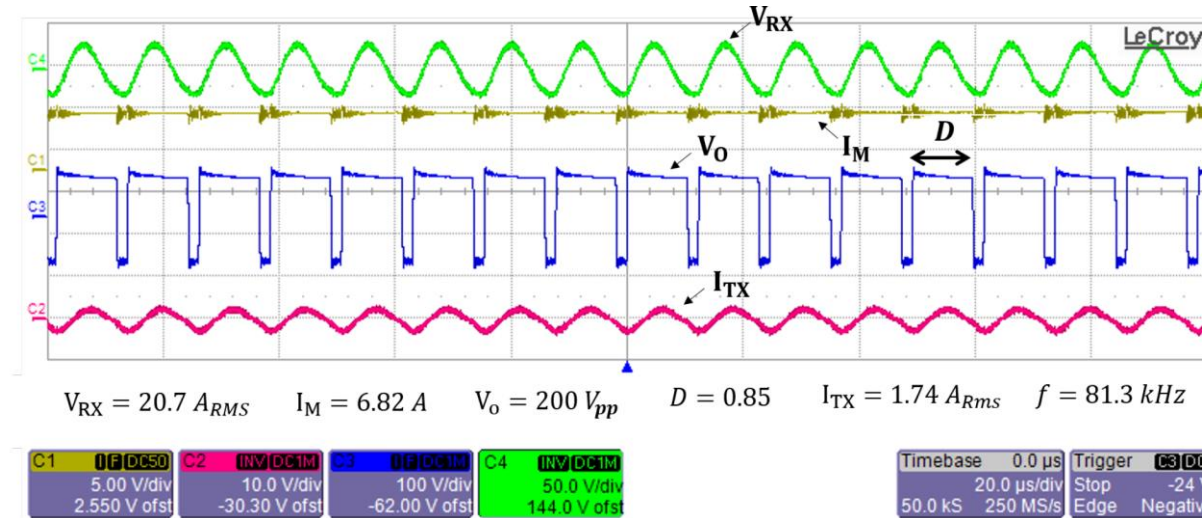

Cases


	A	B	C	D	E	F	G
Frequency (kHz)	95	90	90	95	90	90	97.5
Duty Cycle	0.6	0.75	0.75	0.6	0.6	0.6	0.5
Load Torque (N.m)	0.24	0.27	0.37	0.21	0.21	0.17	-
Motor Power (W)	125	179	244	109	110	89	-
IPT Power (W)	50	51	51	50	90	90	52.7

# AC Motor Drives

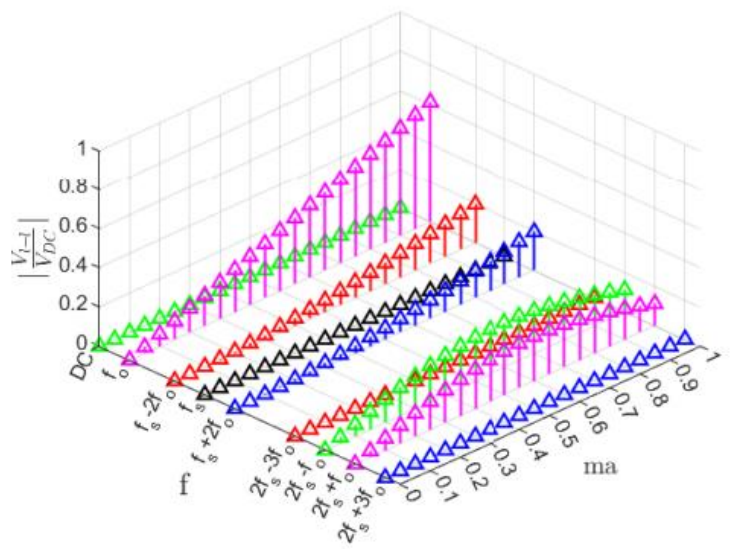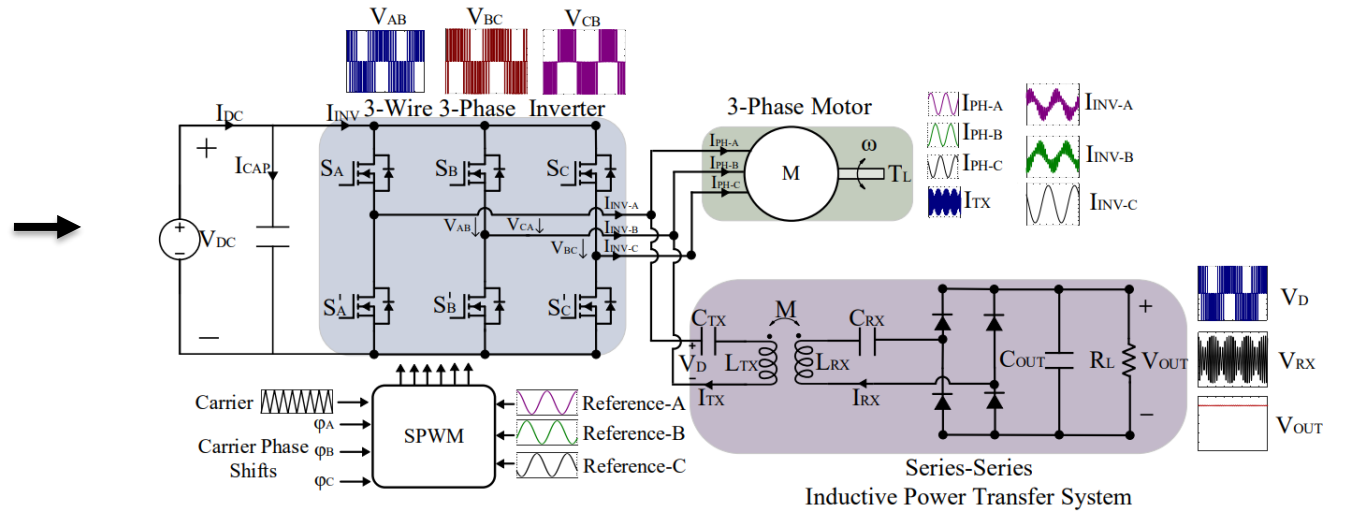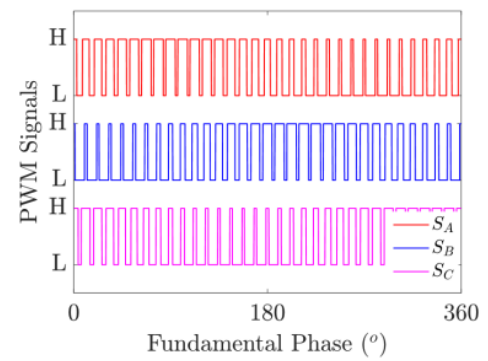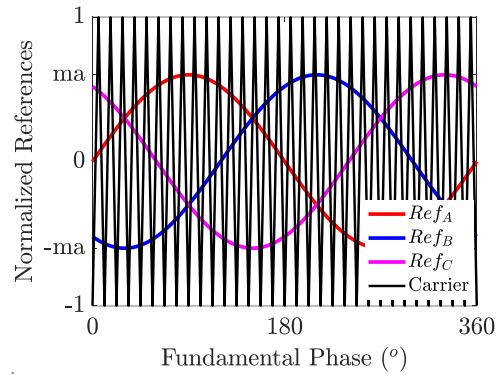


Frequency	Leg A	Leg B	Leg C	Sequence
$f_o$	$0^{\circ}$	$120^{\circ}$	$-120^{\circ}$	Positive
$f_s - 2f_o$	$0^{\circ}$	$120^{\circ}$	$-120^{\circ}$	Positive
$f_s$	$0^{\circ}$	$0^{\circ}$	$0^{\circ}$	Zero
$f_s + 2f_o$	$0^{\circ}$	$-120^{\circ}$	$120^{\circ}$	Negative

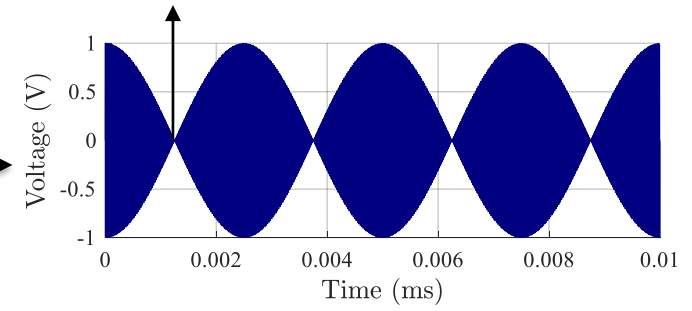There is no transferred power at some time points if only side band exist




no component at  $f_s$


# Carrier Phase Shift

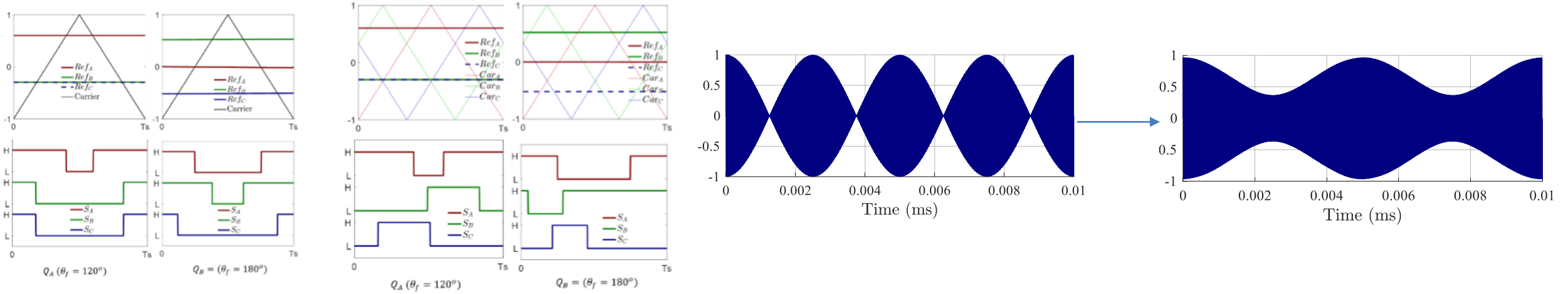




Frequency	Leg A	Leg B	Leg C
$f_o$	$0^\circ$	$120^\circ$	$-120^\circ$
$f_s - 2f_o$	$0^\circ + \phi_A$	$120^\circ + \phi_B$	$-120^\circ + \phi_C$
$f_s$	$0^\circ + \phi_A$	$0^\circ + \phi_B$	$0^\circ + \phi_C$
$f_s + 2f_o$	$0^\circ + \phi_A$	$-120^\circ + \phi_B$	$120^\circ + \phi_C$

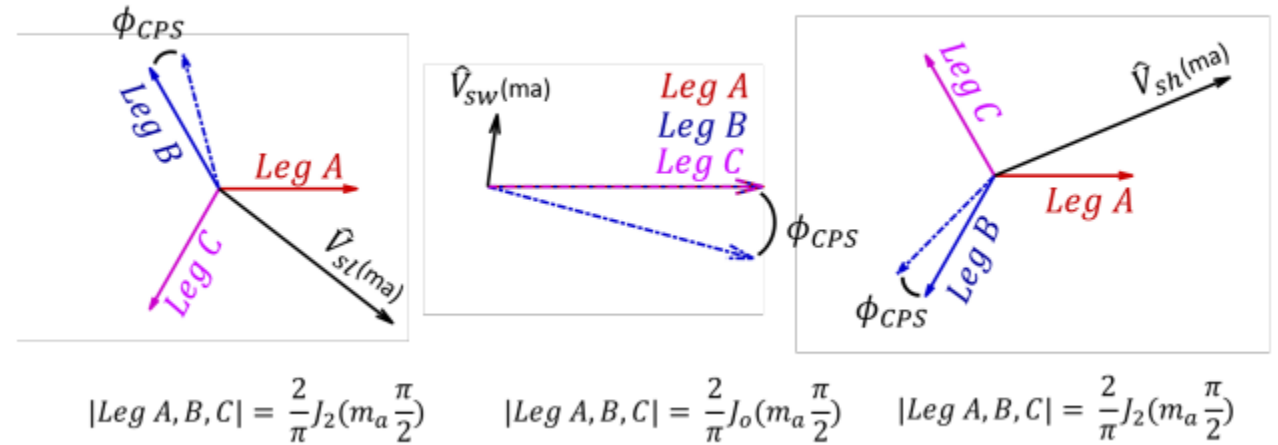





# Primary Side Voltage Control

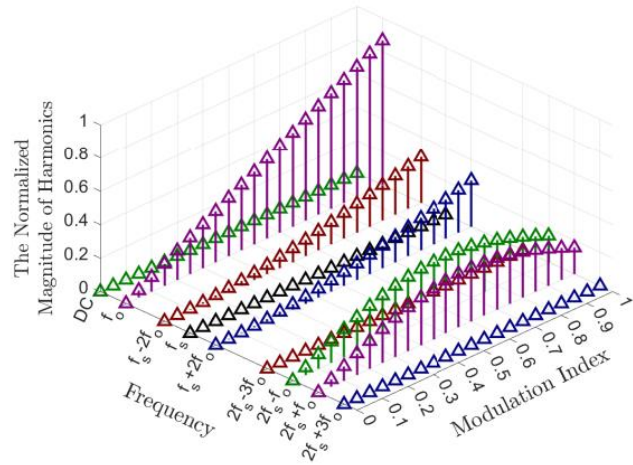
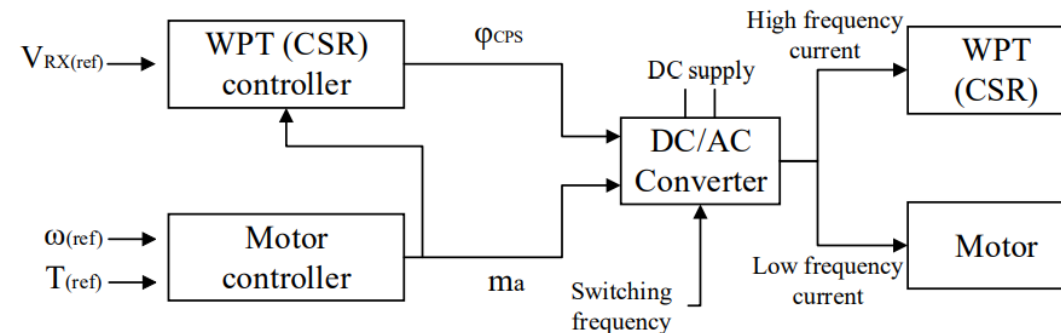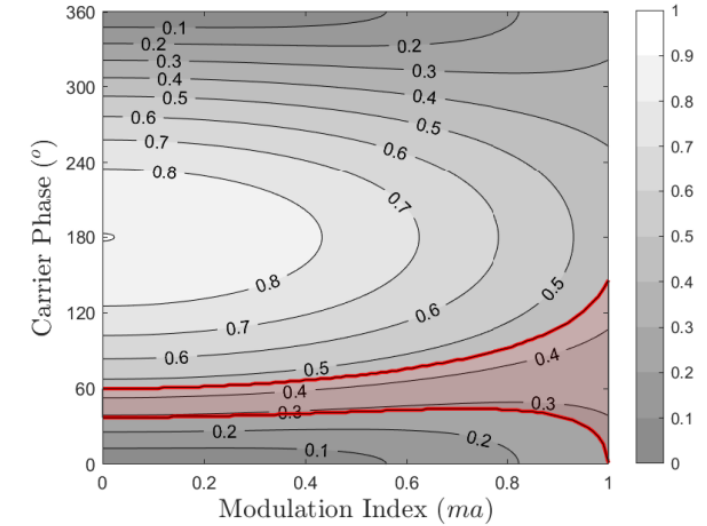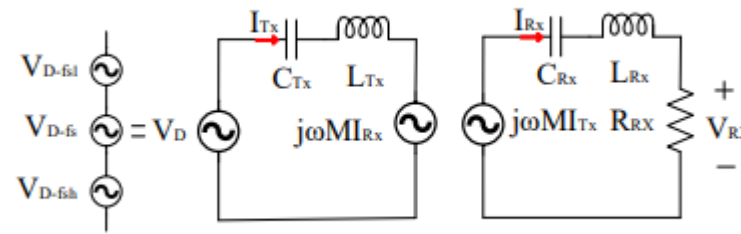
$$\text{Carrier phases} \begin{cases} \phi_{cA} = 0 \\ \phi_{cB} = \phi_{CPS} \\ \phi_{cC} = 0 \end{cases}$$





# Output Voltage Regulation

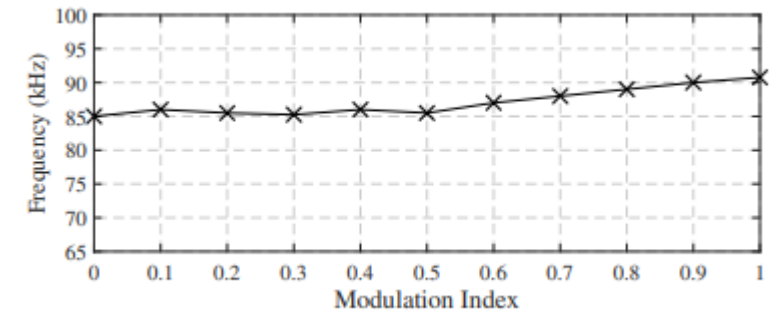
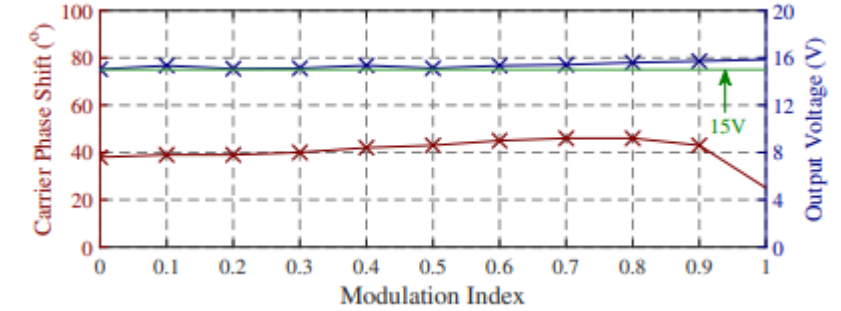
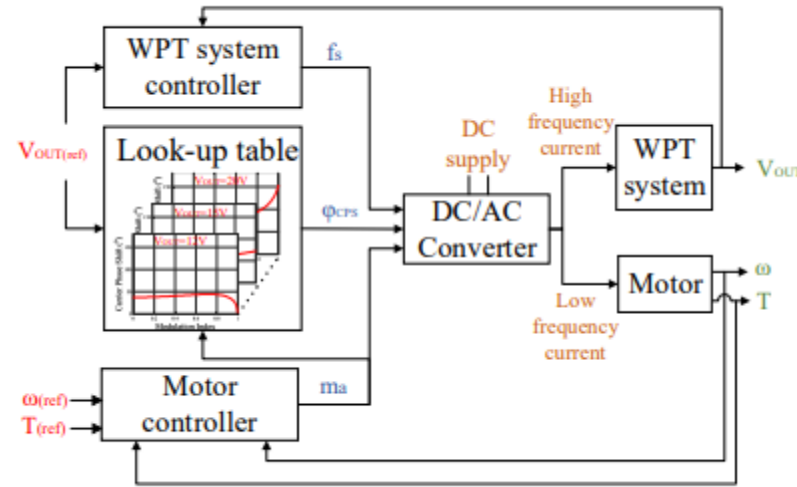
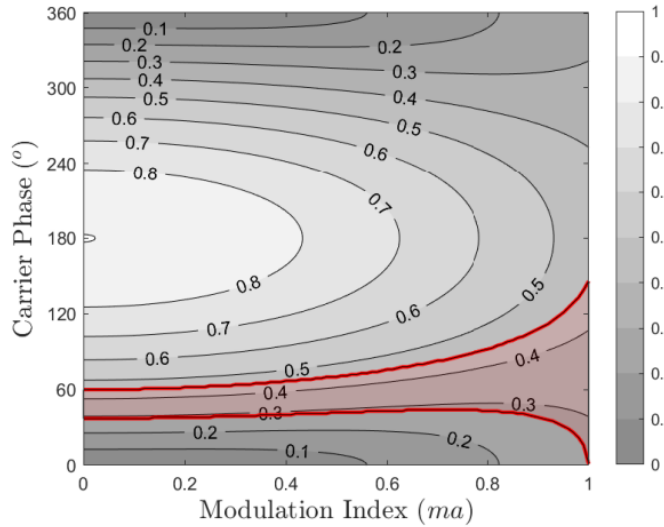



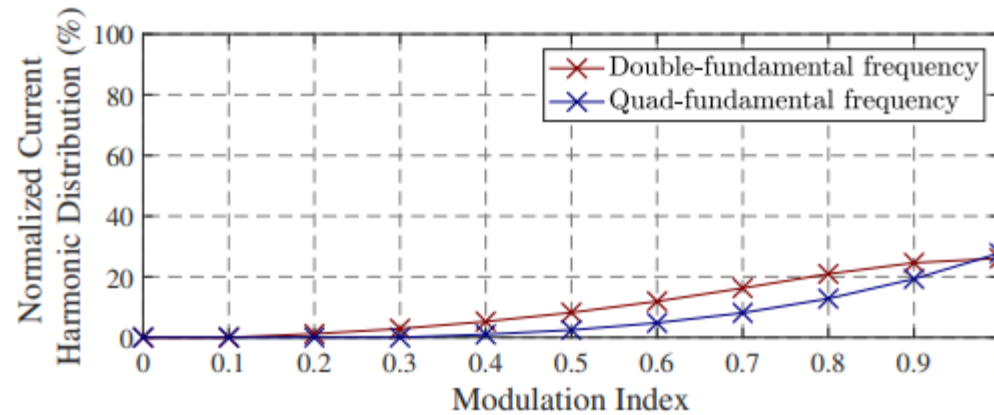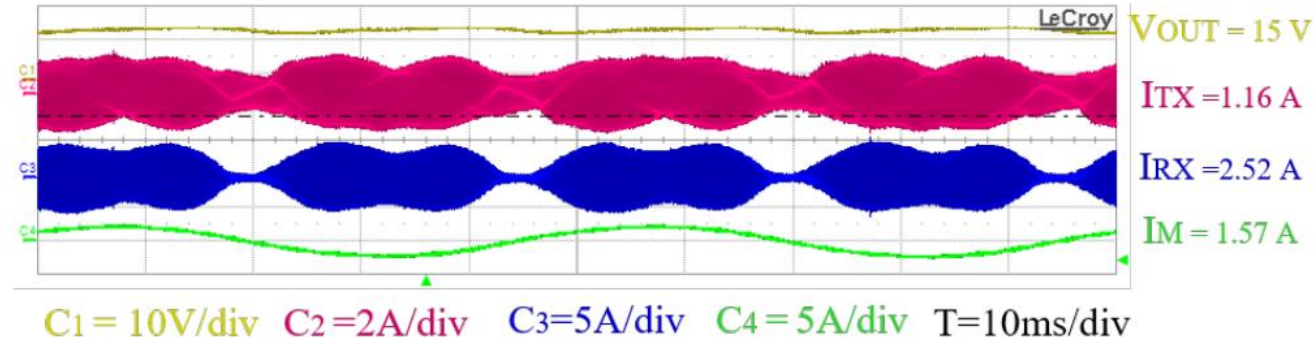
# Low-frequency Ripple at the Output Voltage




# Real-time algorithm

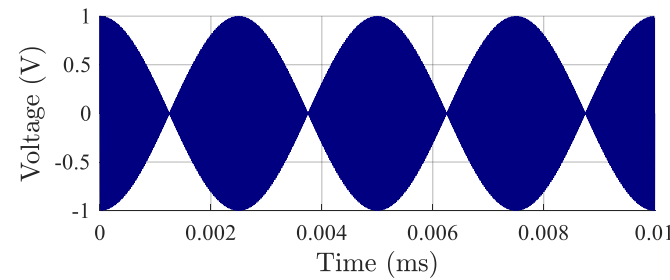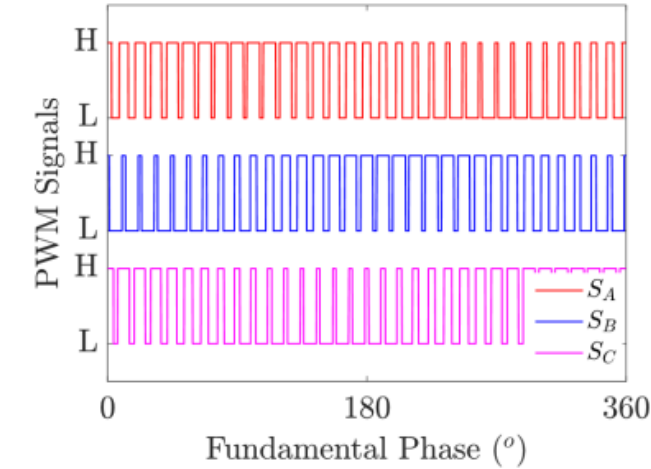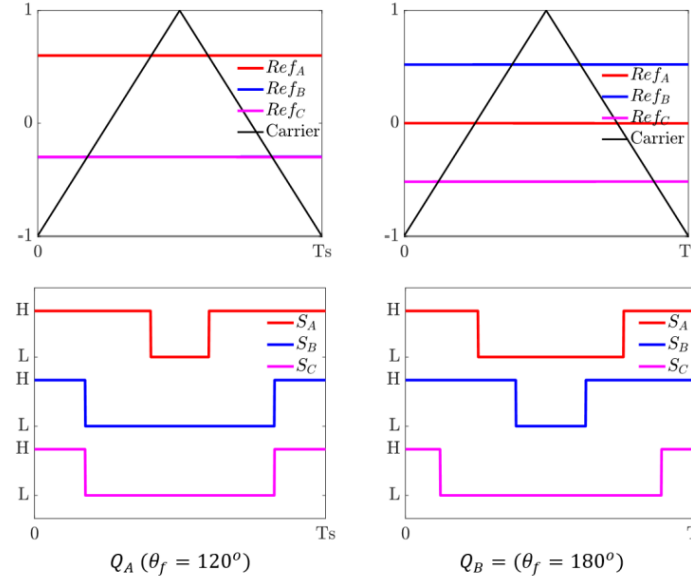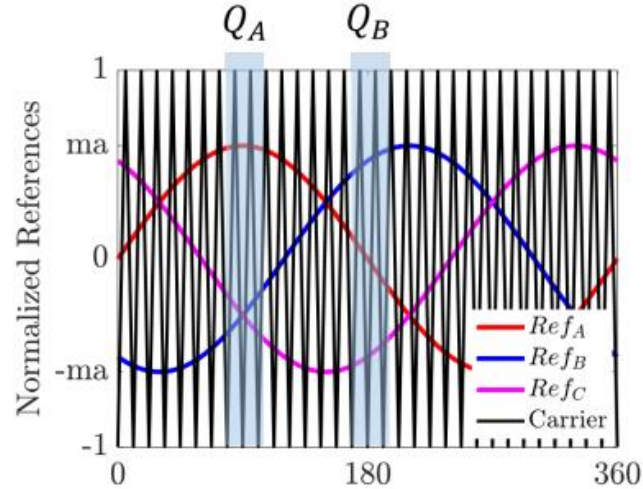

$$\hat{S}_{ABf_s} = \frac{2}{\pi} \sqrt{\sin(\pi D_A)^2 + \sin(\pi D_B)^2 - 2(\sin(\pi D_A)(\sin(\pi D_B)\cos(\phi_A - \phi_B))}$$


$$S_{AB}(t)^{f_s} = S_A(t)^{f_s} - S_B(t)^{f_s}$$
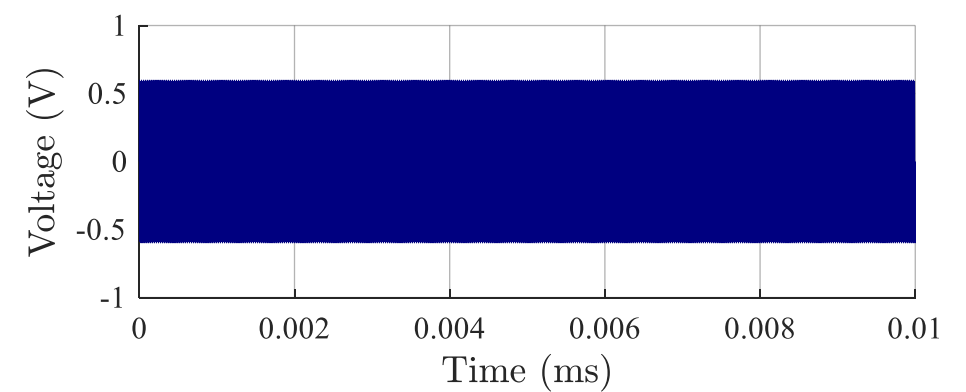
$$= \frac{2}{\pi} \sin(\pi D_A) \cos(2\pi f_s t + \phi_{C-A}) - \frac{2}{\pi} \sin(\pi D_B) \cos(2\pi f_s t + \phi_{C-B})$$

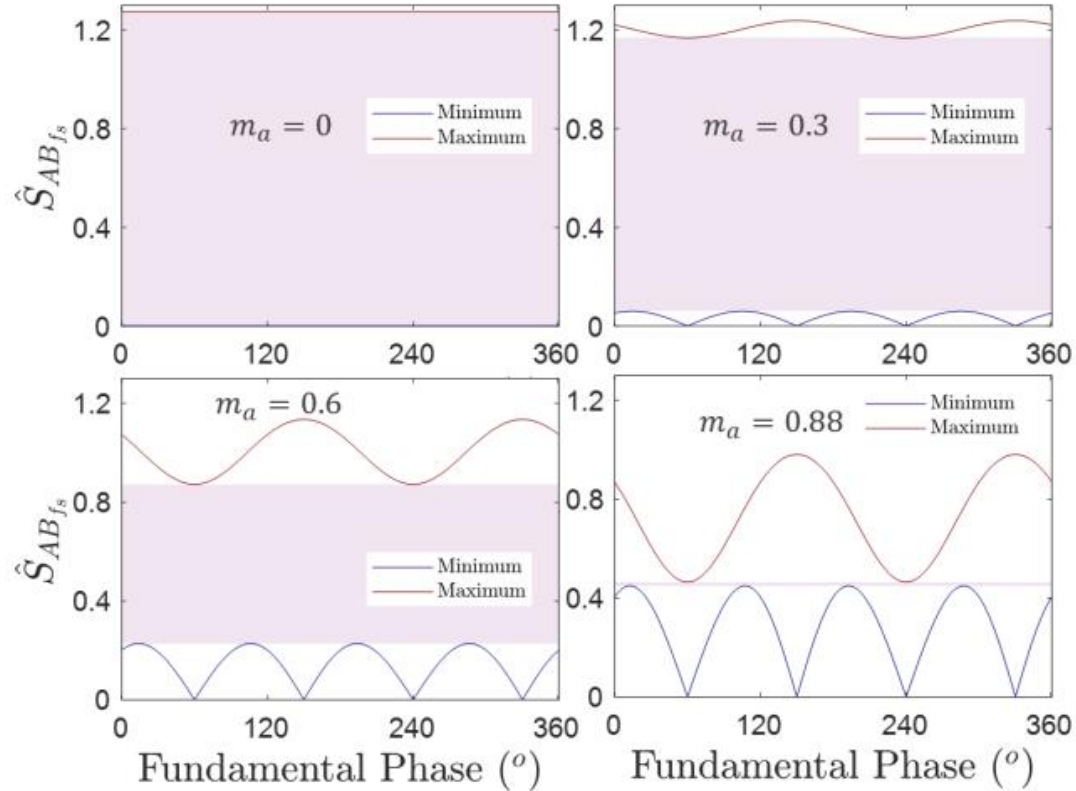
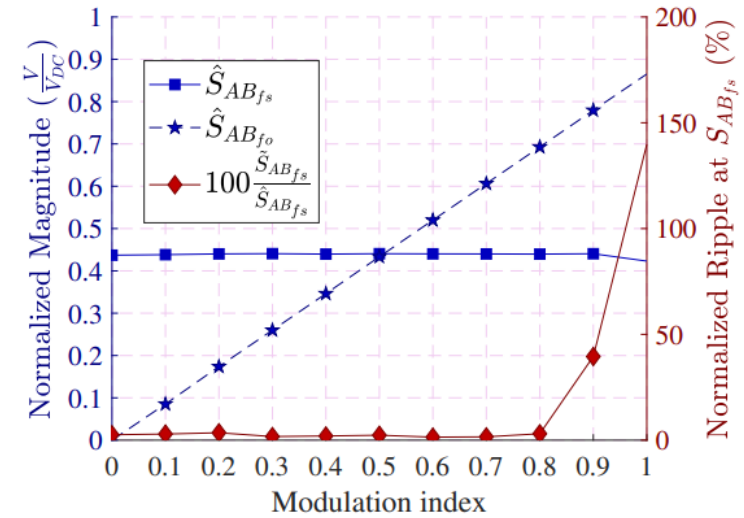
# Restrictions

$$\frac{2}{\pi} |\sin(\pi D_A) - \sin(\pi D_B)| < \hat{S}_{AB_{fs}}$$


$$< \frac{2}{\pi} |\sin(\pi D_A) + \sin(\pi D_B)|$$




$$\hat{S}_{AB_{fs}} = 0.43! \quad m_a < 0.88$$




# Experimental Validation

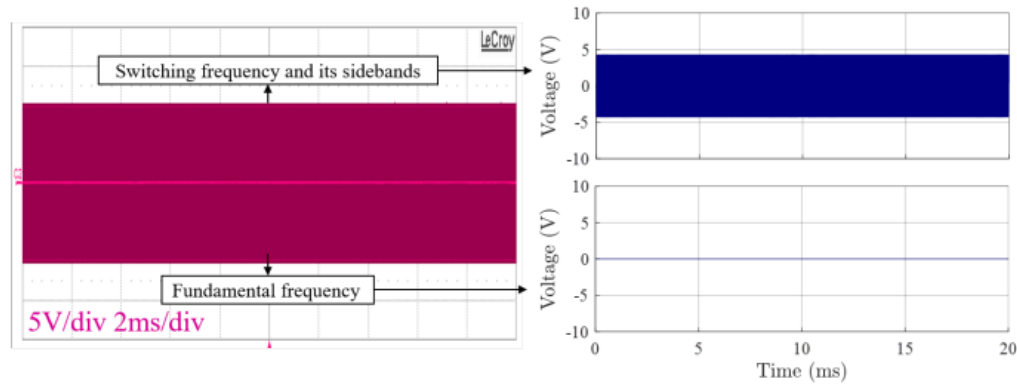


(a)  $m_A = 0$ .

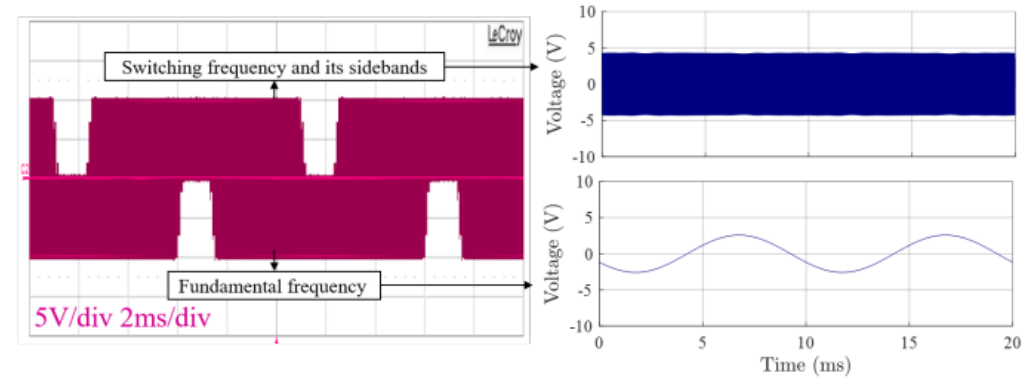

(b)  $m_A = 0.3$ .

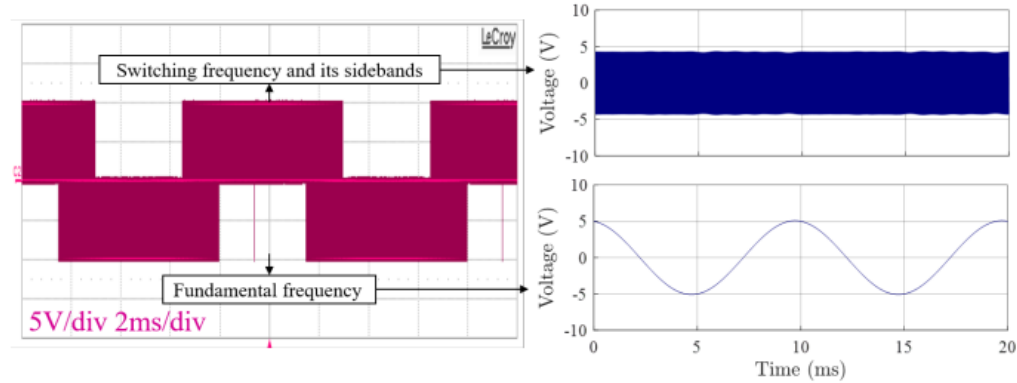

(c)  $m_A = 0.6$ .

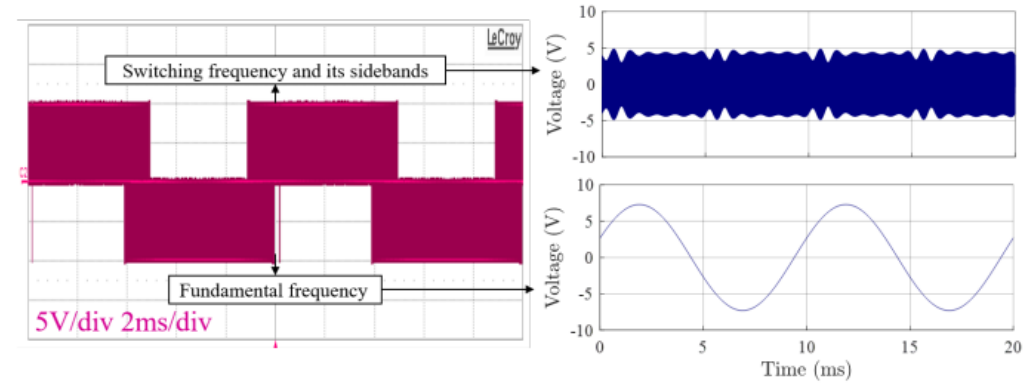


(d)  $m_A = 0.86$ .

# Future Works



- Motor drives have more than 2 wires
- Conventional WPT systems have 2 wires input
- ↓
- Multi-phase WPT systems

## Motivations:

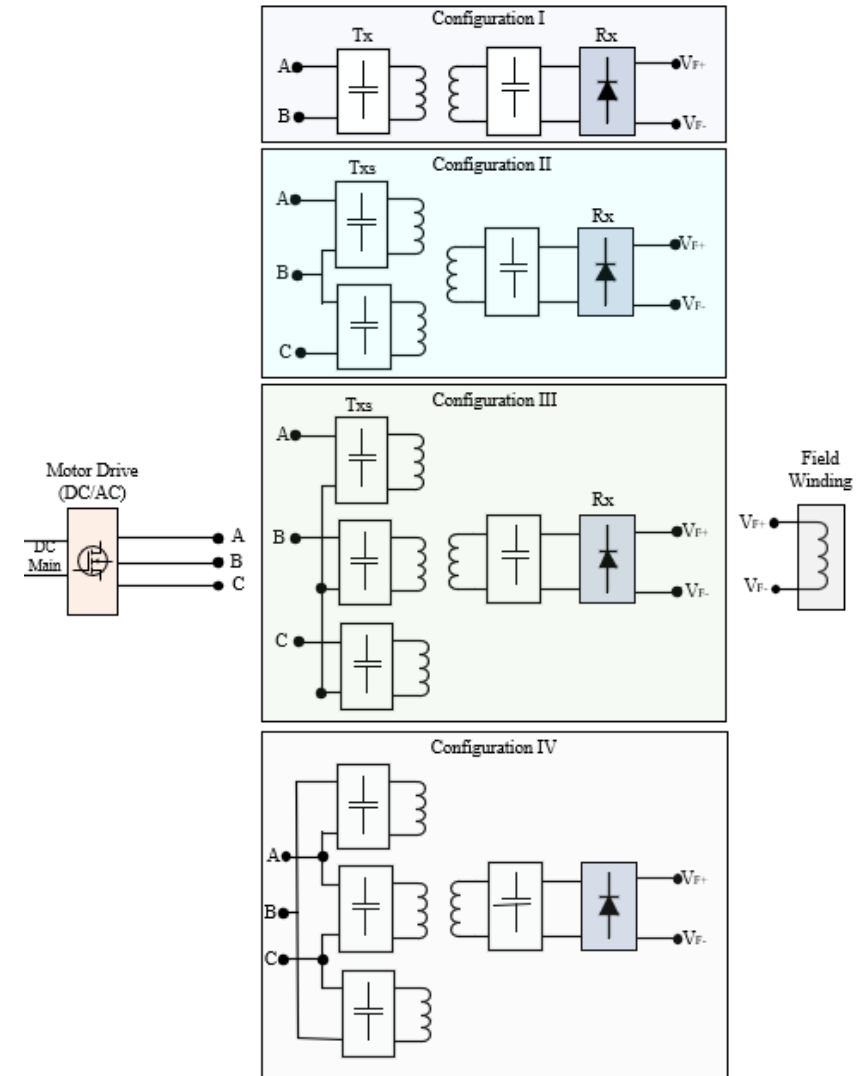1. To increase DC-link utilization rate
2. To increase power
3. To break the restrictions



# Future Works

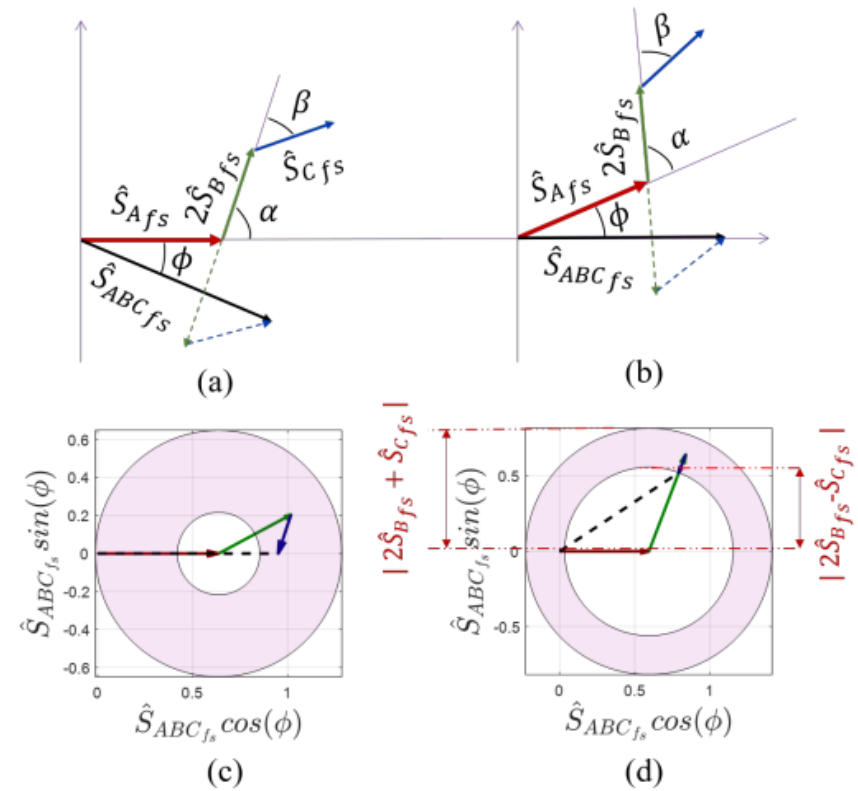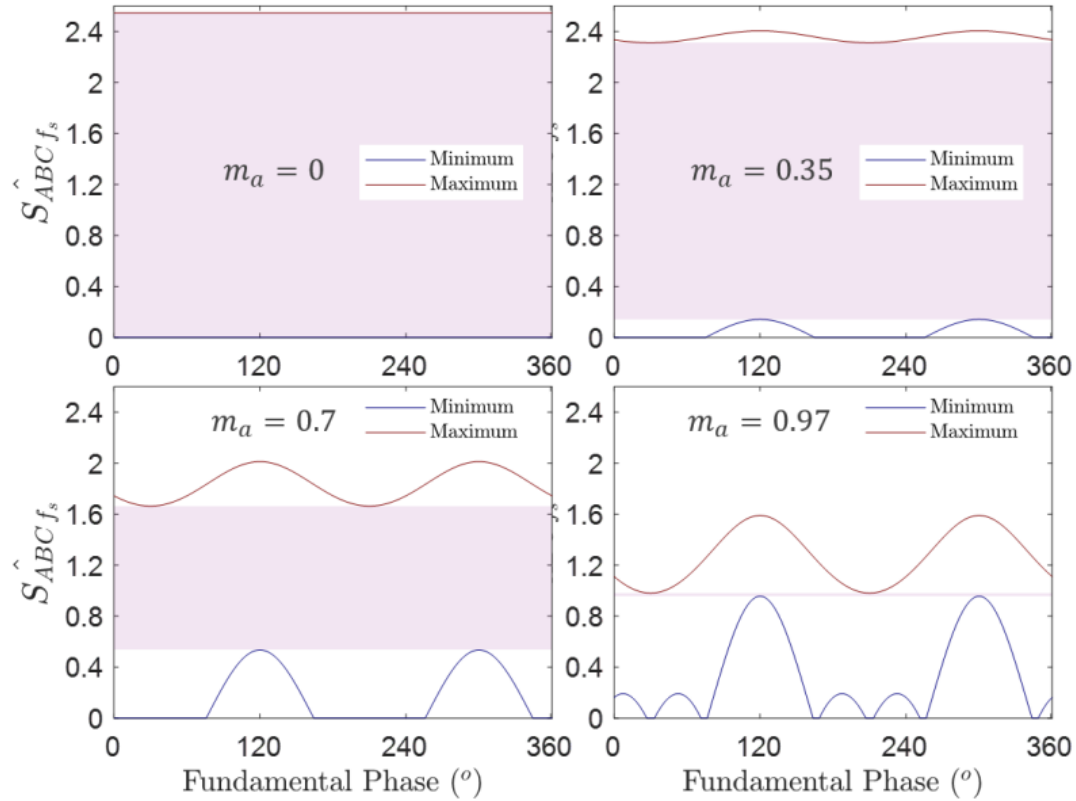

# Challenge- Calculation Burden!

$$\begin{aligned}\phi_{C-A} &= \phi \\ \phi_{C-B} &= \phi + \alpha \\ \phi_{C-C} &= \phi + \alpha + \beta\end{aligned}$$

$$\begin{aligned}\text{if } \hat{S}_{ABCf_s} < \hat{S}_{Af_s} - |2\hat{S}_{Bf_s} - \hat{S}_{Cf_s}| \text{ then} \\ &\quad \phi = 0; \\ \text{if } \hat{S}_{ABCf_s} > \hat{S}_{Af_s} + |2\hat{S}_{Bf_s} - \hat{S}_{Cf_s}| \text{ then} \\ &\quad \phi = 0; \\ \text{else} \\ \phi &= \arccos\left(\frac{\hat{S}_{Af_s}^2 - (2\hat{S}_{Bf_s} - \hat{S}_{Cf_s})^2 + \hat{S}_{ABCf_s}^2}{2\hat{S}_{Af_s}\hat{S}_{ABCf_s}}\right)\end{aligned}\quad (19)$$

$$\begin{aligned}\alpha &= 2\tan^{-1}\left(\frac{(\sigma_2 + \sigma_1)\sigma_4}{4\hat{S}_{Bf_s}\hat{S}_{Cf_s}}\right) \\ \beta &= 2\tan^{-1}\left(\frac{(\sigma_2 - \sigma_1)\sigma_4}{4\hat{S}_{Bf_s}\hat{S}_{Cf_s}}\right)\end{aligned}\quad (21)$$

where

$$\begin{aligned}\sigma_4 &= \hat{S}_{Af_s}^2 - \hat{S}_{Bf_s}^2 - \hat{S}_{Cf_s}^2 + \hat{S}_{ABCf_s}^2 \\ &\quad - 2\hat{S}_{Af_s}\hat{S}_{ABCf_s}\cos(\phi) + 2\hat{S}_{Bf_s}\hat{S}_{Cf_s}\end{aligned}\quad (22)$$

$$\begin{aligned}\sigma_3 &= \sigma_4 \left( \hat{S}_{Af_s}^2 + \hat{S}_{Bf_s}^2 - \hat{S}_{Cf_s}^2 + \hat{S}_{ABCf_s}^2 - 2\hat{S}_{Af_s}\hat{S}_{Bf_s} \right. \\ &\quad \left. - \hat{S}_{Af_s}\hat{S}_{ABCf_s}\cos(\phi) + \hat{S}_{Bf_s}\hat{S}_{ABCf_s}\cos(\phi) \right)\end{aligned}\quad (23)$$

$$\sigma_2 = \frac{8\hat{S}_{Bf_s}^2\hat{S}_{Cf_s}\hat{S}_{ABCf_s}\sin(\phi)}{\sigma_3}\quad (24)$$

$$\sigma_1 = \frac{4\hat{S}_{Bf_s}\hat{S}_{Cf_s}\sqrt{\sigma_4\left(-\hat{S}_{Af_s}^2 + \hat{S}_{Bf_s}^2 + \hat{S}_{Cf_s}^2 - \hat{S}_{ABCf_s}^2 + 2\hat{S}_{Bf_s}\hat{S}_{Cf_s} + 2\hat{S}_{Af_s}\hat{S}_{ABCf_s}\cos(\phi)\right)}}{\sigma_3}\quad (25)$$




---

**Thanks!**

---



# Compensation Topologies

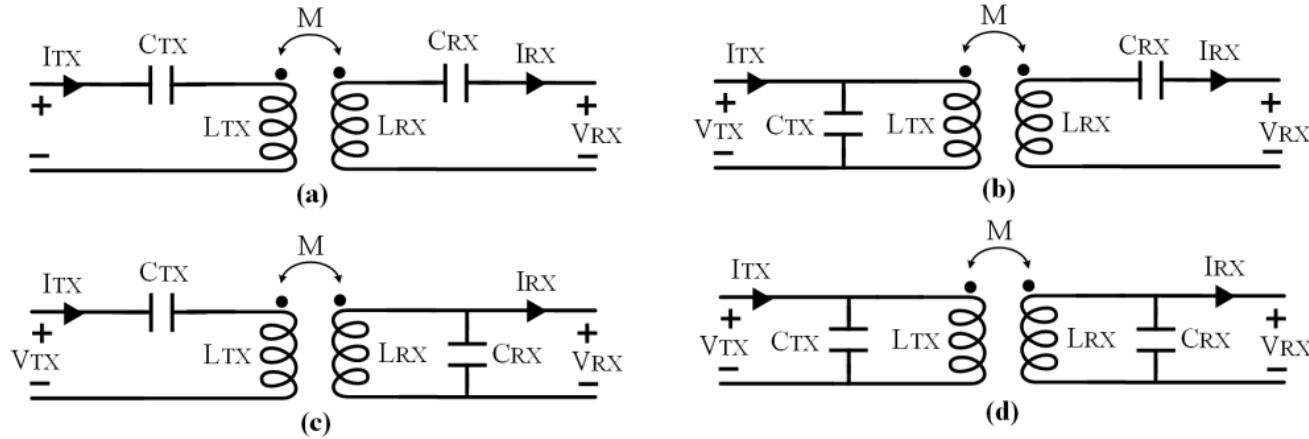

- a) Series-series
- b) Parallel-series
- c) Series-parallel
- d) Parallel-parallel


Series-Series Compensation	
Source Type	Voltage Source
Resonant frequency	Load Independent
Resonant frequency	Coupling Independent
No load operation	Short Circuit
Capacitor Size	Large

# Zero Voltage Switching

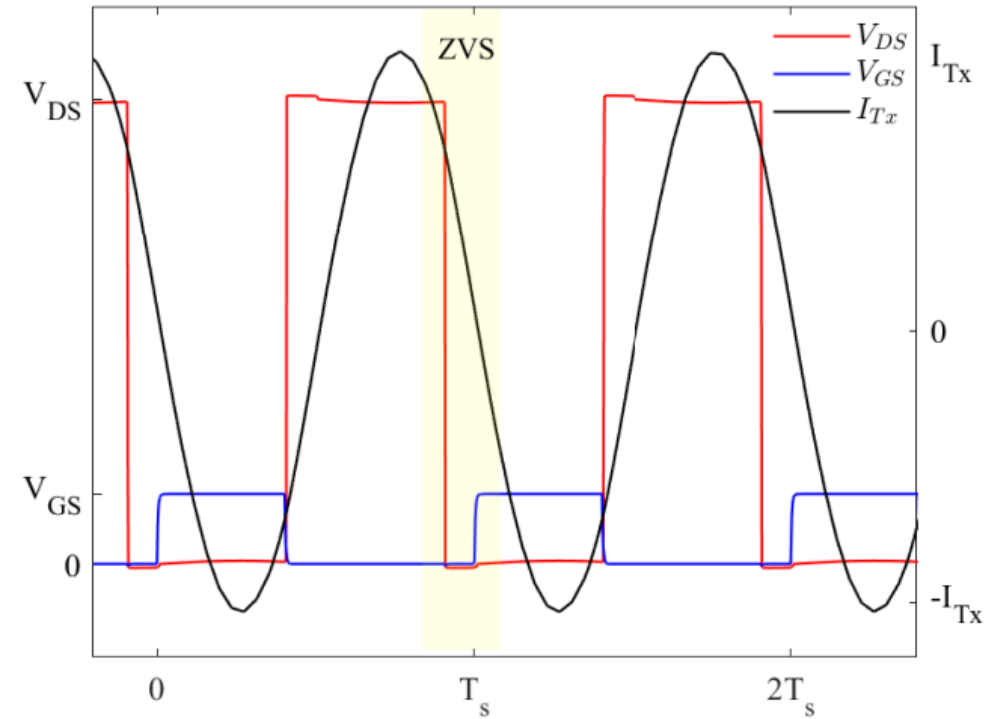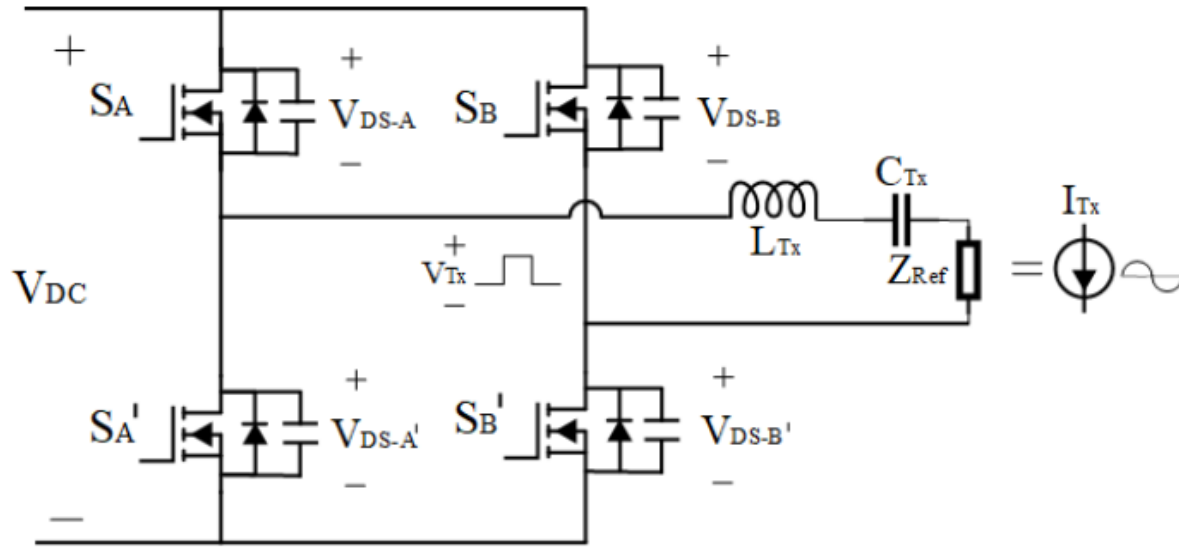

Inductive region → The capacitance of the switches discharges by the load current during dead time.


# Bifurcation Phenomenon

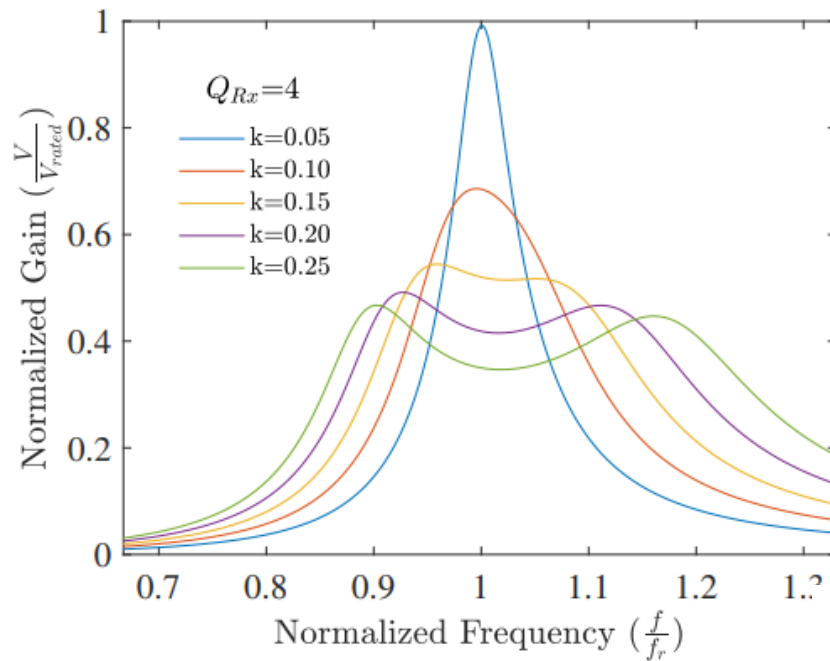

Double-peak  
 $\downarrow$   
 $f_{op} > f_r \rightarrow$  Inductive region  
 $\downarrow$

- Making control difficult
- Decreasing efficiency
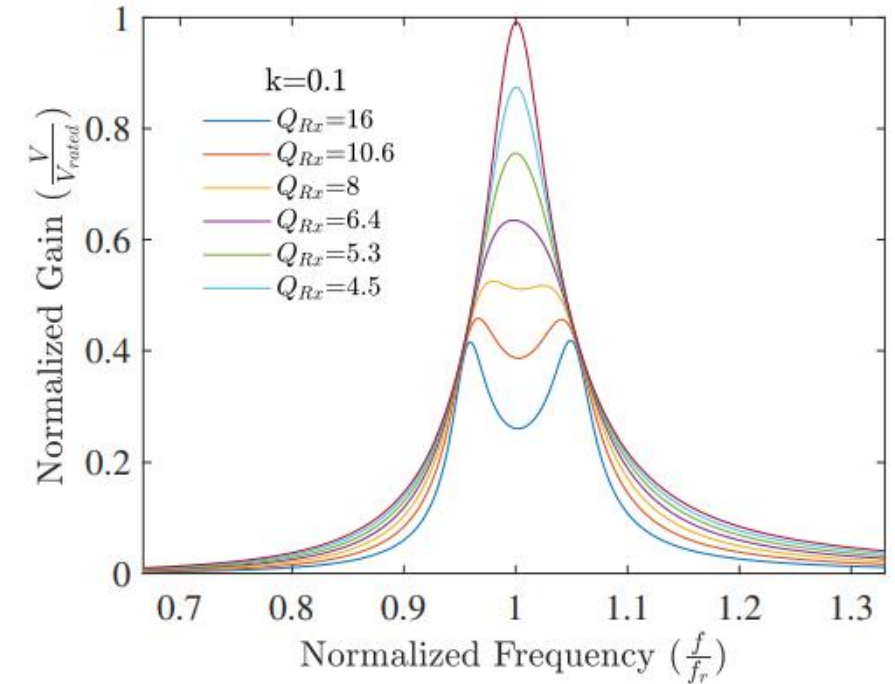
$$k_c = \frac{1}{Q_{Rx}} \sqrt{1 - \frac{1}{4Q_{Rx}^2}}$$



# Wireless Power Transfer System Design Procedure

## The Rated Voltages and Powers

Input Voltage ( $V_{BUS}$ )	100 V <sub>DC</sub>
IPT Output Voltage ( $V_{RX}$ )	20 V <sub>RMS</sub>
Motor Output Power ( $P_M$ )	500 W
IPT Output Power ( $P_o$ )	50 W

## The Motor Parameters

Armature resistance ( $R_a$ )	2 $\Omega$
Armature inductance ( $L_a$ )	7 mH
Motor electrical time constant ( $T_s$ )	3.5 ms

## The Drive Parameters

Duty cycle( $D$ )	0.15 – 0.85
Switching frequency ( $f_s$ )	< 100 kHz
Switching period ( $T_s$ )	> 10 $\mu$ s

$$V_{o,1^{st}}(rms) = \frac{4}{\sqrt{2}\pi} V_{Bus} \sin(\pi D)$$



$$0.15 < D < 0.85$$

$$40 V_{RMS} < V_{o,1^{st}}(rms) < 90 V_{RMS}$$

$$D = 0.15$$

$$D = 0.5$$


$$D = 0.85$$

$$Q_{RX} \rightarrow L_{RX} = \frac{Q_{RX} R_L}{\omega_o} \rightarrow M = \frac{V_{RX} V_{o,1^{st}}}{P_o \omega_o}$$




$$C_{TX,RX} = \frac{1}{L_{TX,RX}} \omega_o^2 \leftarrow L_{TX} = \frac{V_{o,1^{st}}^2}{k^2 \omega_o^2 Q_{RX}} \leftarrow k$$

# Wireless Power Transfer System Design

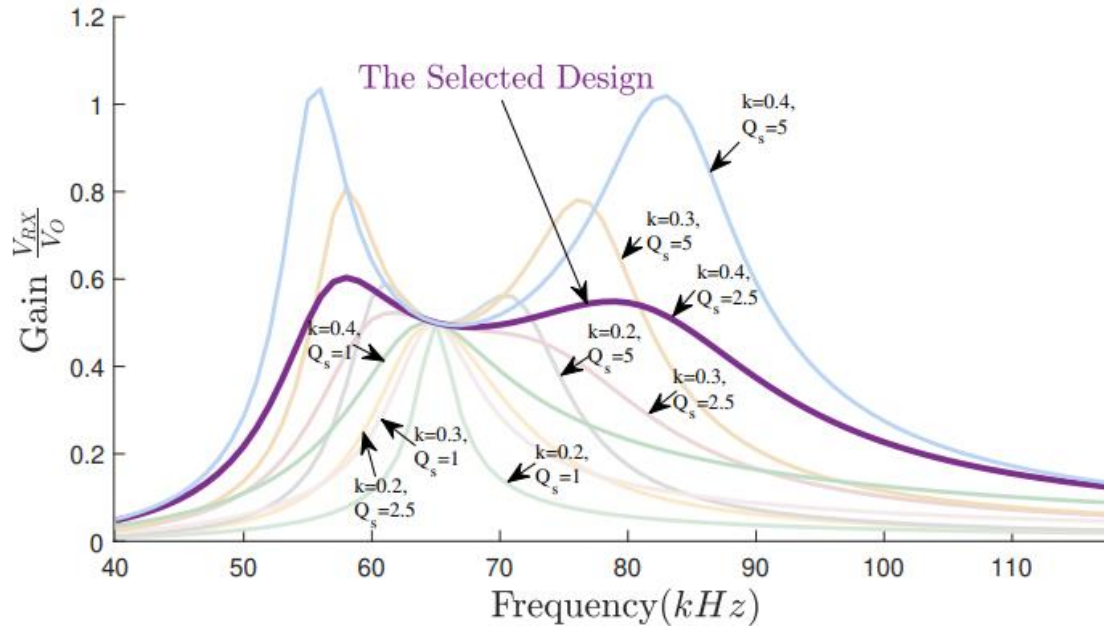

Receiver quality factor ( $Q_{RX}$ )	2.6
Resonant frequency ( $f_0$ )	65 kHz
Coupling factor ( $k$ )	0.40
Load resistance ( $R_L$ )	$8 \Omega$
Receiver coil inductance ( $L_{RX}$ )	$51 \mu H$
Mutual inductance ( $M$ )	$41 \mu H$
Transmitter coil inductance ( $L_{TX}$ )	$205 \mu H$
Receiver resonant capacitance ( $C_{TX}$ )	115 nF
Transmitter resonant capacitance ( $C_{RX}$ )	29 nF
Voltage gain at $f_o$	0.5

# Wireless Power Transfer System Design

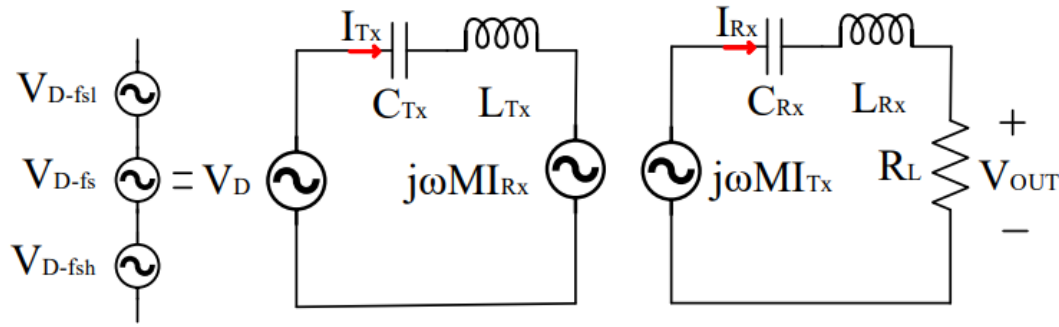

$$\omega_{rl} = \omega_r \sqrt{\frac{1}{1+k}}$$

$$\omega_{rh} = \omega_r \sqrt{\frac{1}{1-k}}$$

$$A_{WPT} = \left| \frac{V_{OUT}}{V_{IN}} \right|$$

$$\frac{dA_{WPT}}{dR_L} = 0$$

$$L_{Rx} = \frac{Q_{Rx} R_L}{\omega_{rh}} \rightarrow A_{WPT(\omega_{rh})} = \left| \sqrt{\frac{L_{Rx}}{L_{Tx}}} \right| \rightarrow L_{Tx} = \frac{L_{Rx}}{A_{WPT(\omega_{rh})}^2}$$

$$C_{Tx} = \frac{1}{\omega_r^2 L_{Tx}}$$


$$C_{Rx} = \frac{1}{\omega_r^2 L_{Rx}}$$

$$M = k \sqrt{L_{Tx} L_{Rx}}$$




# Wireless Power Transfer System Design


Initial/Chosen Parameters	Values	Derived Parameters	Values
$P_{\text{rated}}$	24 W	$A_{\text{WPT}}$	0.5
$V_D$	$30 V_{\text{RMS}}$	$R_L$	$9.3 \Omega$
$V_{\text{out}}$	$15 V_{\text{RMS}}$	$L_{\text{Rx}}$	$50 \mu\text{H}$
$f_{rh}$	85 kHz	$L_{\text{Tx}}$	$200 \mu\text{H}$
$Q_{\text{Rx}}$	2.9	$M$	$40 \mu\text{H}$
$k$	0.4	$f_r$	65.85 kHz
		$C_{\text{Tx}}$	29.2 nF
		$C_{\text{Rx}}$	117 nF

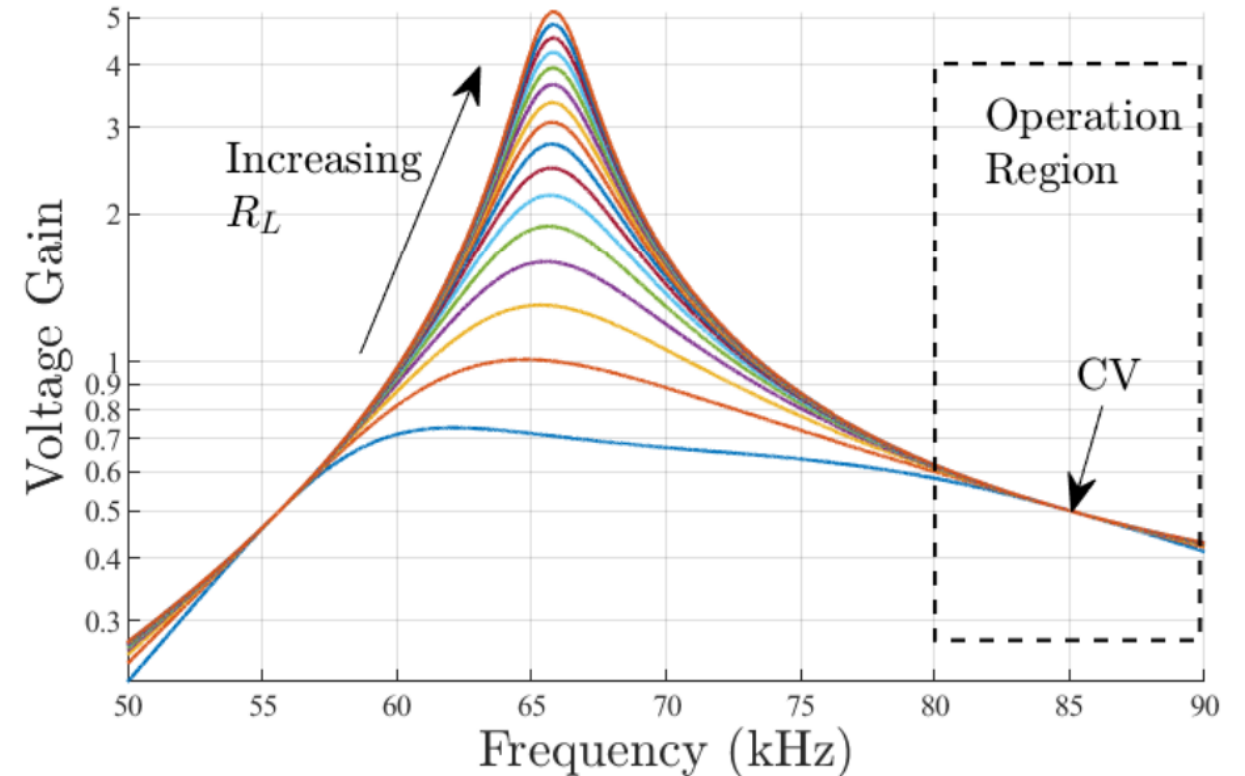
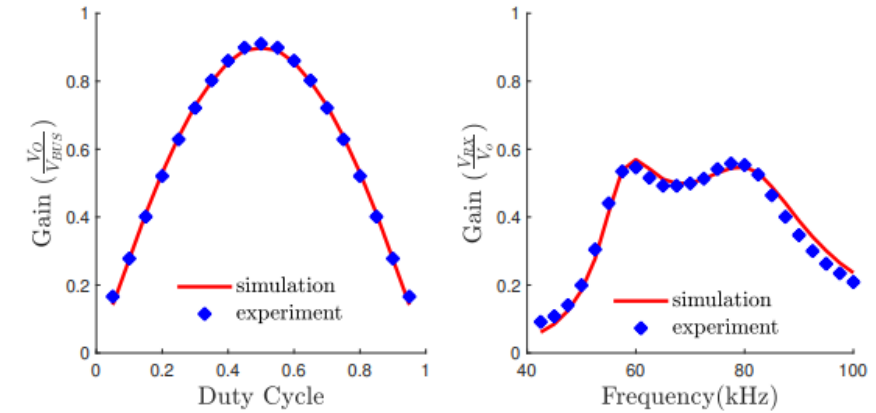
# Experimental Results- WPT System Validation




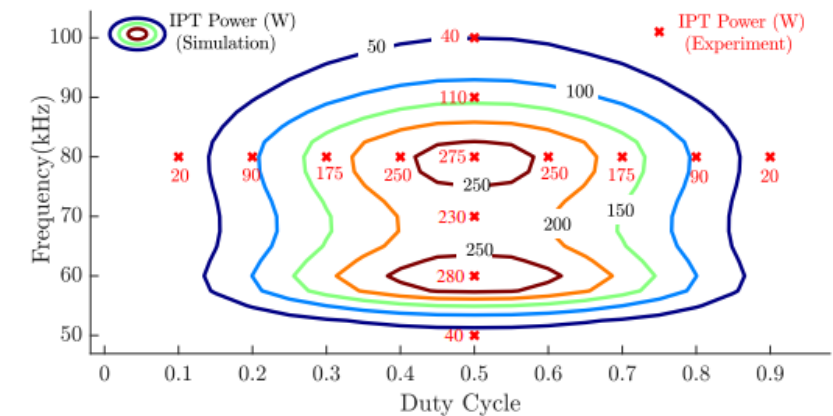(a) Duty cycle-gain characteristic of WPT at 80 kHz. (b) Frequency-gain characteristic of WPT ( $D = 0.5$ ).



	Design values	Measured values
Transmitter inductance	204 $\mu$ H	205 $\mu$ H
Receiver inductance	52 $\mu$ H	51 $\mu$ H
Mutual inductance	41 $\mu$ H	40 $\mu$ H

# Wireless Power Transfer System Design

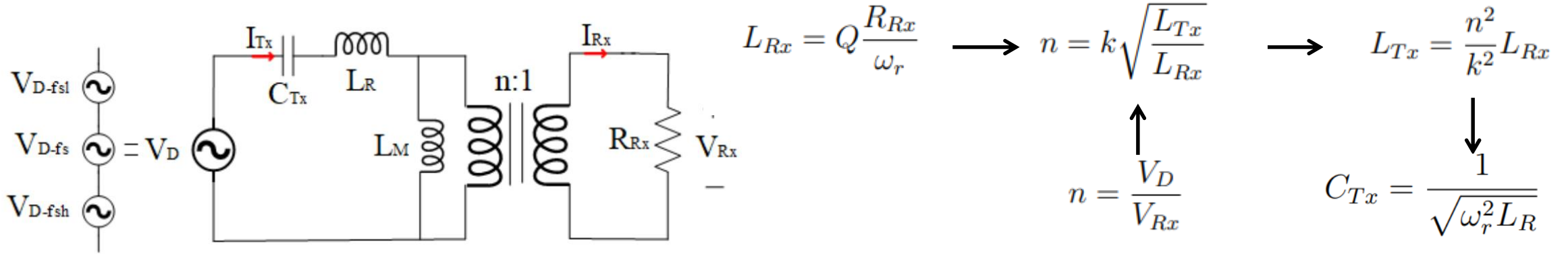

Initial/Chosen Parameters	Values	Derived Parameters	Values	Experimental Values
$P_{rated}$	30 W	$V_{Rx}$	7.56	-
$V_D$	40 $V_{RMS}$	$R_{Rx}$	0.97 $\Omega$	-
$V_{OUT}$	6 $V_{DC}$	$n$	5.95	-
$f_{rh}$	60 kHz	$L_{Tx}$	1510 $\mu H$	-
$Q_{Rx}$	2.5	$L_{Rx}$	6.5 $\mu H$	-
$k$	0.7	$M$	42 $\mu H$	-
$R_L$	1.2 $\Omega$	$C_{Tx}$	6.7 nF	-